 


# EELE 5131

## Assignment 3 — Winter 2019

### Problems

1. The following layout is for a process with p-type substrate. Draw an schematic diagram of the circuit in this layout. Use the provided node labels.



2. Using thin-oxide PMOS transistors (p<sub>ch</sub> model), design a simple current mirror according to the following specifications:
  - Input current is 3  $\mu\text{A}$
  - Nominal output current is 2  $\mu\text{A}$
  - Supply voltage is 1.8 V
  - Maximum operating output voltage is 1.6 V
  - $\sigma(\Delta I_o/I_o)$  due to mismatch must be 2% or lower. Consider  $A_{VT} = 4.1 \text{ mV}\mu\text{m}$  and  $A_\beta = 0.03 \mu\text{m}$ .
  - $\Delta I_o/I_o \leq 3\%$  for an output voltage change of 1 V.
  - Use unit transistors for improved matching. Try to minimize gate area.
  - Specify final design as follows: unit transistor dimensions and circuit diagram.
3. Perform the “6. Layout Creation” tutorial and create the layout for the current mirror designed in Problem 2. Define 3 connections (pins) for the layout: vdd!, iin, iout. Export your layout to stream format using the instructions in the tutorial page (“8. Brief instructions ...”) and e-mail the layout to the instructor as an attachment.
4. A diode-connected thin-oxide NMOS transistor (n<sub>ch</sub> model) is rectangular and has the following dimensions:  $W = 10 \mu\text{m}$ ,  $L = 1 \mu\text{m}$  and the width of the drain and source regions is  $0.48 \mu\text{m}$ . The transistor is biased such that  $i_f = 10$  and the source and bulk are grounded.
  - (a) Calculate  $I_D$  and  $V_G$ .
  - (b) Calculate the extrinsic and intrinsic capacitances that contribute to the drain-ground capacitance. Which capacitance is the dominant component?
  - (c) Calculate the input admittance seen from the drain node to ground as a function of frequency.