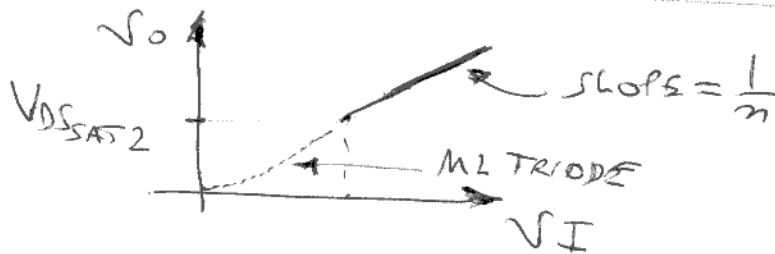


EEL 5131 : SOLUTIONS TO ASSIGNMENT #4 (2019) (1)

$$1) \quad \frac{V_I - V_{th}}{nV_T} - \frac{V_o}{V_T} = f(i_{f1}) \quad (1)$$

$$V_o = \frac{V_I - V_{th}}{n} - V_T f(i_{f1})$$

$$V_o = \frac{1}{n} V_I - \left[\frac{V_{th}}{n} + V_T f(i_{f1}) \right] \quad \text{VALID FOR } M_1, M_2 \text{ ACTIVE}$$




$$b) \quad V_{o_{MIN}} = V_{DSAT2} = V_T (3 + \sqrt{1 + i_{f2}'})$$

FROM (1) $V_I = V_{th} + nV_o + nV_T f(i_{f1})$

$$\therefore V_{I_{MIN}} = V_{th} + nV_{DSAT2} + nV_T f(i_{f1})$$

$$V_{o_{MAX}} = V_{DD} - V_{DSAT1} = V_{DD} - V_T (3 + \sqrt{1 + i_{f1}'})$$
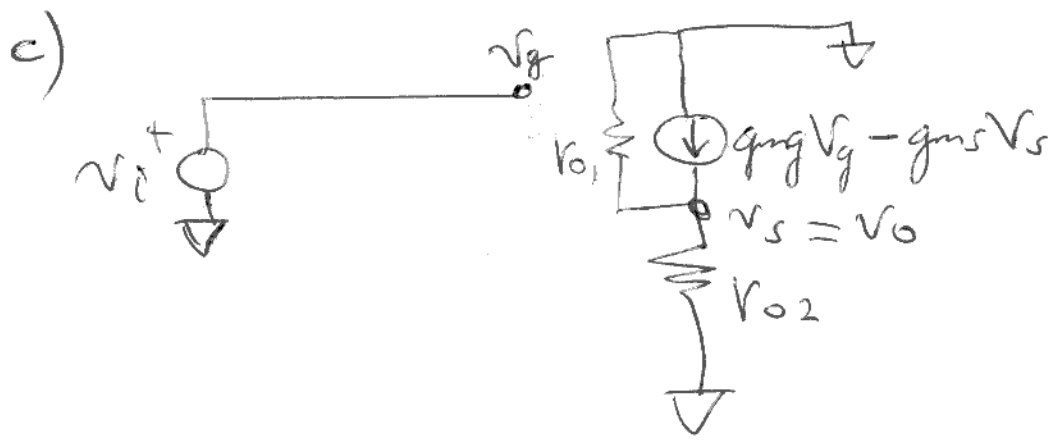
$$\therefore V_{I_{MAX}} = V_{th} + n(V_{DD} - V_{DSAT1}) + nV_T f(i_{f1})$$




$$v_o = (g_m g_m v_i - g_m s v_o) (r_{o1} // r_{o2})$$

$$v_o (1 + g_m s (r_{o1} // r_{o2})) = g_m g_m (r_{o1} // r_{o2}) v_i$$

$$\frac{v_o}{v_i} = \frac{g_m g_m (r_{o1} // r_{o2})}{1 + g_m s (r_{o1} // r_{o2})}$$

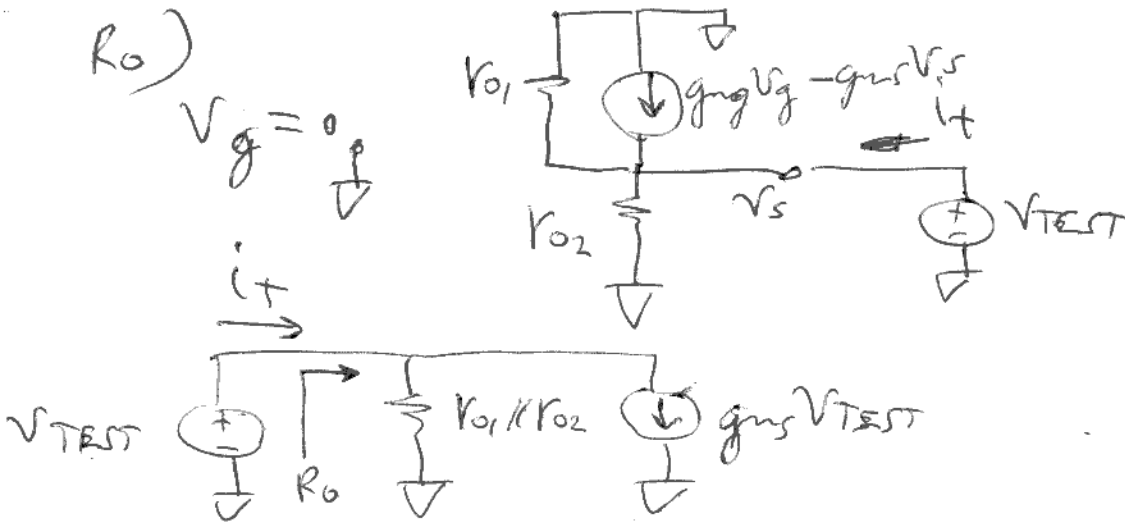IF $g_m g_m (r_{o1} // r_{o2}) \gg 1 \Rightarrow \boxed{\frac{v_o}{v_i} \approx \frac{1}{n}}$
 (SINCE $g_m g_m = \frac{g_m s}{n}$)



$$\boxed{R_o = \frac{v_{TEST}}{i_t} = \frac{1}{\frac{1}{r_{o1}} + \frac{1}{r_{o2}} + g_m s} \approx \frac{1}{g_m s}}$$

$$I_{F2} = I_{F3} = \frac{6\mu A}{I_{SQ2} \times 6} = 10$$

$$r_{o2} = \frac{1\mu m}{0.07\mu m \times 6\mu A} = 2.38 M\Omega$$

$$I_{F1} = \frac{6\mu A}{I_{SQ2} \times 15} = 4$$

$$r_{o1} = r_{o2} = 2.38 M\Omega$$

$$g_{m5} = \frac{2 I_{S1}}{V_T} (\sqrt{1 + \eta^2} - 1) = 0.143 mS$$

$$g_{m4} = 0.110 mS$$

$$\left[a_v = \frac{v_o}{v_i} = 0.765, \text{ USING APPROX: } \frac{1}{\eta} = 0.769 \right]$$

$$\left[R_o = 69 \Omega, \text{ USING APPROX } \frac{1}{g_{m5}} = 6993 \Omega \right]$$

$$2). a_v = g_{m1} (r_{o1} \parallel r_{o2}) \geq 100 \quad (a)$$

$$V_{DD} - (V_{DSSAT1}) \geq 1.5V \quad (b)$$

$$V_{DSSAT2} \leq 0.25V \quad (c)$$

$$I_{REF} \geq C_L \times \frac{dv_o}{dt} = 0.5pF \times \frac{50V}{\mu s} \quad (d)$$

• LOW CURRENT, AREA

• FROM (b), $i_{F1 \text{ MAX}} = ?$

(4)

$$\underbrace{V_{DD}}_{= 1.2V} - V_T (1 + \sqrt{1 + i_{F1}}) \geq 1.5V$$

$$i_{F1} \leq \left(\frac{0.3V}{V_T} - 1 \right)^2 - 1 = \underline{110}$$

• FROM (c), $i_{F2 \text{ MAX}} = \left(\frac{0.25V}{V_T} - 1 \right)^2 - 1 = \underline{73}$

• FROM (d) $I_{REF \text{ MIN}} = \underline{25 \mu A}$

• FROM (a):

$$\frac{2}{n V_T} \frac{1}{(\sqrt{1 + i_{F1}} + 1)} \cdot \frac{1}{\frac{\left| \frac{\partial X_D}{\partial V_{DS}} \right|_p}{L_1} + \frac{\left| \frac{\partial X_D}{\partial V_{DS}} \right|_n}{L_2}} \geq 100$$

SINCE $\left| \frac{\partial X_D}{\partial V_{DS}} \right|_n = \left| \frac{\partial X_D}{\partial V_{DS}} \right|_p$ (FOR THIS PROBLEM), MAKE

$$L_1 = L_2 = L$$

$$\frac{L}{n_p V_T \left| \frac{\partial X_D}{\partial V_{DS}} \right|} \frac{1}{(\sqrt{1 + i_{F1}} + 1)} \geq 100$$

$$L \geq 0.24 \mu m (\sqrt{1 + i_{F1}} + 1) \quad (1)$$


∴ $i_{F \text{ MAX}}$ FOR $L = 0.8 \mu m$ (LOW AREA) = $\underline{4.44}$

BUT THIS RESULTS IN LARGE W TO CONDUCT 25 μA

• IS THERE ANY OPTIMUM L?

AREA $A = W \times L \Rightarrow W = \frac{A}{L} \Rightarrow \frac{W}{L} = \frac{A}{L^2}$

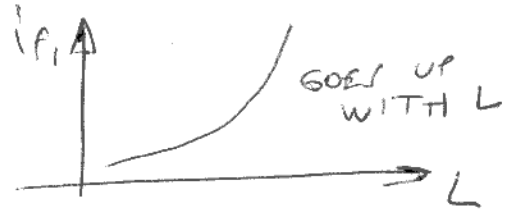
FROM (1) $i_f = \left(\frac{L}{0.24\mu m} - 1 \right)^2 - 1$



ALSO: $16\mu A = I_{SQP} \frac{W}{L} i_f$ (2)

$= I_{SQP} \frac{A}{L^2} \left[\left(\frac{L}{0.24\mu m} - 1 \right)^2 - 1 \right]$

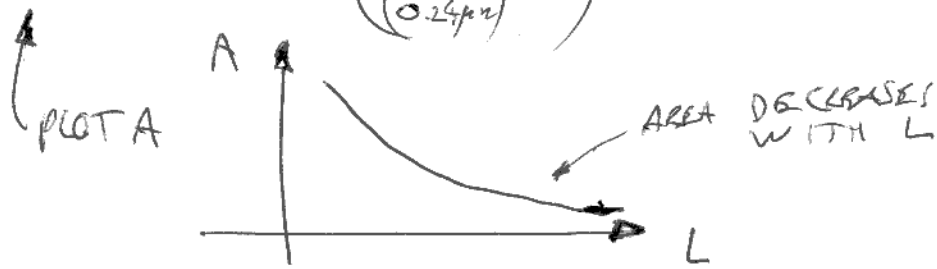$A = \frac{16\mu A}{I_{SQP}} \frac{L^2}{\left(\left(\frac{L}{0.24\mu m} - 1 \right)^2 - 1 \right)}$



STRATEGY FOR MIN. AREA: MAKE i_f CLOSE TO THE MAX $i_f = 100 \rightarrow$ USE (1) AND FIND L

$L = 2.65\mu m$

GET W FROM (2)

$W = 18.5\mu m$

GATE AREA $\approx 49.0\mu m^2$

(USING $L = 0.8\mu m \Rightarrow$ GATE AREA $\approx 109\mu m^2$)

$$L_2 = L_1 = 2.65 \mu\text{m} \Rightarrow W_2 = \frac{16 \mu\text{A} \times 2.65 \mu\text{m}}{I_{\text{SEN}} \times 60} \quad (6)$$

SET $i_{f2} = i_{f3} = 60$

$$W_2 = 7.06 \mu\text{m}$$

FINAL DESIGN :

$$\left(\frac{W}{L}\right)_1 = \frac{18.5 \mu\text{m}}{2.65 \mu\text{m}}$$

$$i_{f1} \approx 100$$

$$i_{f2} \approx 60$$

$$\left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_3 = \frac{7 \mu\text{m}}{2.65 \mu\text{m}}$$

$$I_{\text{REF}} = 16 \mu\text{A}$$

V_I ?

$$|V_{G1}| = V_{DD} - V_I$$

$$|V_{G1}| - |V_{thp}| = nV_T \ln(i_{f1})$$

$$V_{DD} - V_I = |V_{thp}| + nV_T \ln(i_{f1})$$

$$V_I = V_{DD} - |V_{thp}| - nV_T \ln(i_{f1})$$

$$\approx \underline{1.02 \text{ V}}$$

3) a) $I_{D1} = 10 I_{D2}$ ← DUE TO PMOS MIRROR GAIN (7)

$$V_{G1} = V_{th} + nV_T \mathcal{F}(i_{F1})$$

$$V_{G2} = V_{th} + nV_{S2} + nV_T \mathcal{F}(i_{F2})$$

• SINCE $V_{G1} = V_{G2} \Rightarrow nV_T \mathcal{F}(i_{F1}) = nV_{S2} + nV_T \mathcal{F}(i_{F2})$

$$V_{S2} = V_T [\mathcal{F}(i_{F1}) - \mathcal{F}(i_{F2})]$$

$$V_{S2} = V_T [\mathcal{F}(10 i_{F2}) - \mathcal{F}(i_{F2})]$$

VALID FOR
ANY INVERSION
LEVEL

• IF M_1, M_2 IN WEAK INVERSION,

$$\mathcal{F}(i_F) \approx \left(\ln \frac{i_F}{I_0} \right) - 1$$

$$\boxed{V_{S2} = V_T [\ln(10 i_{F2}) - \ln(i_{F2})]} = \boxed{V_T \ln 10}$$

V_{S2} IS PTAT

b) $V_{S2} = 26 \text{ mV} \times \ln(10) = \underline{59.9 \text{ mV}}$

$\therefore I_{D2} = \frac{V_{S2}}{R} = \frac{59.9 \text{ mV}}{100 \text{ k}\Omega} \approx \underline{600 \text{ nA}}$

c) $\left. \begin{array}{l} i_{F1} = 0.1 \\ I_{D1} = 10 I_{D2} = 6 \mu\text{A} \end{array} \right\} \left(\frac{W}{L} \right)_1 = \left(\frac{W}{L} \right)_2 = \underline{600}$

$\left. \begin{array}{l} i_{F3} = 0.1 \\ I_{D3} = 600 \text{ nA} \end{array} \right\} \left(\frac{W}{L} \right)_3 = \underline{260} \quad \left(\frac{W}{L} \right)_4 = 10 \left(\frac{W}{L} \right)_3$

$$4) \quad \begin{aligned} i_{f1} &= i_{f2} = 20 \\ i_{f3} &= i_{f4} = 80 \\ i_{f5} &= 150 \end{aligned}$$

$$L = 2 \mu\text{m}, \quad V_{DD} = 1.8\text{V}, \quad C_L = 0.5\text{pF}$$

$$a) \quad V_{IC_{max}} = \underbrace{V_{DD}}_{1.8\text{V}} - \underbrace{V_{DSSAT5}}_{0.397\text{V}} - \underbrace{V_{GS1}}_{?}$$

$$\frac{|V_{G1}| - |V_{thp}|}{n V_T} - \frac{|V_{DSSAT5}|}{V_T} = f(i_{f1})$$

$$|V_{G1}| = |V_{thp}| + n|V_{DSSAT5}| + n V_T f(i_{f1})$$

$$\text{BUT } |V_{G1}| = -V_{ICM} + V_{DD}$$

$$\boxed{\therefore V_{ICM_{max}} = \underbrace{V_{DD}}_{1.8\text{V}} - \underbrace{|V_{thp}|}_{= 0.43\text{V}} - \underbrace{n|V_{DSSAT5}|}_{0.397\text{V}} - \underbrace{n V_T f(i_{f1})}_{100\text{mV}}}$$

$$= \underline{0.746\text{V}}$$

$$b) \quad V_{ICM} = 0.2\text{V} \Rightarrow |V_{G1}| = 1.8\text{V} - 0.2\text{V} = 1.6\text{V}$$

$$\frac{|V_{G1}| - |V_{thp}|}{n V_T} - \frac{|V_{DSS}|}{V_T} = f(i_{f1})$$

$$|V_{DSS}| = \frac{|V_{G1}| - |V_{thp}|}{n} - V_T f(i_{f1})$$

$$= 0.786\text{V}$$

$$\boxed{V_{O_{MAX}} = \underbrace{V_{DD}}_{1.8\text{V}} - \underbrace{|V_{DSS}|}_{0.786\text{V}} - \underbrace{|V_{DSSAT2}|}_{0.197\text{V}} = 0.817\text{V}}$$

$$c) \text{SR} = 200 \frac{\text{V}}{\mu\text{s}} \Rightarrow I_{D5} = 0.5 \text{PF} \times 200 \frac{\text{V}}{\mu\text{s}} = 100 \mu\text{A} \quad (9)$$

$$w_5 = \frac{100 \mu\text{A} \times 2 \mu\text{m}}{I_{sep} \times 750} = 58 \mu\text{m}$$

$$w_1 = w_2 = \frac{50 \mu\text{A} \times 2 \mu\text{m}}{I_{sep} \times 20} = 217.4 \mu\text{m}$$

$$w_3 = w_4 = \frac{50 \mu\text{A} \times 2 \mu\text{m}}{I_{sep} \times 80} = 12.5 \mu\text{m}$$