

EELE 5131: SOLUTIONS TO ASSIGNMENT #1 ①  
(2019)

$$1) V_{G1} = \frac{R_1}{R_1 + R_2} V_{DD} = 2.02 \text{ V}$$

• ASSUME M1 IN ACTIVE REGION:

$$I_{D1} = \frac{180 \mu\text{A}}{2} \times 6 \times (2.02 \text{ V} - 0.6 \text{ V})^2$$
$$= 1.01 \text{ mA}$$

• M2 DIODE-CONNECTED  $\Rightarrow$  ACTIVE (FOR 'NORMAL'  $I_D$ )

$$I_{D2} = \frac{50 \mu\text{A}}{2} \times 18 \times (V_{SG2} - 0.6 \text{ V})^2 = 1.01 \text{ mA}$$

$$V_{SG2} = 2.1 \text{ V} \Rightarrow V_{DS1} = \underline{V_{DD} - V_{SG2} = 2.9 \text{ V}}$$

• SINCE  $V_{DS1} > V_{OV1} (= 1.37 \text{ V}) \Rightarrow$  ASSUMPTION OF M1 IN ACTIVE REGION VERIFIED.

$$M_1 \begin{cases} I_D = 1.01 \text{ mA} \\ V_{DS} = 2.9 \text{ V} \end{cases}$$

$$M_2 \begin{cases} I_D = 1.01 \text{ mA} \\ |V_{DS}| = V_{SG} = 2.1 \text{ V} \quad (V_{DS} = -2.1 \text{ V}) \end{cases}$$

②  
2) a)

i)  $V_{th} \leq v_I \leq V_{DD} \Rightarrow \text{CUTOFF} \Rightarrow v_o = 0$   
SINCE  $I_D = 0$

ii)  $V_1 < v_I < V_{DD} - V_{th} \Rightarrow \text{ACTIVE}$

$$v_o = \frac{k'}{2} \frac{W}{L} (V_{DD} - v_I - |V_{th}|)^2 R_D$$

iii)  $v_I < V_1 \Rightarrow \text{TRIODE}$

$$v_o = \frac{k'}{2} \frac{W}{L} \left[ 2 (V_{DD} - v_I - |V_{th}|) v_{SD} - v_{SD}^2 \right] R_D$$

$V_1$  : EDGE BETWEEN TRIODE AND ACTIVE

$$\underbrace{v_{SD}}_{V_{DD} - v_o} = \underbrace{(V_{DD} - v_I - |V_{th}|)}_{= V_{ov}} \quad \Big| \quad v_I = V_1$$

$$+ v_o = + v_I + |V_{th}|$$

$$\frac{k'}{2} \frac{W}{L} (V_{DD} - \underset{\uparrow}{v_I} - |V_{th}|)^2 R_D = \underset{\uparrow}{v_I} + |V_{th}|$$

LET  $V_1 + |V_{th}| = X$

$R_D \frac{k'_1}{2} \frac{W}{L} (V_{DD} - X)^2 = X$

$V_{DD}^2 - 2V_{DD}X + X^2 = \frac{1}{\frac{k'_1 W}{2L} R_D} X$

$X^2 + \underbrace{\frac{b}{2}}_{-C} X + V_{DD} = 0$

$a = 1$   
 $b = -6.16 \text{ V}$   
 $c = 9 \text{ V}^2$

$a=1$   
 $b = -2V_{DD} - \frac{1}{\frac{k'_1 W}{2L} R_D}$


$X_{1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = \frac{6.16 \text{ V} \pm (1.39 \text{ V})}{2}$

$\sqrt{b^2 - 4ac} = 1.39 \text{ V}$

$X_{1,2} = \begin{cases} 3.76 \text{ V} > V_{DD} + |V_{th}| \Rightarrow \text{M1 CUTOFF} \\ 2.39 \text{ V} \Rightarrow V_I = X - |V_{th}| = 1.79 \text{ V} \end{cases}$   
 (ROUNDED-OFF, ACTUAL VALUE CLOSEST TO 2.38 V) =  $V_1$


$V_O @ V_I = V_1 \approx 2.39 \text{ V}$

b)

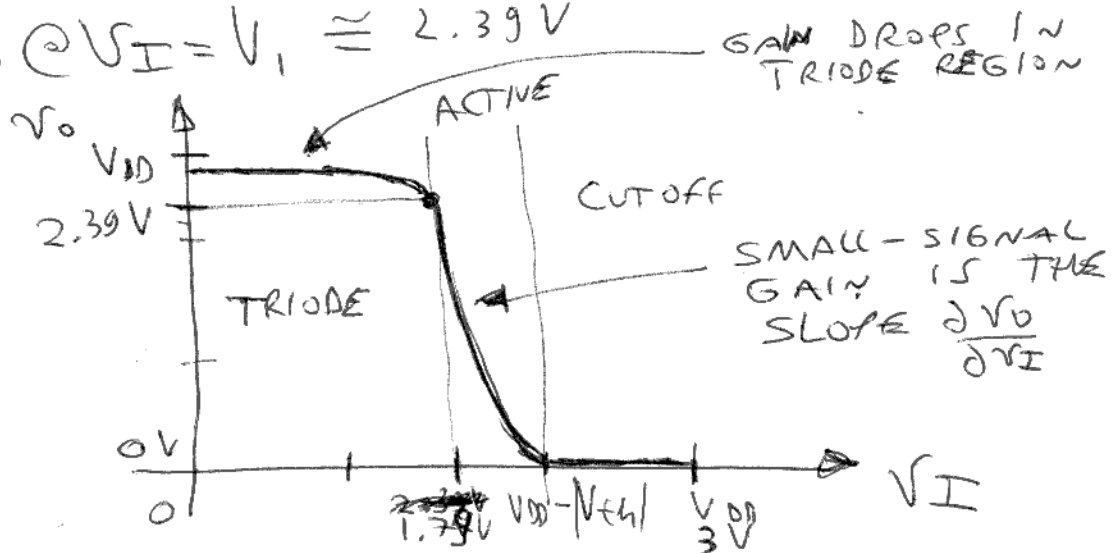


$$④ \quad \frac{\partial V_o}{\partial V_I} = \frac{k'}{2} \frac{W}{L} \times 2 (V_{DD} - V_I - |V_{th}|)^2 R_D \times (-1)$$

$$\left| \frac{\partial V_o}{\partial V_I} \right| = \frac{k'}{2} \frac{W}{L} R_D (V_{DD} - V_I - |V_{th}|)^2$$

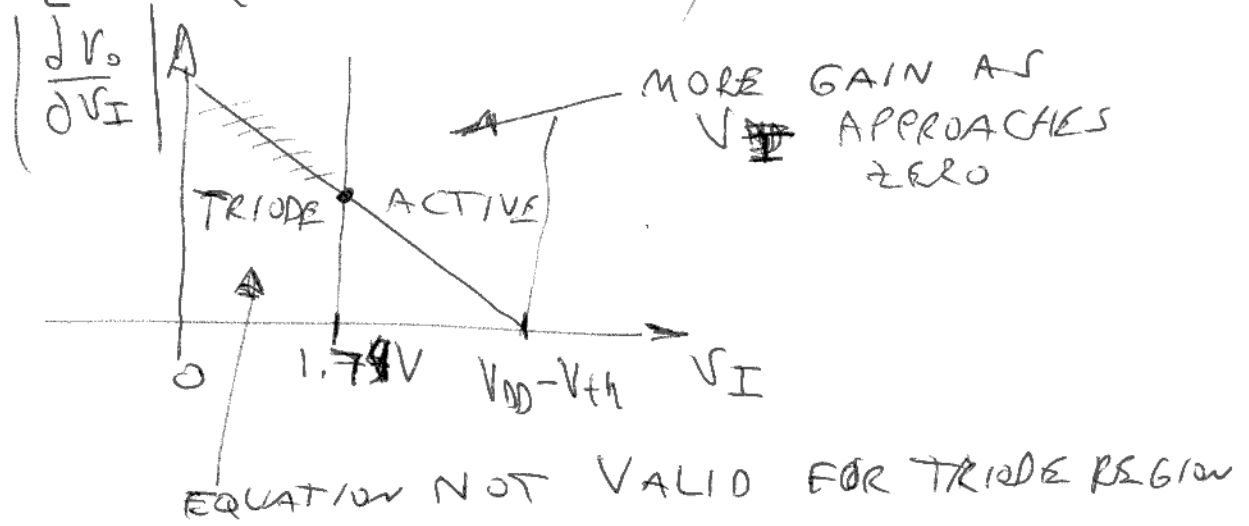

$$c) \quad \therefore a_{v_{max}} = -7.63 \quad | \quad @ V_I = 1.79V$$
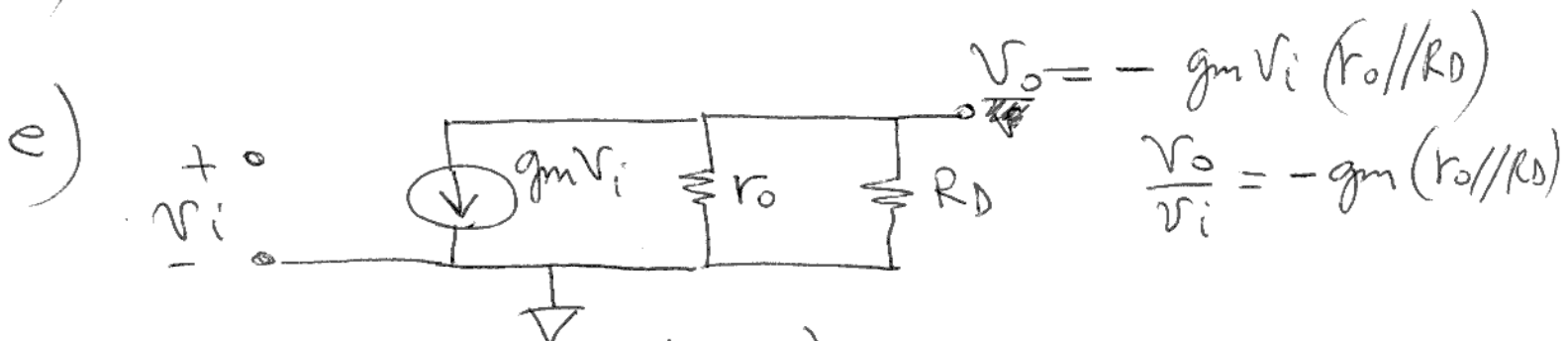
$$d) \quad \Delta V_o = a_v \Delta V_I = -7.63 \times (-5mV) = \underline{38.15mV}$$



$$g_m = k' \frac{W}{L} (V_{DD} - V_I - |V_{th}|) = 0.763 \text{ mS}$$

$$r_o = \frac{L}{I_D \left| \frac{\partial V_o}{\partial V_{DS}} \right|}, \quad I_D = \frac{k'}{2} \frac{W}{L} V_{ov}^2 = 0.233 \text{ mA}$$

$$r_o = 86 \text{ k}\Omega$$

$$r_o // R_D = 8.96 \text{ k}\Omega$$

$$\therefore a_v = \frac{V_o}{V_i} = -6.84$$