

# EELE 5131


## Practice Problems for Midterm — Winter 2019

Parameters for all problems:  $I_{SQn} = 280 \text{ nA}$ ,  $V_{thn} = 0.5 \text{ V}$ ,  $|\partial L/\partial V_{DS}|_n = 0.03 \text{ } \mu\text{m/V}$ ,  $I_{SQp} = 80 \text{ nA}$ ,  $V_{thp} = -0.55 \text{ V}$ ,  $|\partial L/\partial V_{DS}|_p = 0.04 \text{ } \mu\text{m/V}$ ,  $n_n = n_p = 1.3$ ,  $t_{OX} = 6 \text{ nm}$  and  $A_\beta = 3 \text{ } \mu\text{m}$ .

### Problems and Questions

 1. The following layout is for a transistor in a process with p-type substrate.


- What layer is missing to form an NMOS transistor?
- What layers are missing to form a PMOS transistor instead?



Answers: (a) n+, (b) p+ and N-well

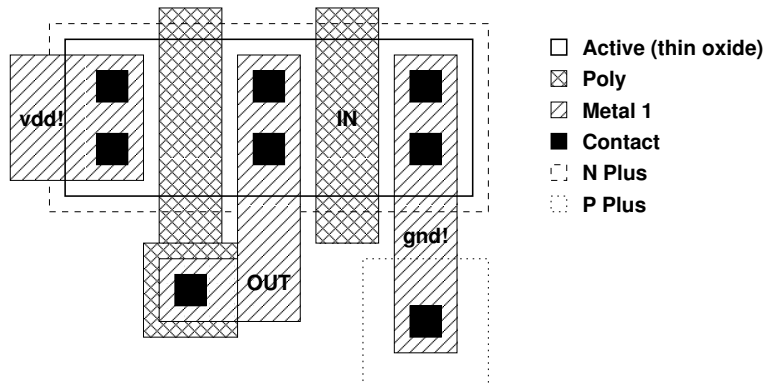
2. The following layout is for a process with p-type substrate.

- Draw an schematic diagram of the circuit in this layout. Use the provided node labels.
- Is there any missing layer(s) and if yes and where? (mark in the figure and explain).



Answer: (b) Active layer missing in substrate contact

 3. A 1:1 PMOS mirror is designed with 2 unit transistors with  $(W/L) = (10\mu\text{m}/1\mu\text{m})$ . The mirror is connected as shown below. The load resistor is  $R = 10\text{ k}\Omega$  and the supply voltage is 1.8 V.



- Draw a current mirror schematic. Include input current source, load resistor and bulk connections.
  - Calculate the source-drain voltage in each transistor for the following values of  $I_{BIAS}$ : 25 nA, 5  $\mu\text{A}$  and 40  $\mu\text{A}$ .
  - Estimate the maximum load voltage and the output resistance of the mirror for  $I_{BIAS} = 40\ \mu\text{A}$ .
  - Calculate the standard deviation (in %) in output current when  $I_{BIAS} = 5\ \mu\text{A}$  separately due to threshold voltage mismatch alone, specific current mismatch alone and the two combined.
4. Design a simple PMOS current mirror subject to the following specifications:
- Supply voltage is 3 V.
  - The operating output voltage range must be from zero up to 2.75 V.
  - The input and output currents are equal to 60  $\mu\text{A}$ .
  - The output current must change by 3 % or less with a decrease of 1 V in the output voltage ( $V_{out}$ ).
  - Minimize gate area as much as possible.

Show the schematic with transistor dimensions for full marks.

5. Re-design the previous current source for an input current of 240  $\mu\text{A}$  and an output current of 30  $\mu\text{A}$ . Use unit transistors for good matching.


**Answer:** use the same design as in (3), with 4 units in parallel for input branch and two in series for output branch.

- Calculate the resistor needed to generate the input current in Problem 5.
- Neglecting channel-length modulation, estimate the difference between the input and output currents in your design in Problem 4 when  $V_{th}$  mismatch between transistors is 15 mV.

8. Design a simple NMOS current mirror subject to the following specifications:
- (a) Supply voltage is 3.3 V.
  - (b) The mirror must operate correctly with an output voltage of at least 0.25 V.
  - (c) The input current is  $60 \mu\text{A}$  and output current is  $90 \mu\text{A}$ .
  - (d) The output current must change by 2 % or less with an increase of 1 V in the output voltage ( $V_{out}$ ).
  - (e) Minimize gate area as much as possible. Assume that due to matching requirements, minimum gate dimension is  $1 \mu\text{m}$ .

Show schematic and unit transistor dimensions for full marks.

 9. Neglecting channel-length modulation, estimate the difference between the input and output currents in your design of the previous problem when  $V_{th}$  mismatch between transistors is 5 mV.
10. In the figure,  $I_{in} = 20 \mu\text{A}$ ,  $V_{DD} = 2.5 \text{ V}$  and  $(W/L)_1 = (W/L)_2 = (2\mu\text{m}/2\mu\text{m})$ .
- (a) Calculate  $I_{out}$  considering the effect of channel-length modulation, assuming perfect matching. Show calculation steps.
  - (b) Neglecting channel-length modulation, estimate the standard deviation in output current due to transistor mismatch.



11. In the figure,  $I_{in} = 0.5 \mu\text{A}$ ,  $V_{DD} = 3 \text{ V}$  and all transistors are equal with  $(W/L) = 20$ . Justify your answers.
- (a) Specify regions of operation for each of M1, M2 and M3: inversion level (weak, moderate or strong) and triode or active.
  - (b) Neglecting channel-length modulation calculate  $i_{f2}$  and  $i_{r2}$ .

