
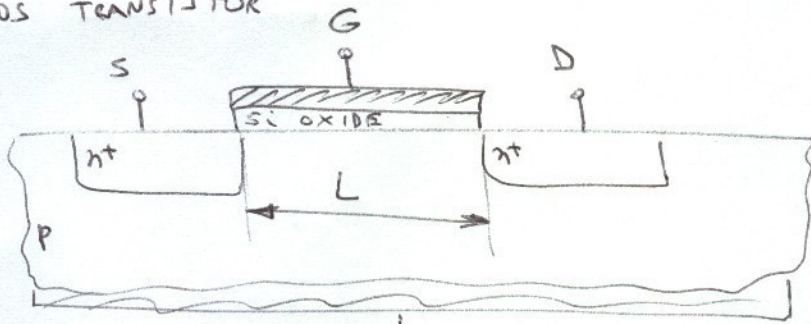


ENGI 5131: BASIC MOSFET MODEL

NMOS TRANSISTOR

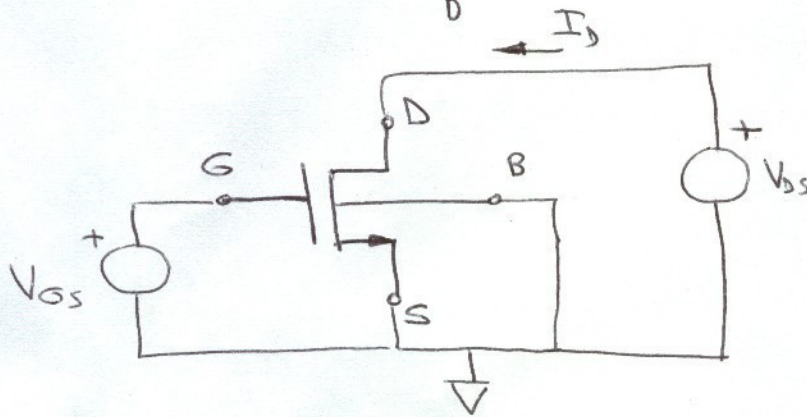

N-CHANNEL TRANSISTOR



V_t : THRESHOLD VOLTAGE

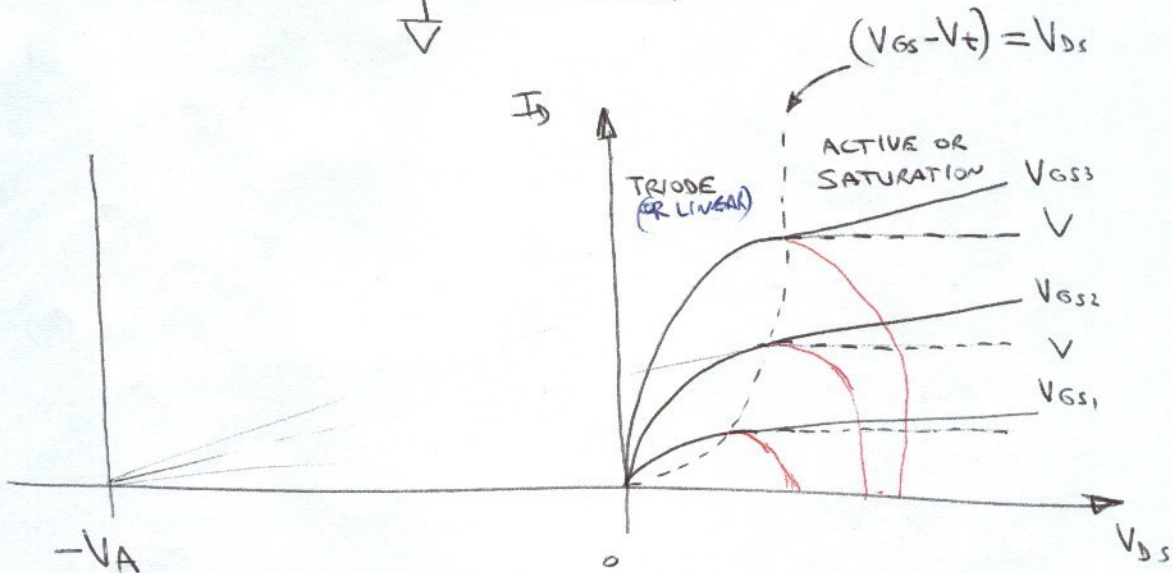


FIG. (1)

• TRIODE REGION

$$I_D = K [2(V_{GS} - V_t) V_{DS} - V_{DS}^2] , \quad (V_{GS} - V_t) \geq V_{DS}$$

• SATURATION REGION

$$I_D \approx K (V_{GS} - V_t)^2$$

↑
NEGLECTING OUTPUT RESISTANCE

↑
SAME AS THIS WITH $V_{DS} = V_{GS} - V_t$

$$I_D = K (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

λ : CHANNEL-LENGTH MODULATION FACTOR ($\frac{1}{V}$)

$\lambda = \frac{1}{V_A}$, V_A : EARLY VOLTAGE. \rightarrow LATER WE WILL SEE HOW TO CALCULATE THIS.

(CUTOFF: $V_{GS} < V_t$)

OVERDRIVE VOLTAGE: $V_{OV} := V_{GS} - V_t$ \rightarrow BODY EFFECT CONSIDERED LATER.

$$K = \frac{\mu_n C_{ox}}{2} \frac{W}{L}, \quad C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$

$k' := \mu_n C_{ox} \rightarrow$ CONSTANT FOR A GIVEN FAB. PROCESS.

$$\epsilon_{ox} \approx 3.45 \times 10^{-11} \frac{F}{m}$$

EXAMPLE

$t_{ox} = 100 \text{ \AA}$ ($1 \text{ \AA} = 10^{-10} \text{ m}$), $\mu_n = 450 \frac{cm^2}{Vs} = 0.045 \frac{m^2}{Vs}$
 $\rightarrow C_{ox} = 3.45 \frac{fF}{(\mu m)^2}$ ($1 \text{ fF} = 10^{-15} \text{ F}$)

$$k' = 155 \frac{\mu A}{V^2}$$


$$V_t = 0.6 \text{ V}$$

NOTE $(V_{GS} - V_t) = V_{DS}$ IN FIG.1 IS A PARABOLA:

$$V_{GS} - V_t = V_{OV} = V_{DS} \Rightarrow I_D = \frac{k'}{2} \frac{W}{L} V_{OV}^2 = \frac{k'}{2} \frac{W}{L} V_{DS}^2$$

OBSERVATION: ACTIVE REGION IS WHEN $V_{DS} \geq V_{OV}$

$V_{DS} = \text{CONSTANT.}$

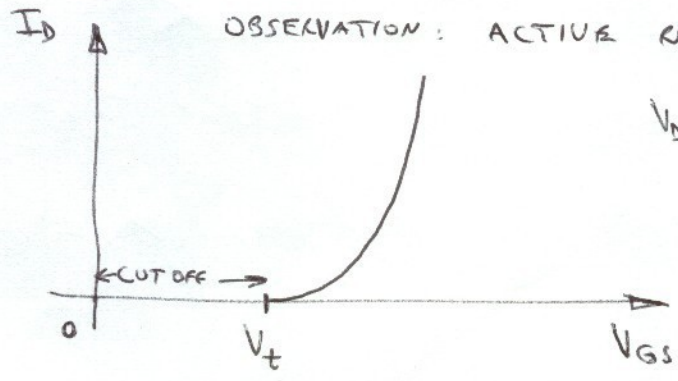

MORE ON OUTPUT RESISTANCE


(21)

- THE EFFECTIVE CHANNEL LENGTH DEPENDS ON V_{DS} : AS V_{DS} INCREASES, THE DEPLETION REGION AT THE DRAIN INCREASES. \therefore EFFECTIVE LENGTH (L_{eff}) DECREASES.

X_d : LENGTH OF DEPLETION REGION

$$V_A \approx L \left(\frac{\partial X_d}{\partial V_{DS}} \right)^{-1} \quad \therefore V_A \propto L$$

SMALL-SIGNAL MODEL FOR $V_{SB} = 0$

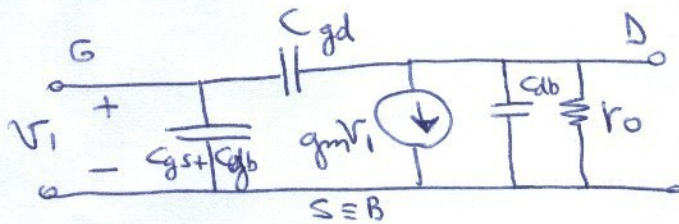

ACTIVE REGION:

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \mu C_{ox} \frac{W}{L} (V_{OV}) = \sqrt{2 I_D \mu C_{ox} \frac{W}{L}}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{L}{I_D \left(\frac{\partial X_d}{\partial V_{DS}} \right)} \quad \left(= \left(\frac{\partial I_D}{\partial V_{DS}} \right)^{-1} \right)$$

$$C_{gs} \approx \frac{2}{3} W L C_{ox} + \underbrace{C_{ov}}_{\text{OVERLAP CAPACITANCE}}$$


$$C_{gd} = C_{ov}$$

C_{db} : DRAIN DEPLETION CAPACITANCE JUNCTION


C_{gb} : POLY-BULK CAPACITANCE OUTSIDE OF CHANNEL AREA

SIMPLE CURRENT MIRROR

IDEALLY:

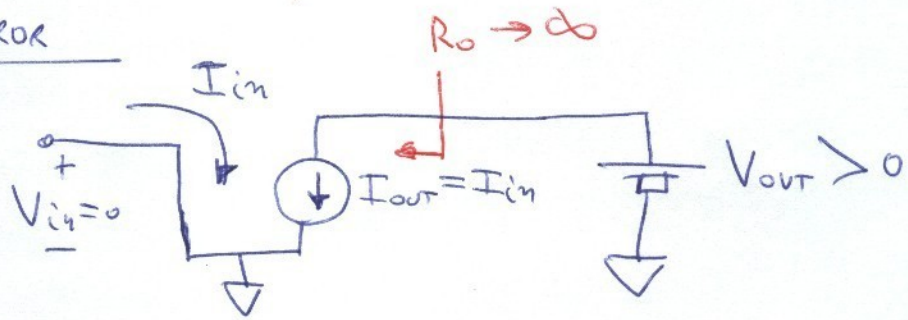

SIMPLE MOS MIRROR

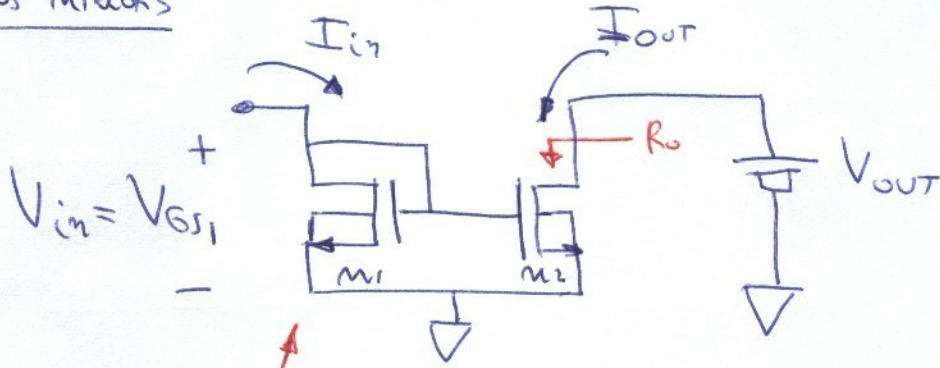


EXPLAIN BIPOLAR-CONNECTED → EXERCISE PAGE 6

- ASSUME $M_1 = M_2$ AND V_A VERY LARGE ($\lambda \approx 0$) THEN $I_{OUT} \approx I_{IN}$ IF $V_{OUT} \geq V_{OV2}$ (SINCE $V_{GS1} = V_{GS2}$)

$$I_{in} = \frac{k'}{2} \frac{W}{L} V_{OV}^2 \Rightarrow V_{OV} = \sqrt{\frac{2 I_{in}}{k' \left(\frac{W}{L}\right)}} (\leq V_{OUT})$$

- CONSIDER NOW V_A

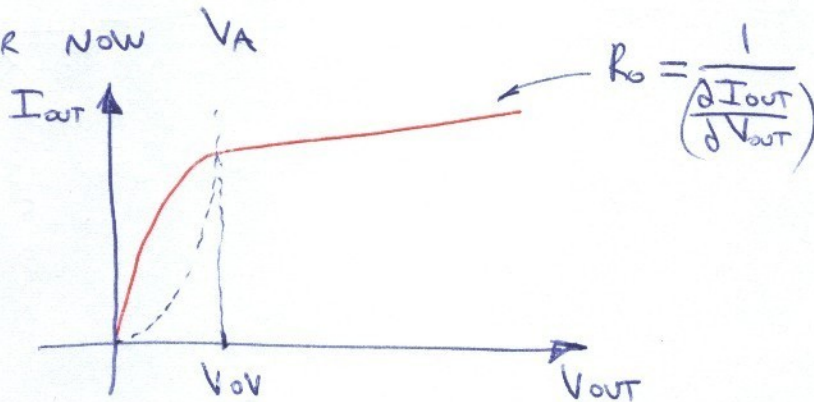

$$I_{OUT} = \frac{k'}{2} \frac{W}{L} V_{OV}^2 \left(1 + \frac{V_{OUT}}{V_A}\right)$$

$$\frac{dI_{OUT}}{dV_{OUT}} = \frac{k'}{2} \frac{W}{L} V_{OV}^2 \frac{1}{V_A} \approx \frac{I_{OUT}}{V_A} \Rightarrow R_o = \frac{V_A}{I_{OUT}} = r_{o2}$$

$$R_o = r_{o2} = \frac{L}{\left(\frac{\partial X_d}{\partial V_{DS}}\right) I_{OUT}}$$

SUMMARY:

1. V_{in} NOT ZERO \rightarrow $\left[\sqrt{\frac{2 I_{in}}{k' \frac{W}{L}}} + V_t \right]$ V_{OV}

• CAN REDUCE BY INCREASING $\frac{W}{L}$ BUT $V_{OV} > 100mV$ TO KEEP EQUATIONS VALID (STRONG INVERSION)

2. $I_{OUT} \neq I_{in}$ DUE TO R_o NOT ∞ .

• DIFFERENCE IS $\Delta I = \frac{(V_{OUT} - V_{in})}{R_o}$

$$= \frac{(V_{OUT} - V_{OV} - V_t)}{L} \times \left| \frac{\partial X_d}{\partial V_{DS}} \right| \times I_{OUT}$$

• CAN BE REDUCED BY INCREASING L


3. $I_{OUT} \neq I_{in}$ DUE TO MISMATCH IN M_1, M_2

4. MINIMUM V_{OUT} NOT ZERO $\rightarrow V_{OV}$ (SAME CONSIDERATIONS AS V_{in})

(JUMP TO PAGE 29) \rightarrow EXAMPLE P. 4.3

• SMALL-SIGNAL \rightarrow JUMP TO PROBLEM 3.4 PAGE 15

PMOS TRANSISTOR

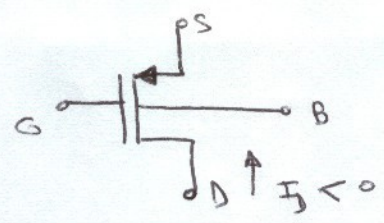

$$V_t < 0$$

SAME EQUATIONS THAN FOR NMOS WORK IF SIGNS OF VOLTAGES AND CURRENTS ARE INVERTED.

$$I_D = - \frac{k'}{2} \frac{W}{L} (V_{GS} - V_t)^2$$

$$V_{DS} < 0$$


$$V_{GS} < 0$$

$$k'_p < k'_n$$

IN GENERAL FOR A GIVEN TECHNOLOGY. THIS IS BECAUSE MOST PROCESSES ARE OPTIMIZED FOR NMOS TRANSISTORS

↓
DUE TO $\mu_p < \mu_n$ (EVERYTHING ELSE IS THE SAME)

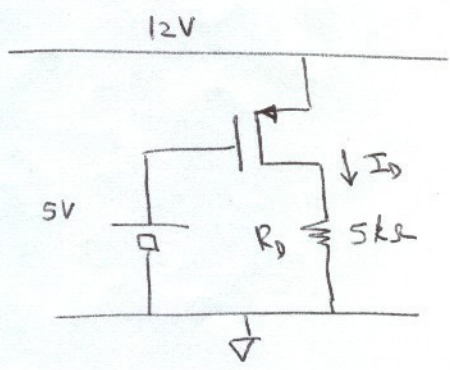EXAMPLES: 7.6, 7.7 AND EXERCISE (PAGES 4, 5, 6 2007) → SHOW THESE FIRST



$$V_{t0} = -1V$$

$$k' = \frac{15 \mu A}{V^2}$$

$$\frac{W}{L} = 5$$

$$V_{SG} = 12V - 5V = 7V \Rightarrow V_{OV} = -6V$$

ASSUME ACTIVE REGION: $I_D = \frac{k'}{2} \frac{W}{L} (-7V + 1V)^2 = 1.35 \text{ mA}$

$$V_{R_D} = 1.35 \text{ mA} \times 5k\Omega = 6.75V \Rightarrow V_{SD} = 12V - 6.75V = 5.25V < |V_{OV}|$$

∴ TRANSISTOR NOT IN ACTIVE REGION → TRIODE.

$$\begin{cases} I_D = \frac{k'}{2} \frac{W}{L} [2 |V_{OV}| V_{SD} - V_{SD}^2] \\ V_{SD} = 12V - I_D R_D \end{cases} \rightarrow \text{SOLVE 2 EQ. 2 UNKNOWNNS.}$$

$$C_{gs} = \frac{2 C_{ox} W L}{3}$$


$$r_o = \frac{V_A}{I_D} = \frac{1}{\lambda I_D}$$

$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}} = \mu \left(\frac{k'(W/L) I_D}{2(2\phi_f + V_{SB})} \right) \quad \begin{matrix} \text{(SECOND-ORDER EFFECT)} \\ \text{(BODY EFFECT)} \end{matrix}$$

$$\frac{g_{mb}}{g_m} = \chi = \frac{\mu}{2 \sqrt{2\phi_f + V_{SB}}}, \quad 0.1 \leq \chi \leq 0.3$$

(PROBLEM 1.15 FOR PRACTICE)

EXAMPLE 7.6 (SPENCER & GAUSI)

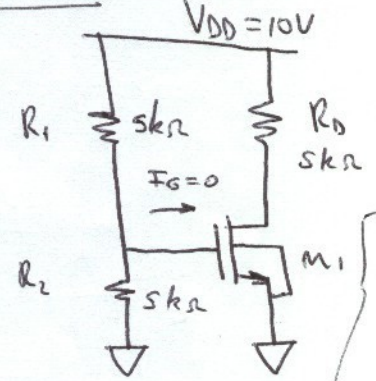

FIND I_D

$$\left. \begin{matrix} k' = 2 \times 10^{-5} \frac{A}{V^2} = 20 \frac{\mu A}{V^2} \\ \frac{W}{L} = 5 \\ V_{t0} = 1V \end{matrix} \right\}$$



$\Rightarrow V_{OV} = 4V$
NOTE V_{GS} MAY BE QUITE LARGE.

$$V_G = V_{DD} \frac{R_2}{R_1 + R_2} = 5V = V_{GS}$$

$$I_D = \frac{k'}{2} \frac{W}{L} (V_{GS} - V_t)^2 \quad \text{IF } \overbrace{V_{GS} - V_t}^{V_{OV}} \ll V_{DS}$$


TRY SINCE V_{DS} IS UNKNOWN ANYWAY
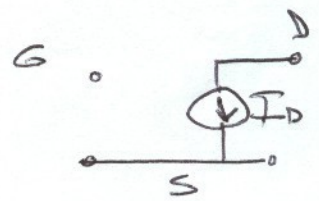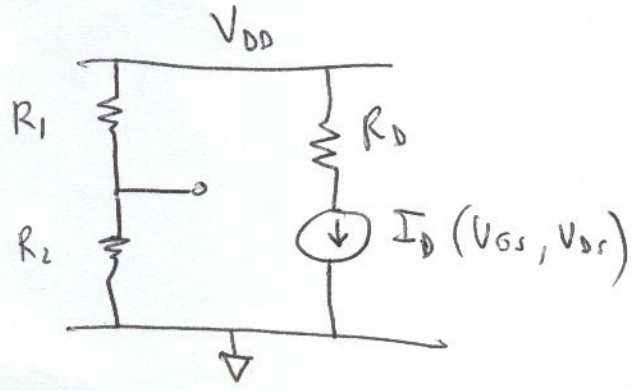
$$I_D = 800 \mu A \Rightarrow V_{DS} = 10V - 800 \mu A \times 5k\Omega = 6V > V_{OV} \quad (\text{OK})$$




EQUIVALENT CIRCUIT (LARGE SIGNAL, L.F.)

EXAMPLE 7.7 (S&G.)

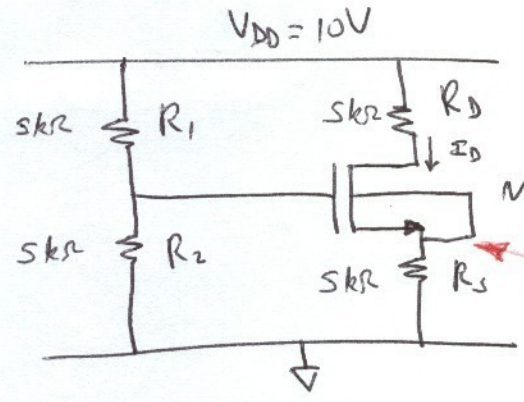

$$\begin{cases} k' = 20 \mu\text{A}/\text{V}^2 \\ \frac{W}{L} = 5 \\ V_{t0} = 1\text{V} \end{cases}$$

NOTE THIS IS NOT COMMON IN I.C.S

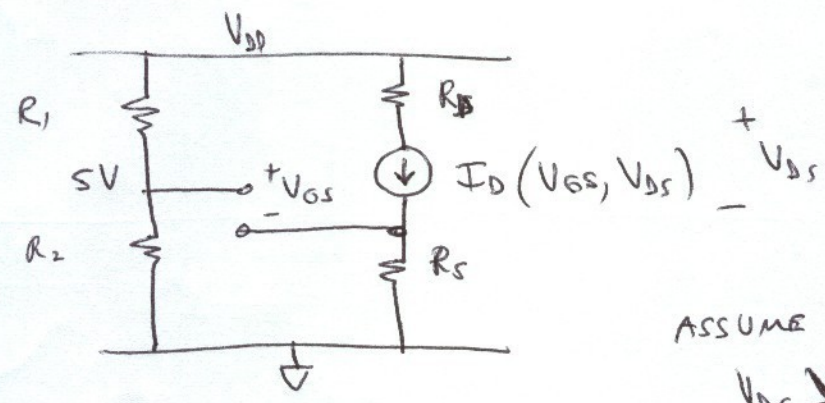

ASSUME FOR NOW

$$V_{DS} \rightarrow V_{OV}$$

$$V_{GS} = \underbrace{5\text{V} - I_D R_S}_{=V_{GS}} - V_t$$

$$I_D = \frac{k'}{2} \frac{W}{L} (V_{OV})^2$$

$$I_D = \frac{k'}{2} \frac{W}{L} (V_G - I_D R_S - V_t)^2$$

$$\frac{2L}{k'W} I_D = (V_G - V_t)^2 - 2(V_G - V_t) I_D R_S + I_D^2 R_S^2$$

$$R_S^2 I_D^2 - \left[\frac{2L}{k'W} + 2(V_G - V_t) R_S \right] I_D + (V_G - V_t)^2 = 0$$


$$25\text{m}\Omega^2 I_D^2 - 60\text{k} \frac{\text{V}^2}{\text{A}} I_D + 16\text{V}^2 = 0$$

$$I_{D1,2} = \frac{60\text{k} \pm \sqrt{3.6 \times 10^9 - 1.6 \times 10^9}}{50\text{m}} = \begin{cases} 2.09\text{mA} \\ 306\mu\text{A} \end{cases}$$

$$V_{R_D} = 5\text{k}\Omega I_D = 10.45\text{V} @ I_D = 2.09\text{mA} \text{ (NOT POSSIBLE)}$$

$$\therefore I_D = 306\mu\text{A} \Rightarrow V_{DS} = 10\text{V} - 306\mu\text{A} \times 10\text{k}\Omega = 6.94\text{V} \rightarrow \text{ACTIVE REGION}$$
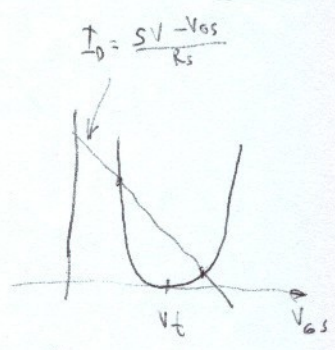
$$V_{GS} = 3.47\text{V} \Rightarrow V_{OV} = 2.47\text{V}$$




• QUESTION: WHAT IS THE MAXIMUM R_D TO KEEP M1 IN ACTIVE REGION?

$$V_{DS} = V_{ov} = 2.47V \Rightarrow 2.47V = 10V - 306\mu A (R_D + 5k\Omega)$$

$$\boxed{R_D = 19.6 k\Omega}$$

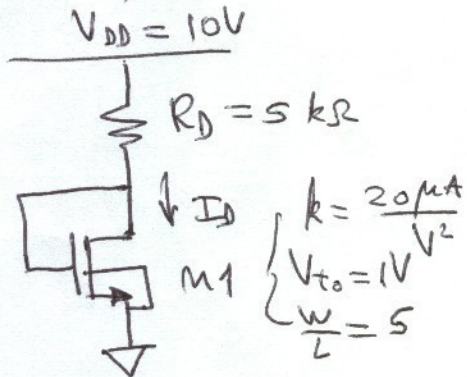• EXERCISE:

CALCULATE I_D, V_{DS} AND STATE REGION OF OPERATION



SOLUTION: $V_{GS} = V_{DS} \Rightarrow V_{DS} > V_{GS} - V_t = V_{ov} \rightarrow$ ACTIVE REGION (ALWAYS)


$$I_D = \frac{k'W}{2L} \left(\underbrace{V_{DD} - I_D R_D - V_t}_{= V_{GS}} \right)^2$$

$$R_D^2 I_D^2 - \left[\frac{2L}{k'W} + 2(V_{DD} - V_t)R_D \right] I_D + (V_{DD} - V_t)^2 = 0$$






$$25m I_D^2 - 110k I_D + 81V^2 = 0$$

$3.46 mA \times$ NOT POSSIBLE


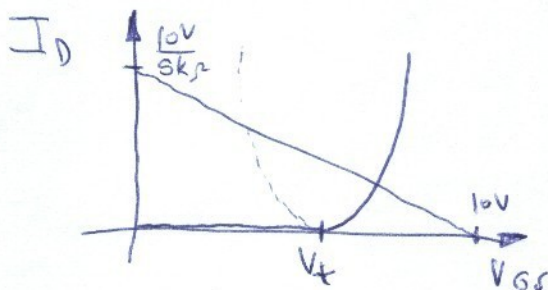
$$I_{D1-2} = \boxed{935 \mu A} \rightarrow V_{DS} = V_{GS} = \boxed{5.32 V}$$



REVIEW OF SMALL-SIGNAL ANALYSIS

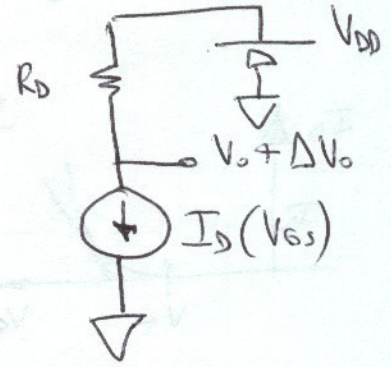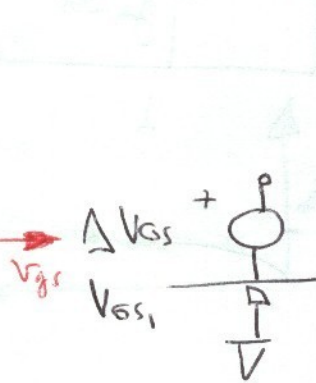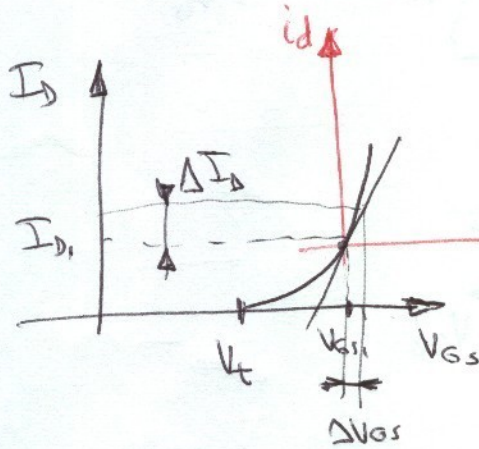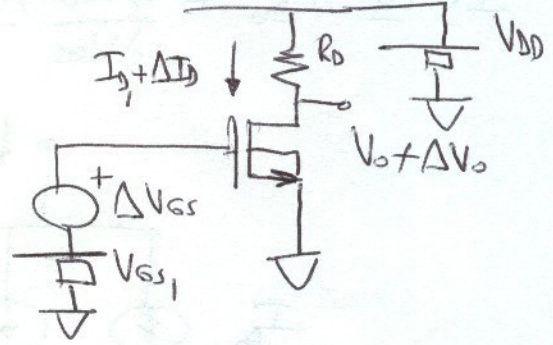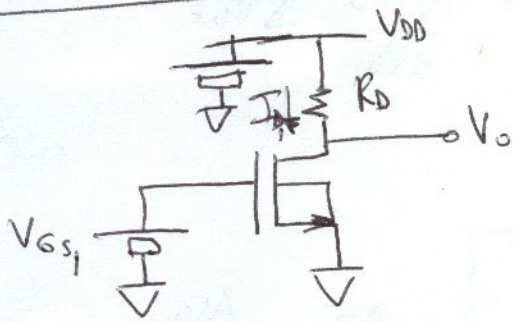


$$I_D \approx I_{D1} + \underbrace{\frac{\partial I_D}{\partial V_{GS}} \bigg|_{V_{GS1}}}_{g_m} \cdot \Delta V_{GS} \Rightarrow \Delta I_D$$

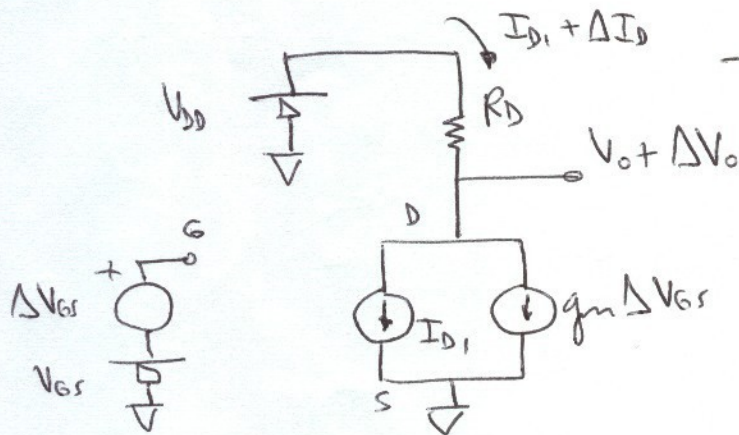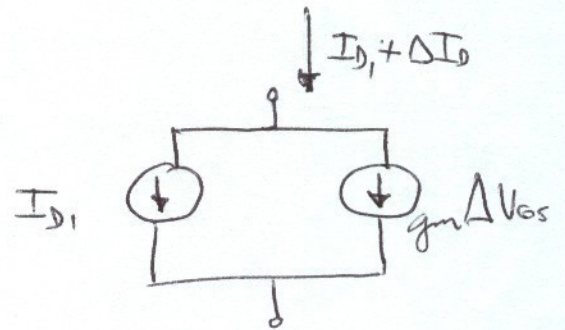

→ APPLY SUPERPOSITION

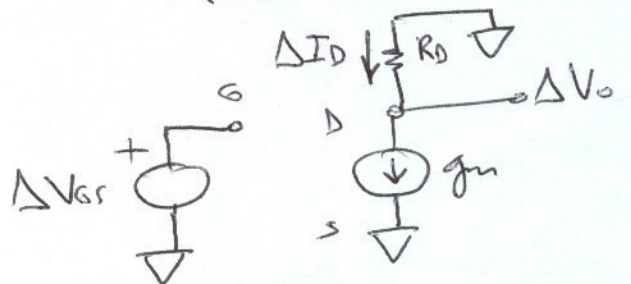- $\Delta V_{GS} = 0 \Rightarrow$ DC CIRCUIT. BIAS POINT
- EVERYTHING EXCEPT ΔV_{GS} EQUAL TO ZERO!




SMALL-SIGNAL CIRCUIT.

STEPS FOR SMALL-SIGNAL CIRCUIT GENERATION

$\Delta V_{GS}, \Delta I_D, \Delta V_O \rightarrow v_{gs}, i_d, v_o$ ← lowercase for small-signal quantities.

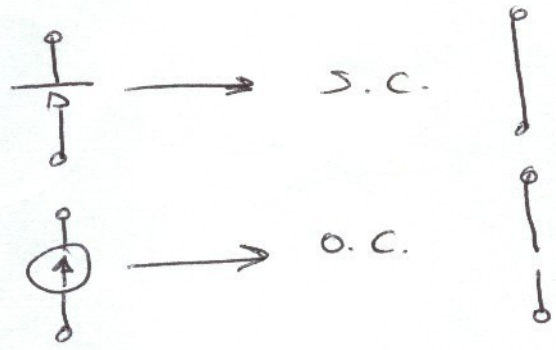
- REPLACE NONLINEAR DEVICES WITH LINEARIZED MODELS
- PASSIVATE INDEPENDENT DC SOURCES:



• CURRENTS AND VOLTAGES IN SMALL-SIGNAL CIRCUIT ARE DEVIATIONS FROM DC BIAS POINT. PRESENT λ, V_A TOO

(PRESENT MOSFET MODEL) AFTER THIS EXAMPLE

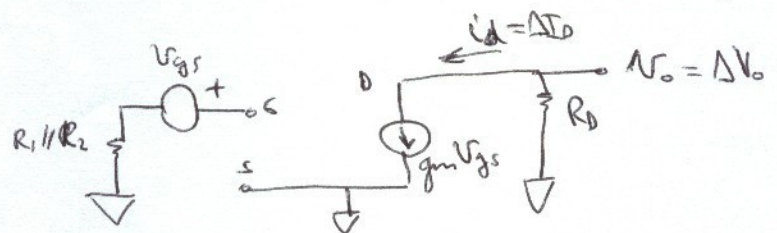EXAMPLE: CIRCUIT OF EXAMPLE 7.6 WITH $\Delta V_{GS} = v_{gs} = 100\text{mV}$



$$g_m = \left. \frac{dI_D}{dV_{GS}} \right|_{V_{GS} = 5V} = k' \frac{W}{L} (V_{GS} - V_t) = 0.4 \text{ ms}$$

$$i_d = 0.4 \text{ ms} \times 100 \text{ mV} = 40 \mu\text{A}$$

$$v_o = 40 \mu\text{A} \times 5 \text{ k}\Omega = 0.2 \text{ V}$$

TOTAL CURRENT $\approx 800 \mu\text{A} + 40 \mu\text{A} \approx 840 \mu\text{A}$

EXACT CURRENT = $\frac{k'}{2} \frac{W}{L} (5.1V - 1V)^2 = 840.5 \mu\text{A}$

} quite close