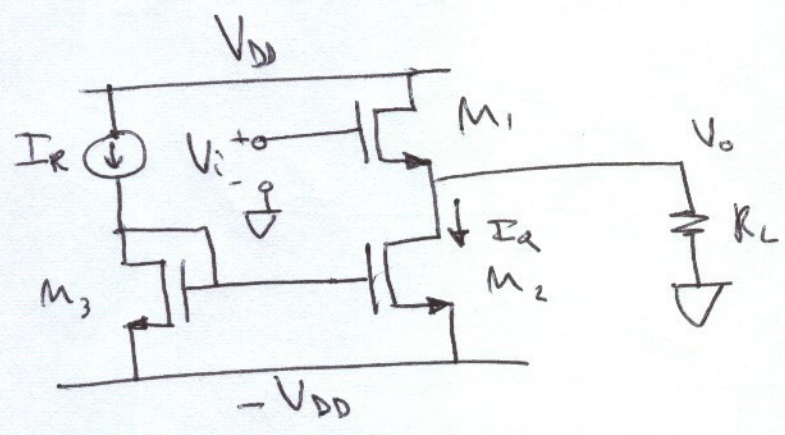


• COMPENSATION CAPACITOR NOT NECESSARY \rightarrow CL ACTS AS COMP. CAP. (43)

OUTPUT STAGES (CH 5)


SOURCE FOLLOWER




$$V_i = V_o + V_{t1} + V_{ov1}$$

$$V_i = V_o + V_{t0} + \gamma \left(\sqrt{2\phi_f + V_o + V_{DD}} - \sqrt{2\phi_f} \right) + \sqrt{\frac{2(I_D + \frac{V_o}{R_L})}{k' (\frac{W}{L})_1}}$$
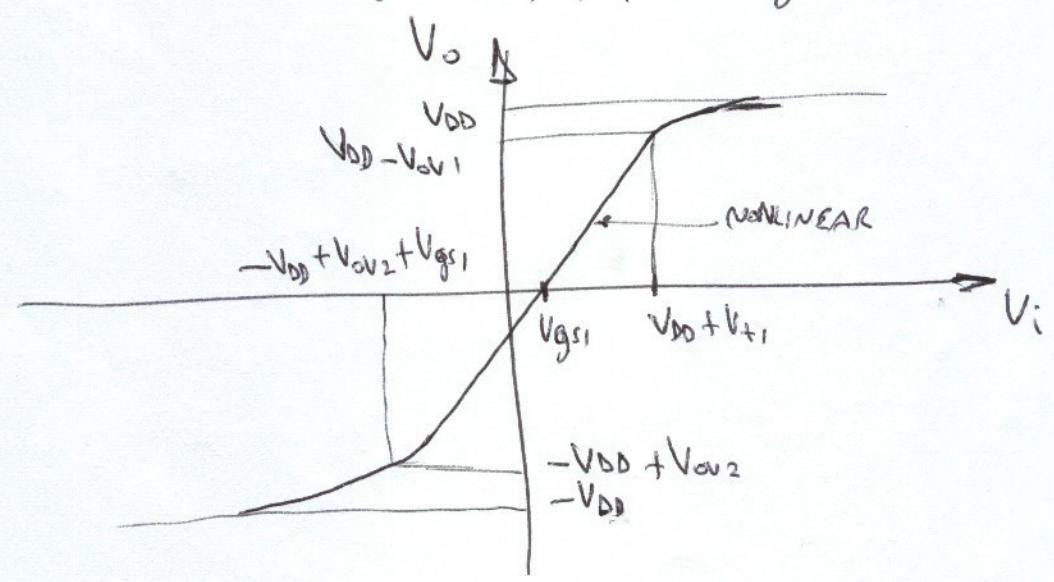
$$R_L \rightarrow \infty \Rightarrow \frac{v_o}{v_i} = \frac{1}{1 + \gamma} = \frac{g_m}{g_m + g_{mb}}$$



CLASS AB OUTPUT STAGE

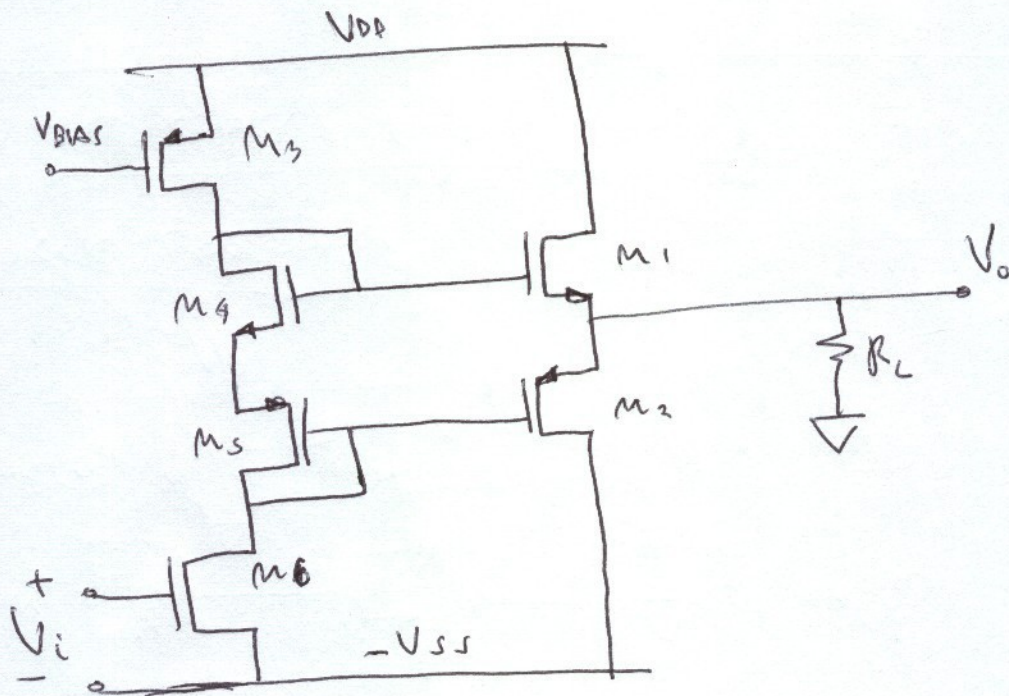

$$IF \left\{ \begin{array}{l} V_{OV4} = V_{OV1} \\ V_{OV5} = V_{OV2} \end{array} \right. \Rightarrow (*)$$


$$\sqrt{\frac{2 I_{D4}}{k_p' \left(\frac{W}{L}\right)_5}} + \sqrt{\frac{2 I_{D4}}{k_n' \left(\frac{W}{L}\right)_4}} = \sqrt{\frac{2 I_{D1}}{k_n' \left(\frac{W}{L}\right)_1}} + \sqrt{\frac{2 I_{D2}}{k_p' \left(\frac{W}{L}\right)_2}}$$

$$(*) \quad I_{D1} = I_{D4} \frac{\left(\frac{1}{k_n' \left(\frac{W}{L}\right)_4} + \frac{1}{k_p' \left(\frac{W}{L}\right)_5}\right)}{\left(\frac{1}{k_n' \left(\frac{W}{L}\right)_1} + \frac{1}{k_p' \left(\frac{W}{L}\right)_2}\right)}$$

$$\left\{ \begin{array}{l} V_{Omax} = V_{DD} - |V_{DS3}|_{min} - V_{GS1} = V_{DD} - |V_{OV3}| - V_{GS1} \\ V_{Omin} = -V_{SS} + V_{OV6} + V_{SG2} \end{array} \right.$$

• (DISCUSS EXAMPLE PAGE 384)

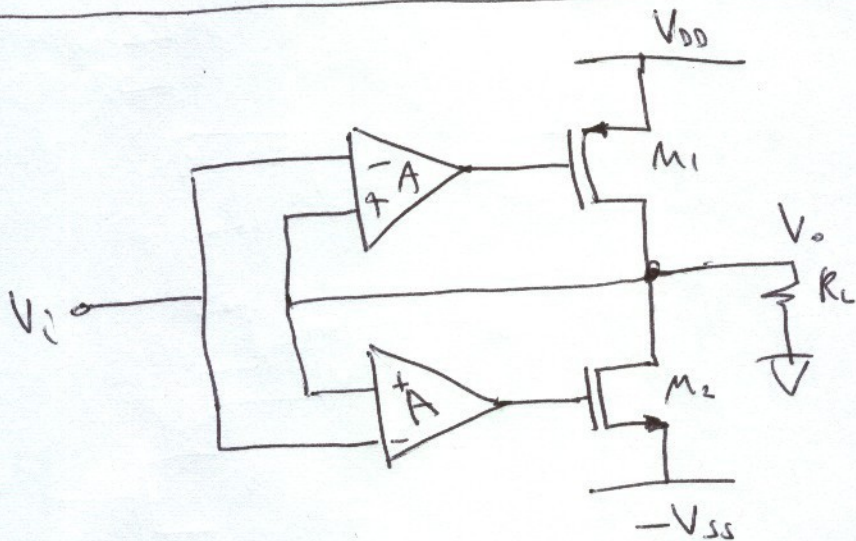COMMON SOURCE CONFIGURATION WITH ERROR AMPLIFIERS



• GOOD SWING BUT BAD FREQUENCY RESPONSE.

PROBLEM S.22 : SWING $\pm 1V$, $R_L = 1k\Omega$, $V_{DD} = V_{SS} = 2.5V$

$I_{BIAS} = 10\mu A$, $I_{D1Q} = 100\mu A$

$(\frac{W}{L})_3 = \frac{50}{1}$, $(\frac{W}{L})_6 = \frac{25}{1}$

$(\frac{W}{L})_{1-6}$? (MINIMIZE AREA)

TABLE 2.3 BUT $L_{eff} = L_{dwn}$, $L = 1\mu m$.

(THERE IS BODY EFFECT).

$\mu_n^1 = \frac{\mu_n E_{ox}}{t_{ox}} = \frac{550 \times 10^{-4} \times 3.45 \times 10^{-11}}{150 \times 10^{-10}} = 126.5 \frac{\mu A}{V^2}$

$\mu_p^1 = \frac{\mu_p E_{ox}}{t_{ox}} = \frac{250 \times 10^{-4} \times 3.45 \times 10^{-11}}{150 \times 10^{-10}} = 57.5 \frac{\mu A}{V^2}$

$V_{tn} = 0.7V$

$V_{tp} = -0.7V$

$V_{ov1} = V_{ov4} \Rightarrow$ SAME CURRENT DENSITY

$I_{D1} = \frac{k'_n(W/L)_1 V_{ov1}^2}{2} \Rightarrow V_{ov1}^2 = \frac{2 I_{D1}}{k'_n(W/L)_1} = \frac{2 I_{D4}}{k'_n(W/L)_4}$

$(I_{D1} = 10 I_{D4})$

$\frac{I_{D1}}{I_{D4}} = \frac{(W/L)_1}{(W/L)_4} = \frac{W_1}{W_4}$

$\therefore \begin{cases} W_4 = \frac{W_1}{10} \\ W_5 = \frac{W_2}{10} \end{cases}$

ALSO!

$$I_{D1} = I_{D4} \frac{\left(\frac{1}{k'_n(W/L)_4} + \frac{1}{k'_p(W/L)_5} \right)}{\left(\frac{1}{k'_n(W/L)_1} + \frac{1}{k'_p(W/L)_2} \right)} = I_{D4} \frac{\left(\frac{1}{k'_n W_4} + \frac{1}{k'_p W_5} \right)}{\left(\frac{1}{k'_n W_4} + \frac{1}{k'_p 10 W_5} \right)} = 10 I_{D4} \text{ (NOTHING NEW)}$$

$V_{OMAX} = V_{DD} - |V_{ov3}| - V_{GS1} = 2.5V - V_{GS1} - 83mV$

$|V_{ov3}| = \sqrt{\frac{2 \times 10\mu A}{k'_n \times 50}} = \underline{83mV}$ ~~DEEP SUBTHRESHOLD?~~
(ASSUME LINEAR)

$V_{OMIN} = -V_{S3} + V_{ov6} + V_{GS2}$

$V_{ov6} = \sqrt{\frac{2 \times 10\mu A}{k'_n \times 25}} = \underline{80mV}$

AVAILABLE SWING = $V_{OMAX} - V_{OMIN} = 5V - 2 \times 80mV = 4.84V$

~~2.5V~~ $V_{GS1} + 83mV = 2.5V - 1V \Rightarrow V_{GS1} \leq 1.42V$
 $|V_{GS2}| \leq 1.42V$

$f_n = \frac{1}{C_{ox}} \cdot \sqrt{2g \in MA} = \frac{150 \times 10^{-10}}{3.45 \times 10^{11}} \sqrt{2 \times 1.6 \times 10^{-19} \times 3.45 \times 10^{11} \times 4 \times 10 \times 10^6} = 0.09$

$\phi_p = 0.250 \quad \phi_{FV} = 0.3$

$$V_{tn} \Big|_{V_0 = 1V} = V_{tn} \Big|_{V_{SB} = 3.5V} = 0.7V + \gamma_n \left(\sqrt{2\phi_f + 3.5V} - \sqrt{2\phi_f} \right)$$

$$= 0.81V$$

$$V_{tp} \Big|_{V_0 = -1V} = -0.7 - \gamma_p \left(\sqrt{2\phi_f + 3.5V} - \sqrt{2\phi_f} \right)$$

$$= 1.01V$$

$$\left. \begin{aligned} V_{OV1} &= 1.42V - 0.81V = 0.61V \\ (V_{OV2}) &= 1.42V - 1.01V = 0.41V \end{aligned} \right\} \begin{array}{l} \text{WITH MAX} \\ \text{CURRENT} \\ I = \frac{1V}{1k\Omega} = 1mA \end{array}$$


$$1mA = \frac{k'_n}{2} \left(\frac{W}{L} \right)_1 (0.6V)^2 \Rightarrow \left(\frac{W}{L} \right)_1 = 43.9$$

$$1mA = \frac{k'_p}{2} \left(\frac{W}{L} \right)_2 (0.4)^2 \Rightarrow \left(\frac{W}{L} \right)_2 = 217.4$$

TAKE : $W_1 = 45 \mu m$, $W_4 = 4.5 \mu m$
 $W_2 = 220 \mu m$, $W_5 = 22 \mu m$

FREQUENCY RESPONSE

(DISCUSS MOS CAPACITANCE MODEL)

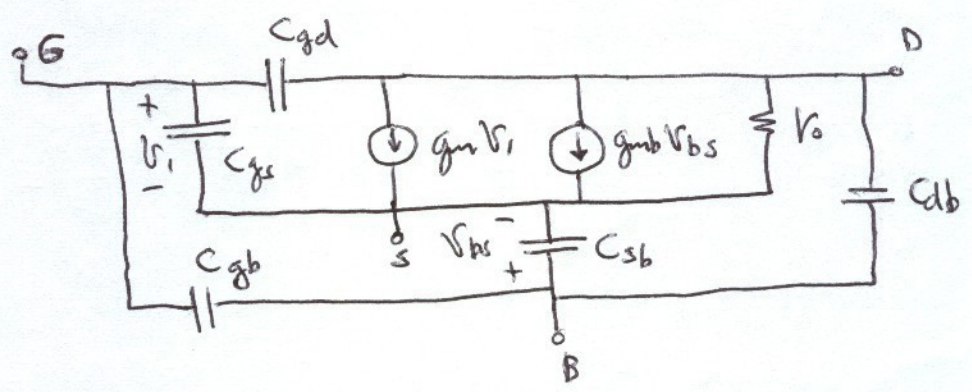

$$C_{gs} = \frac{2}{3} C_{ox} W L_{eff} + W L_d C_{ox}$$



$$C_{gd} = W L_d C_{ox}$$

$$C_{sb} = \frac{C_{sbo}}{\left(1 + \frac{V_{SB}}{\psi_0}\right)^{\frac{1}{2}}}, \quad C_{db} = \frac{C_{dbo}}{\left(1 + \frac{V_{DB}}{\psi_0}\right)^{\frac{1}{2}}}$$

(GO BACK TO PAGE 10 AND EXPLAIN SIDEWALL CAPACITANCES.)

C_{gb} : CAPACITANCE OF THE ROUTING THAT CONNECTS THE ~~DRAIN~~ GATE.

TRANSITION FREQUENCY

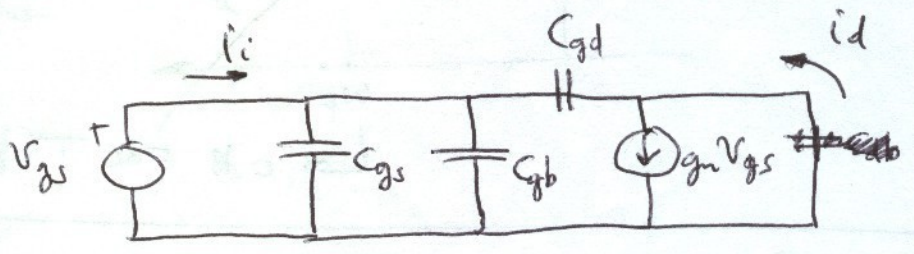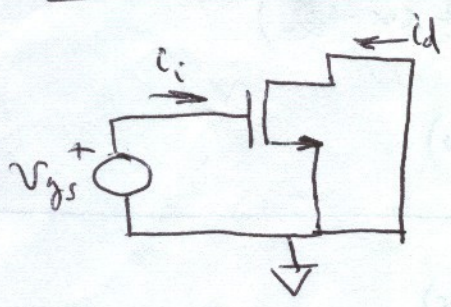

$$i_i = \frac{V_{gs}}{[s(C_{gs} + C_{gb} + C_{gd})]^{-1}} = V_{gs} s (C_{gs} + C_{gb} + C_{gd})$$

$$i_d \approx g_m V_{gs}$$

$$\frac{i_d}{i_i} \approx \frac{g_m}{s (\sum C)}$$

$$\omega_T \rightarrow \left| \frac{i_d}{i_i} \right| = 1 \Rightarrow \omega_T = \frac{g_m}{C_{gs} + C_{gb} + C_{gd}}$$

IF $C_{gs} \gg C_{gb}$ AND C_{gd} :


$$f_T \approx \frac{g_m}{2\pi C_{gs}} = \frac{\frac{k' W}{L} V_{ov}}{2\pi C_{gs}} = \frac{\mu_n C_{ox} V_{ov} \frac{W}{L}}{2\pi \frac{2}{3} C_{ox} W L} = \frac{3\mu_n}{4\pi L^2} \cdot V_{ov}$$

$$V_{ov} \uparrow \rightarrow f_T \uparrow$$

$$L \downarrow \rightarrow f_T \uparrow \quad \text{QUADRATICALLY}$$

(51)

STABILITY OF FEEDBACK AMPLIFIERS (CH9)

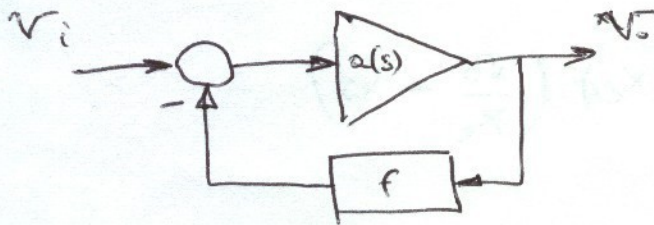


$$T(j\omega) = A(s)f \quad \leftarrow \text{OPEN-LOOP TRANSFER FUNCTION}$$


$$T_o = a_o f$$

$$A(s) = \frac{V_o}{V_i} = \frac{a(s)}{1 + a(s)f}, \quad a(s) = \frac{a_o}{1 - \frac{s}{p_1}}$$
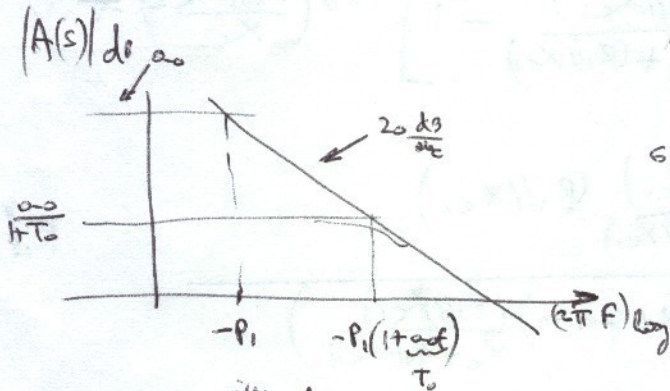
$$A(s) = \frac{a_o}{1 + a_o f} \left(\frac{1}{1 - \frac{s}{p_1}} \frac{1}{1 + a_o f} \right) \left(\sim \frac{1}{f} \text{ IF } a_o \rightarrow \infty \right)$$



GAIN * PRODUCT = CONSTANT.

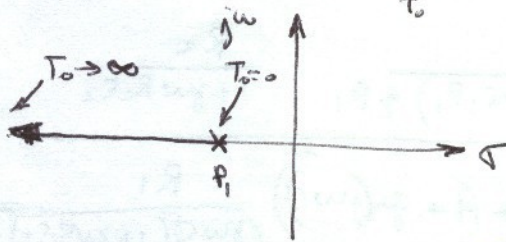

LOCUS OF POLE

$$T_{dB} = a_{dB} + f_{dB} \Rightarrow T = a_{dB} - \left(\frac{1}{f}\right)_{dB}$$


(MENTION NYQUIST CRITERION)
(MENTION GAIN PEAKING).

$$\text{PHASE } T(j\omega_o) = -135^\circ$$

$$|T(j\omega_o)| = 1$$



$$|a(j\omega_o)f| = 1$$

$$|A(j\omega_o)| = \frac{|a(j\omega_o)|}{|1 - 0.7 - j0.7|} = \frac{1.3}{f} > \frac{1}{f}$$

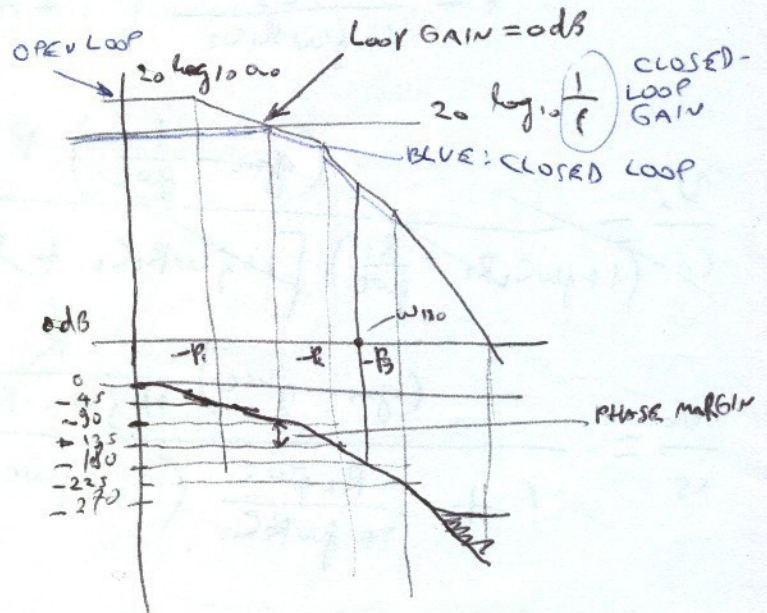


Bode Plot: $f = 0.01$



$$T(s) = a(s)f$$

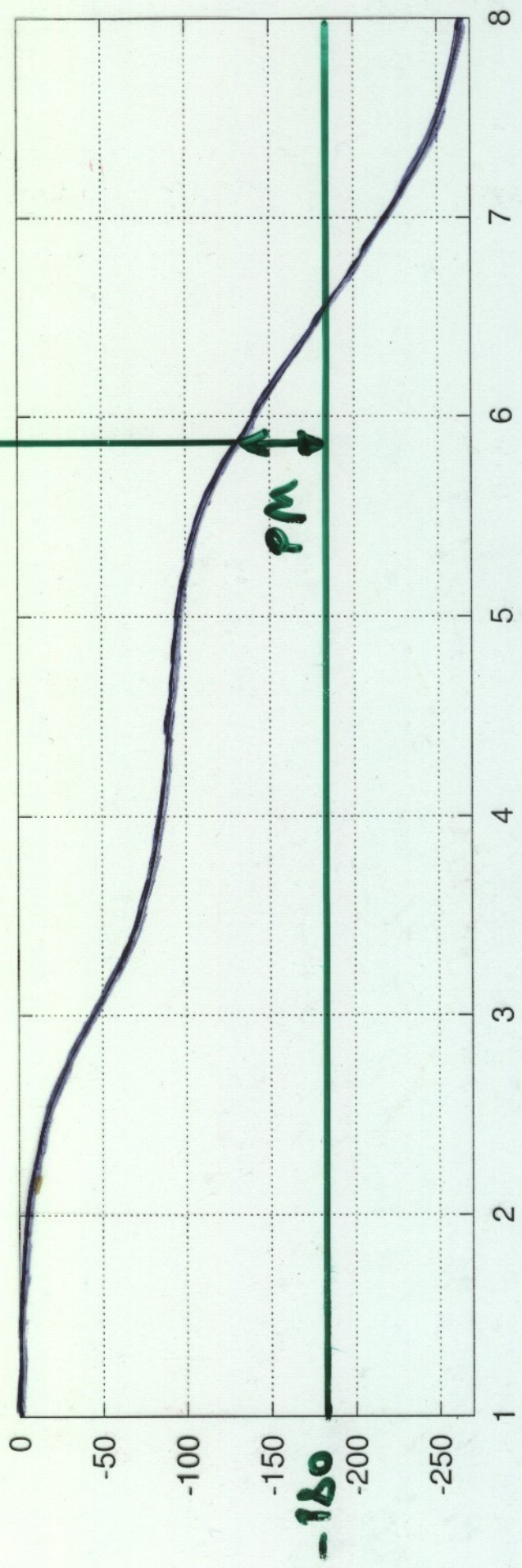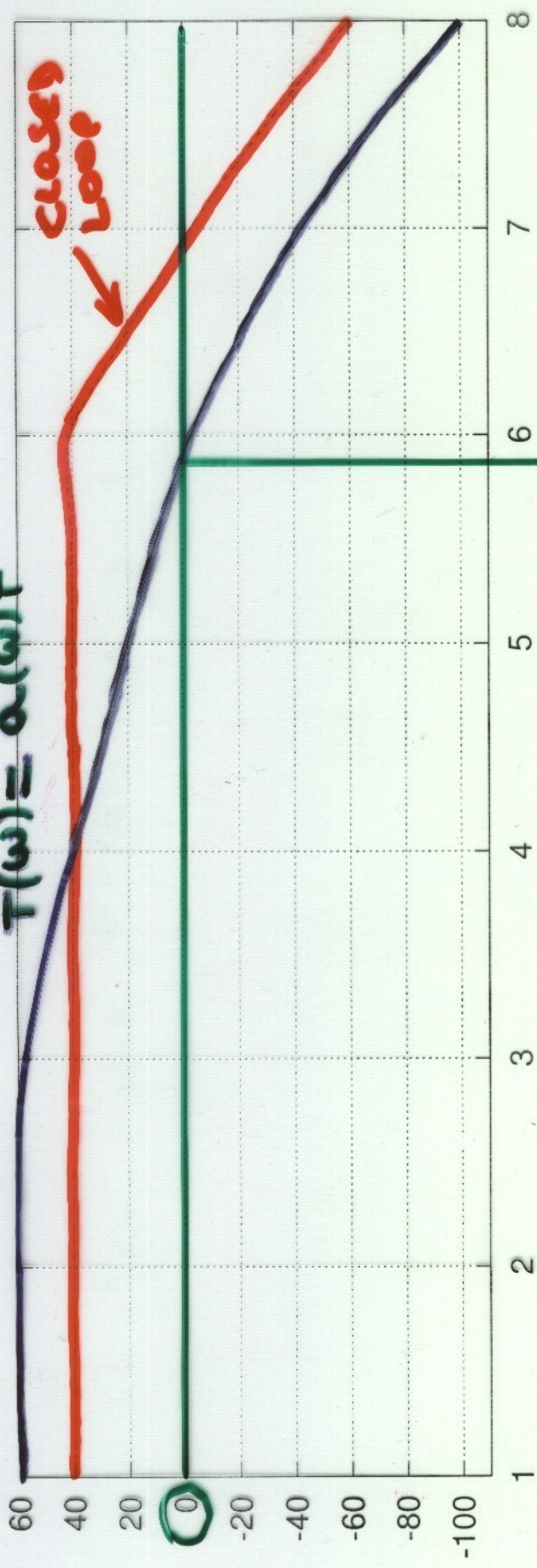



NYQUIST : $f = 0.1$

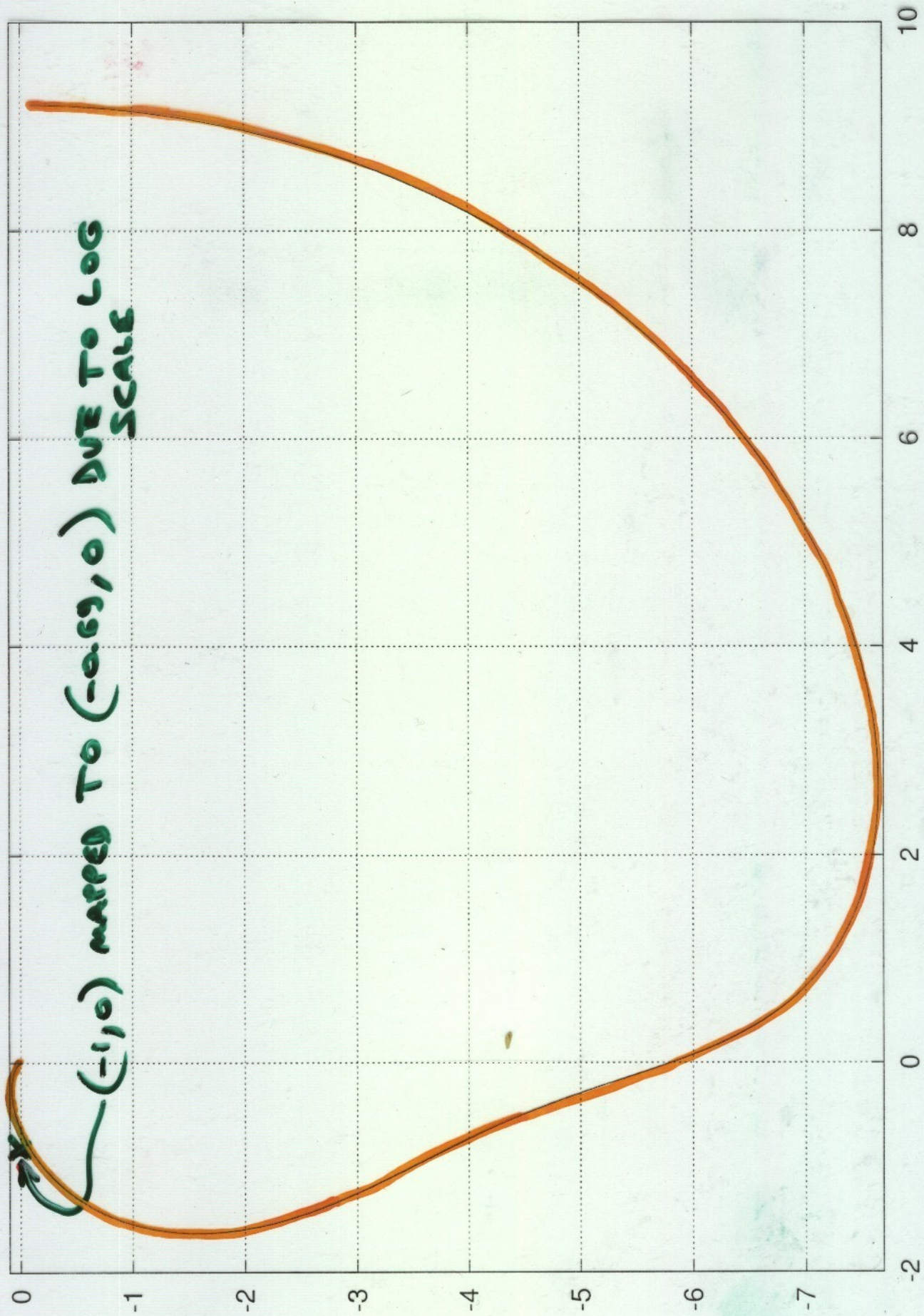

Bode plot: $f = \omega \text{ rad/s}$

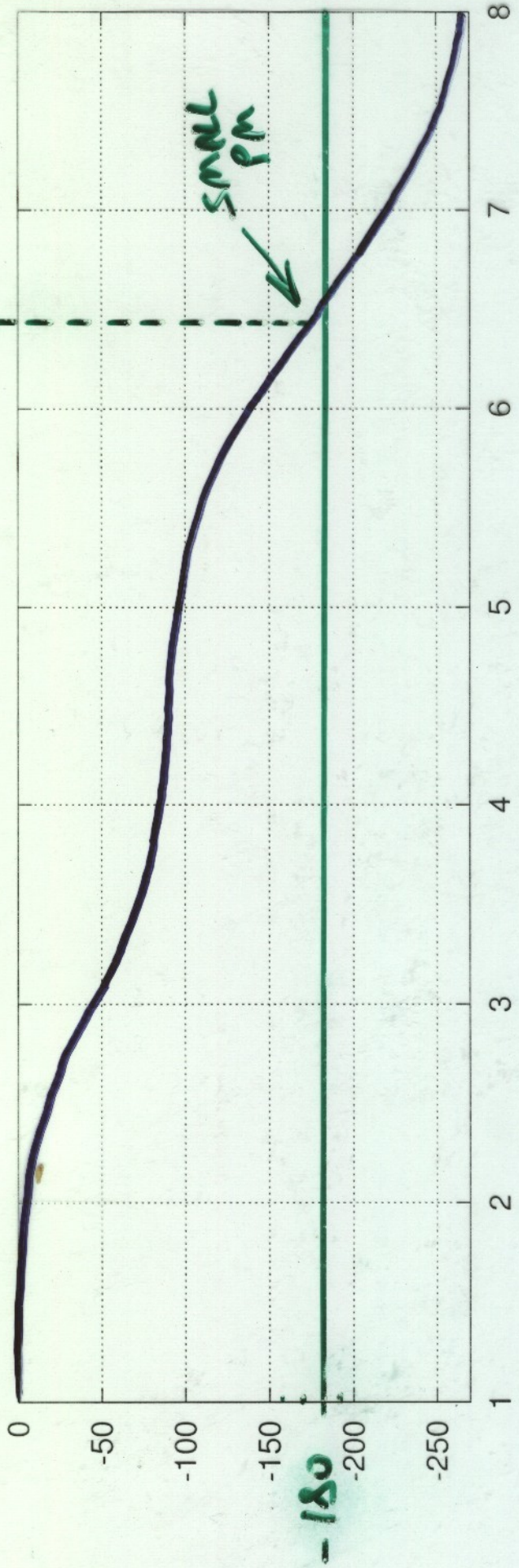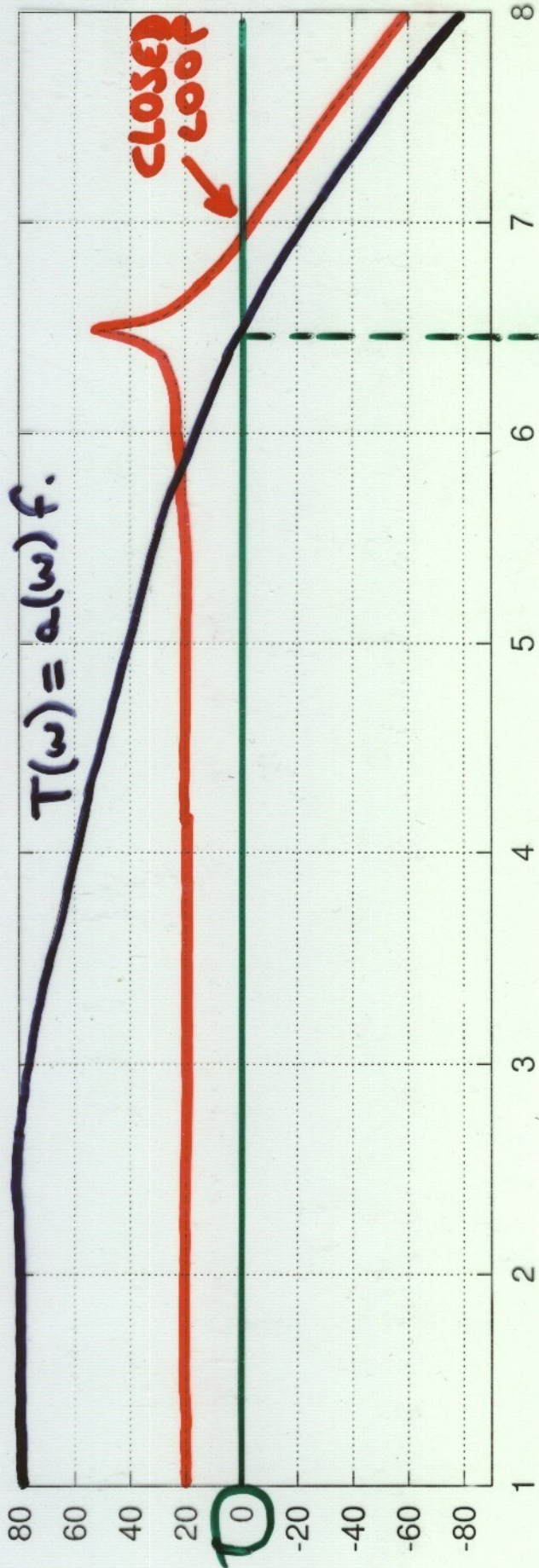

BOSE PLOT : $f = 0.01$

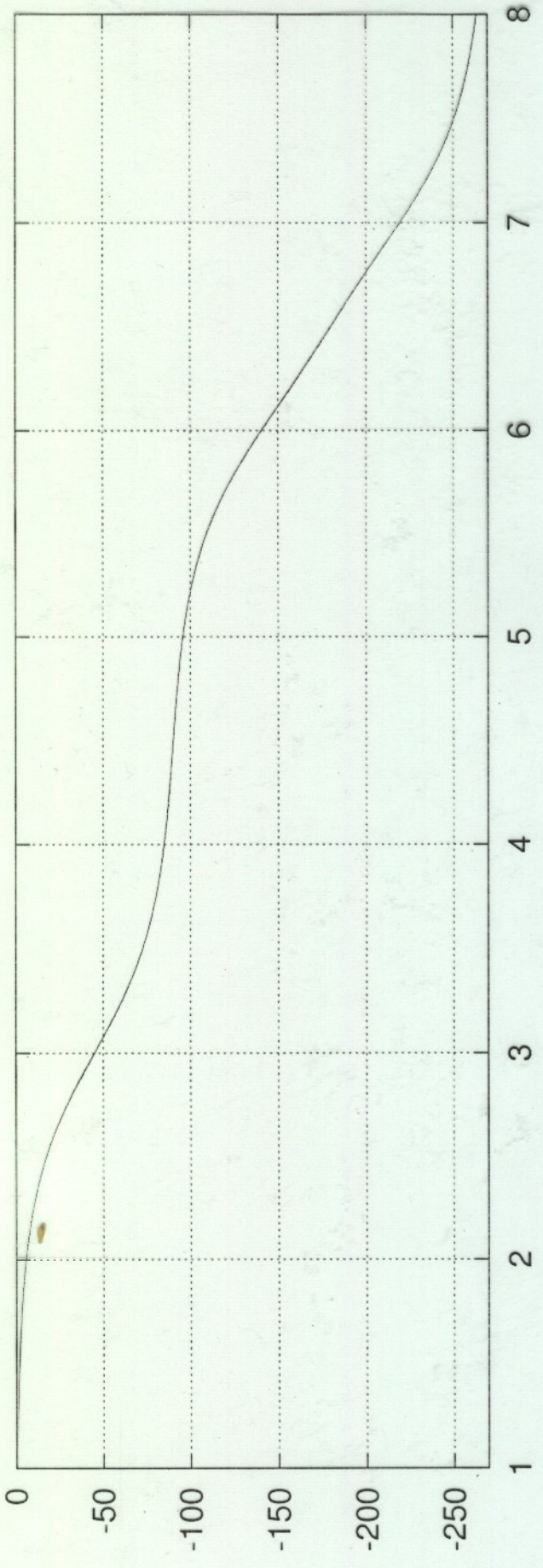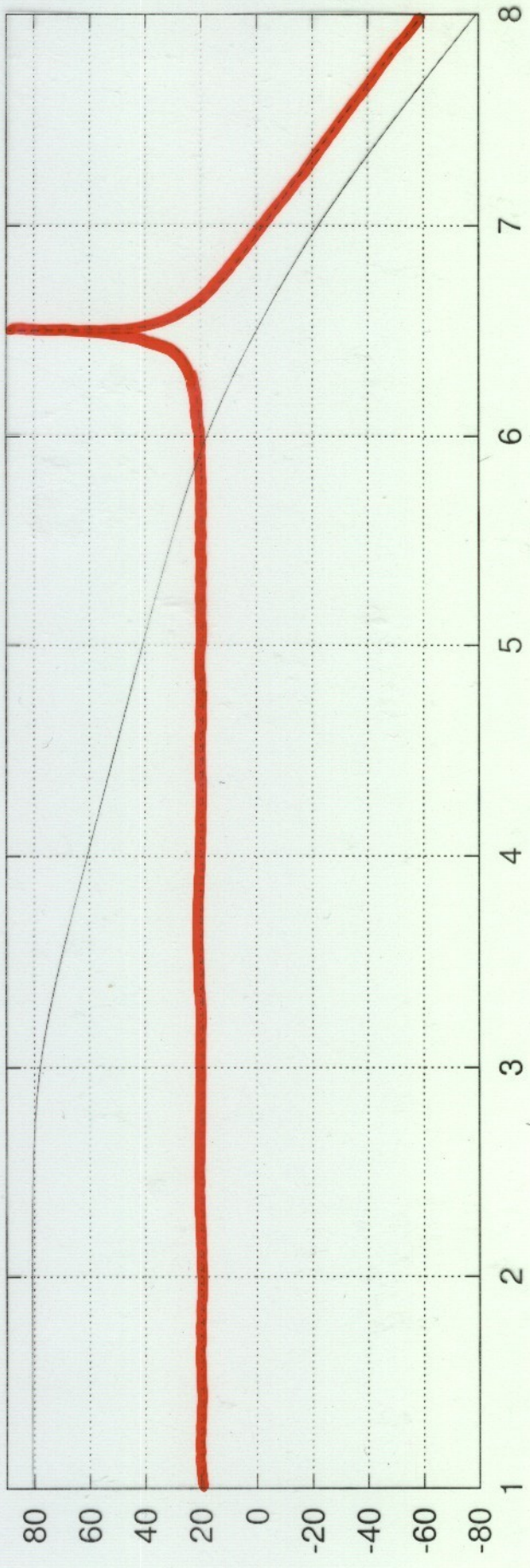

EXAMPLE

$$Q(\omega) = \frac{10^5}{\left(1 + j \frac{\omega}{2\pi \times 1 \text{ kHz}}\right) \left(1 + j \frac{\omega}{2\pi \times 1 \text{ MHz}}\right) \left(1 + j \frac{\omega}{2\pi \times 10 \text{ MHz}}\right)}$$

$$f = 0.01$$


$$f = 0.1$$

$$T(\omega) = Q(\omega) F \quad \text{LOOP TRANSFER FUNCTION}$$

in dB: $20 \log_{10} (T(\omega)) = 20 \log_{10} |Q(\omega)| - \underbrace{20 \log_{10} \left(\frac{1}{F}\right)}_{\approx \text{CLOSED-LOOP DC GAIN}}$

$F = 0.01 \Rightarrow$ SUBTRACT 40 dB
 $F = 0.1 \Rightarrow$ SUBTRACT 20 dB.

$a_0 \approx 100 \text{ dB.}$

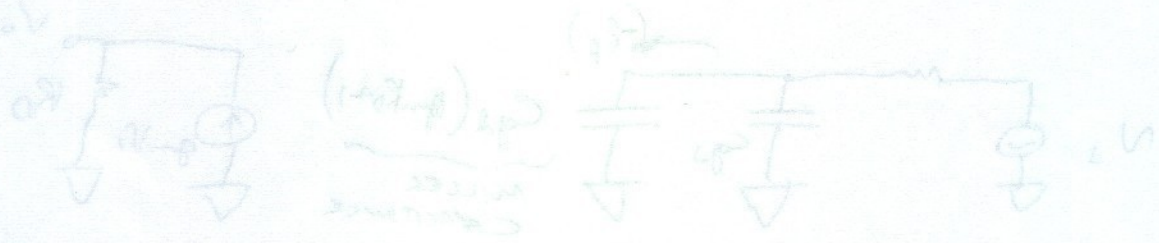


$\left. \begin{aligned} C_1 &= 10 \text{ pF} \\ C_2 &= 0.01 \text{ pF} \\ R_1 &= (100 + 100) = 200 \text{ k}\Omega \end{aligned} \right\}$

$$C_1 \gg C_2 \Rightarrow \frac{C_1}{C_2} \gg 1 \Rightarrow \frac{10 \text{ pF}}{0.01 \text{ pF}} = 1000$$

$$C_M = (1 + 10) \times 0.01 \text{ pF} = 11 \text{ pF} \gg C_2 = 0.01 \text{ pF}$$



$$20 \log_{10} \left(\frac{1}{F} \right) = 20 \log_{10} \left(\frac{1}{0.01} \right) = 40 \text{ dB}$$

COMPENSATION (FIG. 9.12)

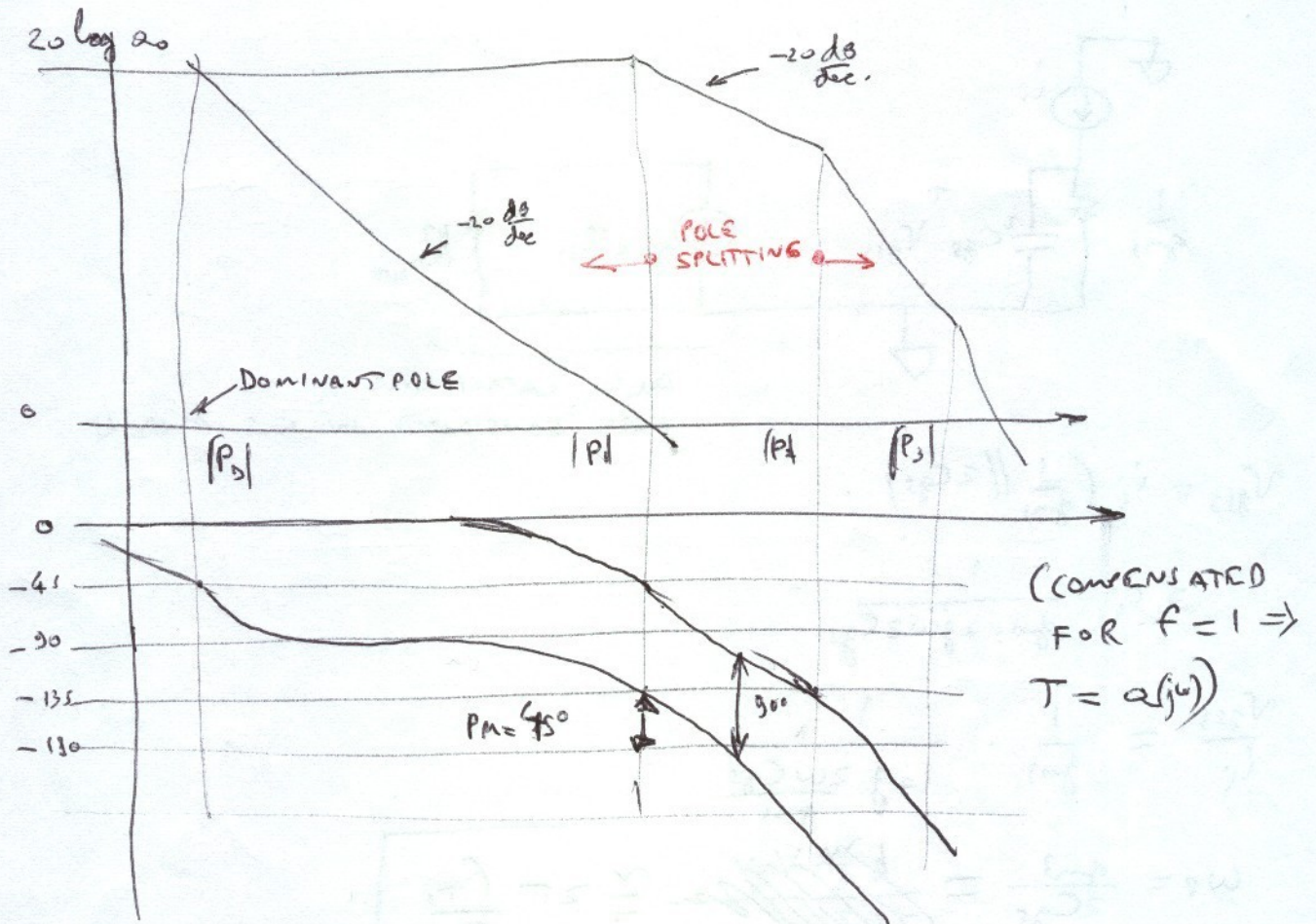

- SIMPLE
- BANDWIDTH GREATLY REDUCED
- CAP. CAN NOT BE INTEGRATED (COMMENT EXAMPLE P. 635)
- SOMETIMES COMPENSATION IS MADE FOR $f < 1$
- IDEA: ~~MOVE P_2 TO A LOWER P_1~~ LOWER P_1 INSTEAD \rightarrow BANDWIDTH DEPENDS ON (P_2) (FIG. 9.15 P. 638)

POLE SPLITTING

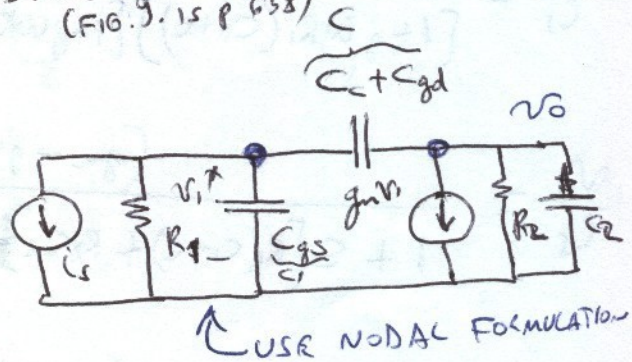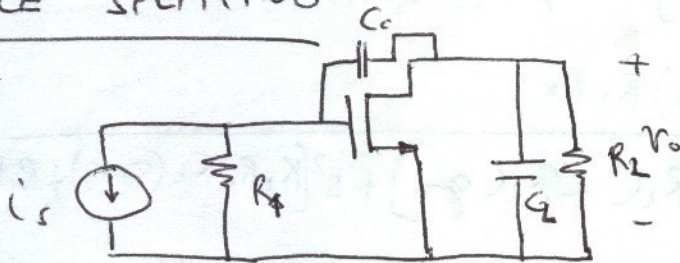

\uparrow USE NODAL FORMULATION

$$\frac{V_o}{i_s} = \frac{(g_m - C_{gs}s) R_2 R_1}{1 + s[(C_1 + C_c) R_2 + (C_1 + C_c) R_1 + g_m R_1 R_1 C] + s^2 R_2 R_1 (C_1 C_1 + C C_2 + C C_c)}$$

ZERO $\rightarrow z = \frac{g_m}{C}$ (HIGH IN BIPOLAR, LOW IN MOS)

DENOMINATOR
 $D(s) = \left(1 - \frac{s}{p_1}\right) \left(1 + \frac{s}{p_2}\right) = 1 - s \left(\frac{1}{p_1} + \frac{1}{p_2}\right) + \frac{s^2}{p_1 p_2}$


IF $|p_2| \gg |p_1| \Rightarrow D(s) \approx 1 - \frac{s}{p_1} - \frac{s^2}{p_1 p_2}$

$\therefore p_1 \approx - \frac{1}{(C_2 + C)R_2 + (C_1 + C)R_1 + g_m R_2 R_1} \approx - \frac{1}{(g_m R_2 C) R_1}$ WITH C
↓

MILLER CAP.


$p_2 \approx - \frac{g_m C}{C_2 C_1 + C(C_2 + C_1)}$ ↑ WITH C (AT LEAST INITIALLY) FOR SMALL C

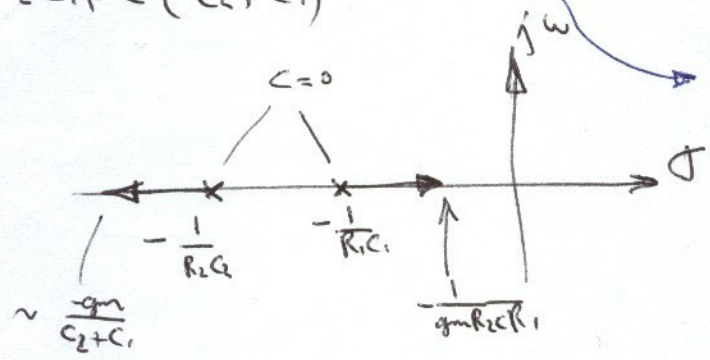SINCE $C_1, C_2 \gg C_1$
 $p_2 \approx - \frac{g_m}{C_2 + C_1}$



• COMMON-SOURCE STAGES GENERALLY PRODUCE A DOMINANT POLE (POLE-SPLITTING OCCURS)


TWO-STAGE MOS AMPLIFIER COMPENSATION

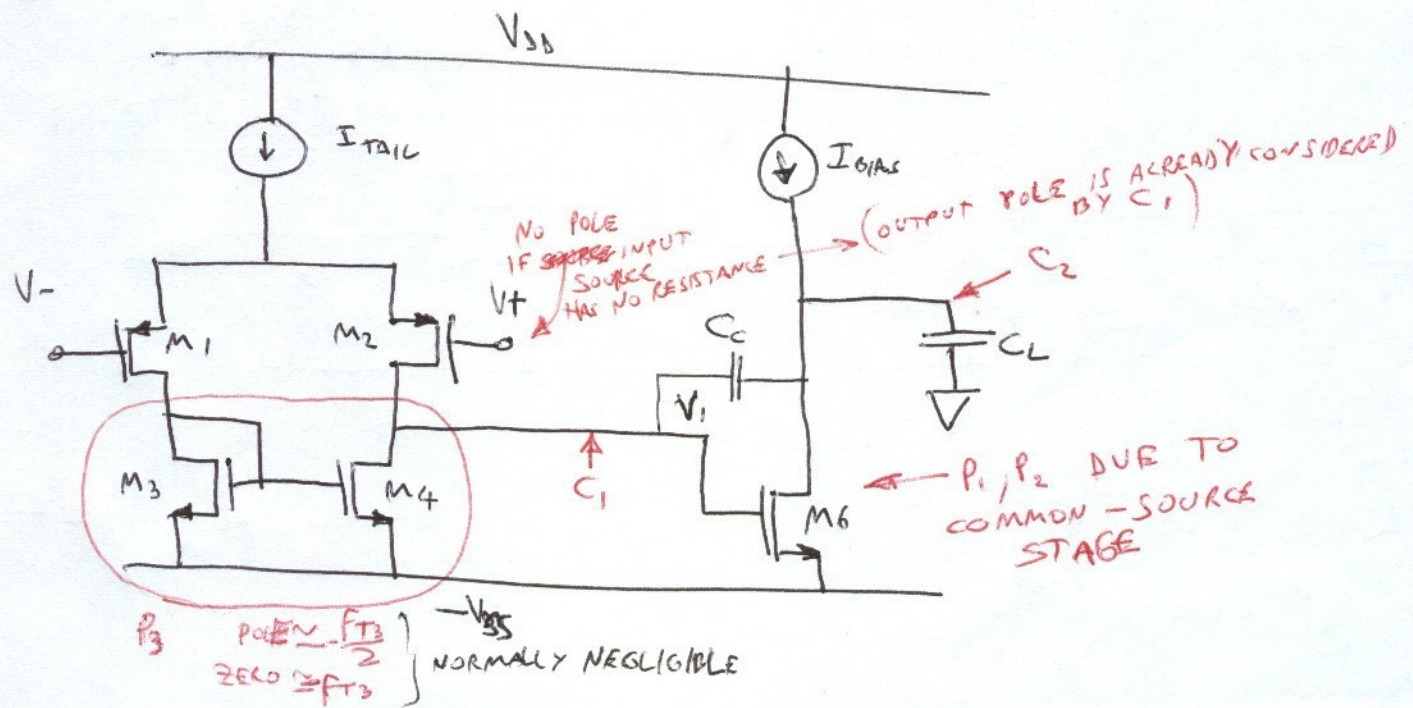

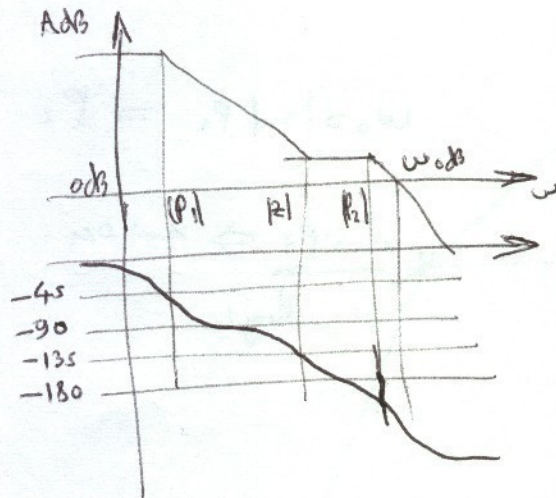PROBLEM:

$Z = \frac{g_{m6}}{C}$ SOMETIMES BELOW ω_{odb}

• ZERO IN POSITIVE HALF PLANE \Rightarrow REDUCES PHASE MARGIN




EXPLANATION: C_c ACTS AS A SHORT THAT BYPASSES M_6 AT HIGH FREQ \Rightarrow ~~MAKES~~ ^{ADDS} 180° PHASE SHIFT.

SOLUTIONS:

1) USE SOURCE-FOLLOWER TO BLOCK CURRENT FEED-FORWARD:


(ELIMINATES ZERO)

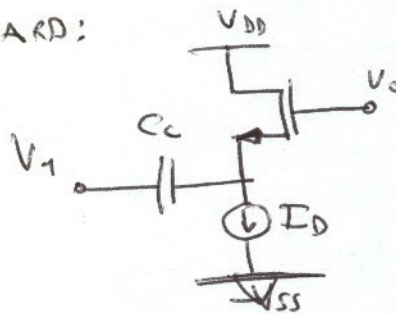

PROBLEMS:


- EXTRA BIASING CURRENT \rightarrow NOT IF OUTPUT STAGE IS USED
- REDUCED SWING

2) USE COMMON-DRAIN STAGE:

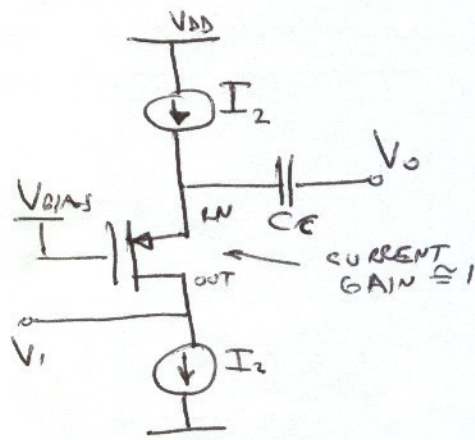


ELIMINATES ZERO AND ~~WIRE~~ MOVES P_2 UP, BECAUSE THE INPUT IS NO LONGER LOADED BY $C_c \rightarrow$ CAN USE SMALLER C_c

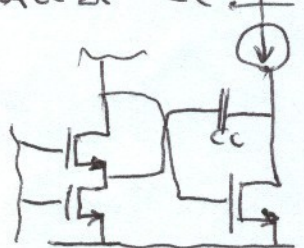• CASCODE AMPLIFIERS DO NOT NEED EXTRA BRANCH.



3) ADD RESISTOR IN SERIES WITH C_c :

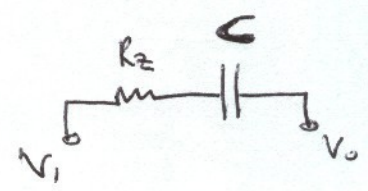

$$P_1 \approx - \frac{1}{g_{m6} R_2 R_1 C}$$

$$P_2 \approx - \frac{g_{m6}}{C_1 + C_2}$$

$$P_3 \approx - \frac{1}{R_2 C_1}$$

TYPICALLY
VERY HIGH FREQ
SINCE R_2, C_1
SMALL.

$$z = \frac{1}{\left(\frac{1}{g_{m6}} - R_2\right) C}$$

$$R_2 = \frac{1}{g_{m6}} \Rightarrow z \rightarrow \infty$$

$R_2 > \frac{1}{g_{m6}} \Rightarrow$ NEGATIVE SEMIPLANE
ZERO HELPS WITH
PHASE MARGIN.

EXAMPLE: COMPENSATE ~~BY~~ SAMPLE O.A. DESIGNED
BEFORE FOR $PM=45^\circ$, $C_L=5PF$, UNITY FEEDBACK
(PAGE 550)

IF $P_1 \ll P_2 \Rightarrow$ MOVE P_1 DOWN TO MAKE ω_{uds} COINCIDENT
WITH P_2 . BETWEEN P_1, P_2 WE HAVE $-40 \frac{dB}{dec}$.

$$a_o |P_1| = |P_2|$$

$$a_o \approx g_{m1} (r_{o1} || r_{o4}) g_{m6} (r_{o6} || r_{o7}) = g_{m1} R_1 g_{m6} R_2$$

$$R_2 \approx \frac{1}{g_{m6} R_1 C} = \frac{g_{m6}}{C_1 + C_2} \quad \text{with } C_L=5PF \Rightarrow \text{PARASITIC CAPS.}$$


$$\frac{g_{m1}}{C} \approx \frac{g_{m6}}{C_L}$$

$$\left. \begin{aligned} g_{m1} &= \frac{1mA}{V} \\ g_{m6} &= \frac{1.55mA}{V} \end{aligned} \right\}$$

$$\Rightarrow \boxed{C = 3.2 PF}$$

$$\boxed{R_2 = \frac{1}{g_{m6}} = 645 \Omega}$$

SHOW FIG. 9.29
PAGE 653

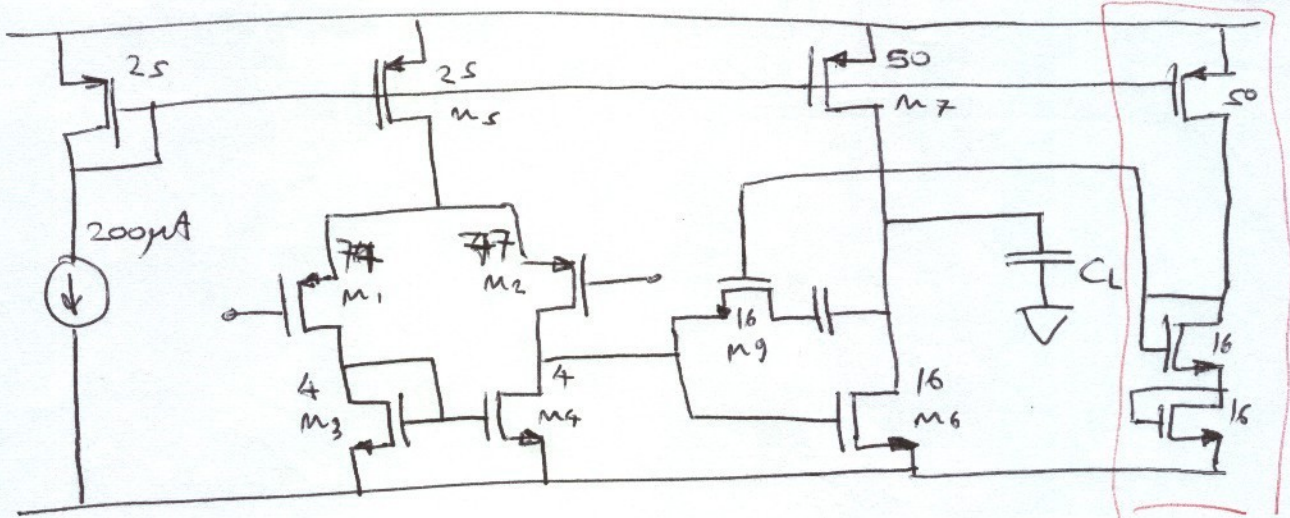

REPLICA
BIASING
(EXTRA CURRENT)

$A_{dm} = 7471$
 $\omega_{0dB} = \begin{cases} \approx 350 \text{ MHz BEFORE COMP. (UNSTABLE)} \\ \approx 35 \text{ MHz AFTER COMP.} \end{cases}$

NOTE THAT

CONST = GAIN X BANDWIDTH CAN NOT BE USED IF THE DOMINANT POLE IS NOT THE ONLY ONE UNTIL ω_{0dB}

OBSERVATION: IF A CLASS AB OUTPUT STAGE IS USED, THERE IS NO NEED FOR RESISTOR. SINCE THE ZERO IS ELIMINATED WITH METHOD (1).

$r_{ds16} = \frac{1}{\frac{\partial I_{D16}}{\partial V_{ds}}}$, $\frac{\partial I_{D16}}{\partial V_{ds}} = \frac{k'}{2} \frac{W}{L} (2V_{ov} - 2V_{ds})$
 $\approx k' \frac{W}{L} V_{ov}$ if $V_{ds} \ll V_{ov}$

$\therefore r_{ds16} = \frac{1}{g_{m16}}$ IF $\left[\begin{aligned} \left(\frac{W}{L}\right)_{16} &= \left(\frac{W}{L}\right)_6 \\ \text{AND} \\ V_{ov16} &= V_{ov6} \end{aligned} \right.$

$C_{min} \approx \frac{1 \text{ fF}}{\mu\text{m}^2}$