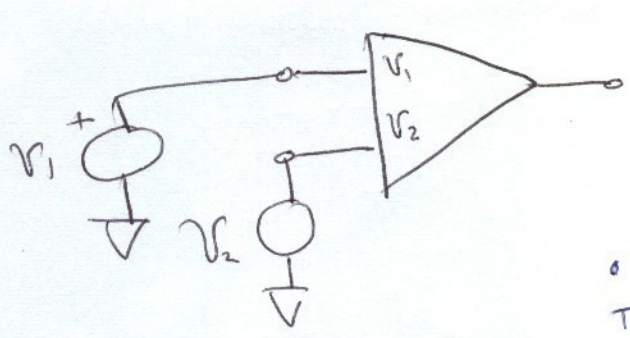



DIFFERENTIAL AMPLIFIERS



$$v_0 = A_{dm} (v_1 - v_2)$$

↑ OUTPUT PROPORTIONAL TO DIFFERENCE.

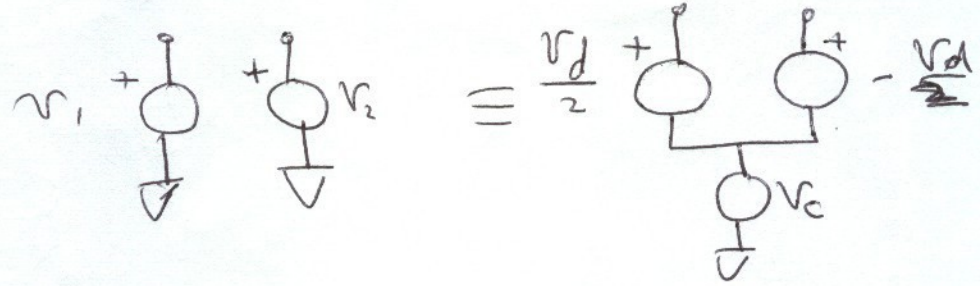• NO NEED OF CAPACITORS OR LEVEL SHIFTERS TO COUPLE DIFFERENTIAL AMPS.



$$\begin{cases} v_d = v_1 - v_2 \\ v_c = \frac{v_1 + v_2}{2} \end{cases}$$


• IN PRACTICE, AMPLIFIERS RESPOND TO COMMON-MODE VOLTAGE IN ADDITION TO DIFFERENTIAL VOLTAGE.

$$A_{dm} = \frac{v_0}{v_d}$$

$$A_{cm} = \frac{v_0}{v_c}$$

$$CMRR = \frac{A_{dm}}{A_{cm}} \quad , \quad CMRR \text{ HIGH IS GOOD.}$$

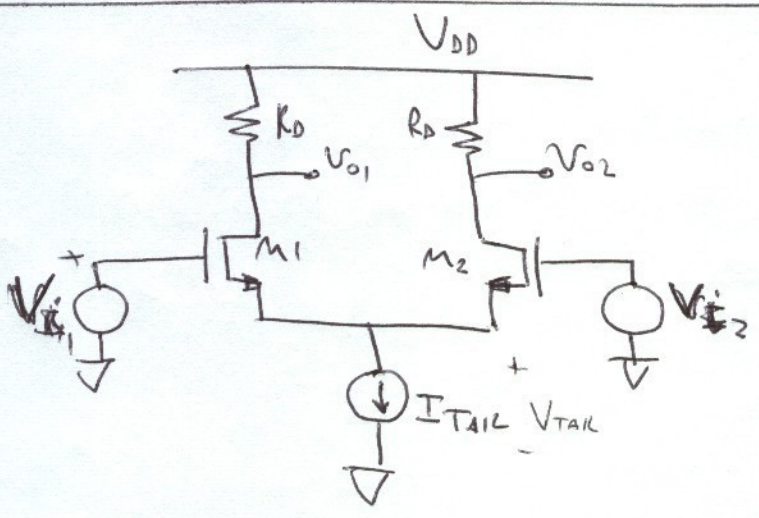DC TRANSFER OF A SOURCE-COUPLED PAIR (3.5.1)



- ASSUME $\lambda = 0$,
- NO BODY EFFECT.
- DISCUSS COMMON-MODE VOLTAGE RANGE

$$V_{d1} - V_{gs1} + V_{gs2} - \sqrt{I_{d2}} = 0$$

$$V_{gs1} = V_t + \sqrt{\frac{2I_{d1}}{k' \frac{W}{L}}}, \quad V_{gs2} = V_t + \sqrt{\frac{2I_{d2}}{k' \frac{W}{L}}}$$

$$V_{id} = V_{d1} - V_{d2} = V_{gs1} - V_{gs2} = \frac{\sqrt{I_{d1}} - \sqrt{I_{d2}}}{\sqrt{\frac{k' W}{2L}}}$$

BUT $I_{d1} + I_{d2} = I_{TAIL}$


$$\therefore I_{d1} = \frac{I_{TAIL}}{2} + \frac{k' W}{4L} V_{id} \sqrt{\frac{4I_{TAIL}}{k' W} - V_{id}^2}$$

VALID FOR $0 \leq I_{d1} \leq I_{TAIL}$

$$|V_{id}| \leq \sqrt{\frac{2 I_{TAIL}}{k' \frac{W}{L}}}$$

$$V_{id} = 0 \Rightarrow I_{d1} = I_{d2} = \frac{I_{TAIL}}{2} \Rightarrow I_{TAIL} = 2I_{d1} \Big|_{V_{id}=0}$$

$$|V_{id}| \leq \sqrt{2} \sqrt{\frac{2 I_{d1} \Big|_{V_{id}=0}}{k' \frac{W}{L}}} = \sqrt{2} V_{ov} \Big|_{V_{id}=0}$$

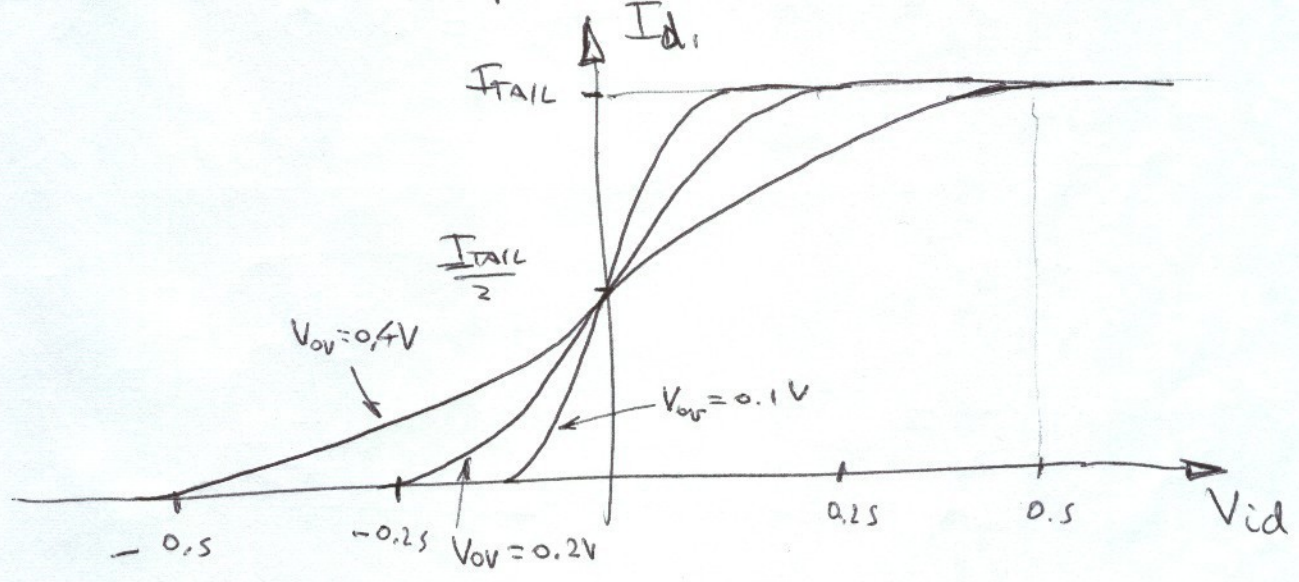


SMALL-SIGNAL ANALYSIS

- DIFFERENTIAL MODE : $A_{dm} = -g_m (r_o // R_D)$

$$A_{dmSE} = \pm \frac{g_m (r_o // R_D)}{2}$$

(SINGLE OUTPUT, DEPENDING WHICH ONE)

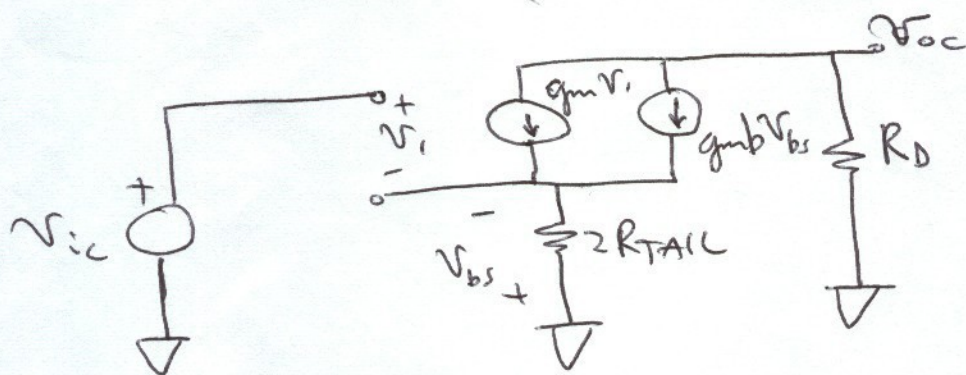- COMMON MODE : (FOR NOW NEGLECT EFFECT OF r_o)



$$V_{oc} = -(g_m V_i + g_{mb} V_{sb}) R_D$$

$$V_i = V_{ic} - V_{sb}, \quad V_{sb} = (g_m V_i - g_{mb} V_{sb}) 2R_{TAIL}$$

$$V_{sb} = [g_m (V_{ic} - V_{sb}) - g_{mb} V_{sb}] 2R_{TAIL}$$

$$V_{sb} \left(\frac{1}{2R_{TAIL}} + g_m + g_{mb} \right) = g_m V_{ic}$$

$$V_{sb} = \frac{g_m}{\frac{1}{2R_{TAIL}} + g_m + g_{mb}} V_{ic}$$

$$\frac{V_{oc}}{R_D} = -g_m (V_{ic} - V_{sb}) + g_{mb} V_{sb}$$

$$\frac{V_{oc}}{R_D} = -g_m V_{ic} + (g_m + g_{mb}) \frac{g_m}{\frac{1}{2R_{TAIL}} + g_m + g_{mb}} V_{ic}$$

$$\frac{V_{oc}}{V_{ic}} = \left[-g_m + (g_m + g_{mb}) \frac{g_m}{\frac{1}{2R_{TAIL}} + g_m + g_{mb}} \right] R_D$$

$$\frac{V_{oc}}{V_{cc}} = \frac{-g_m \left(\frac{1}{2R_{TAIL}} + g_{m1} + g_{m2} \right) + g_m (g_{m1} + g_{m2})}{\frac{1}{2R_{TAIL}} + g_{m1} + g_{m2}} R_D$$



$$= - \frac{g_m R_D}{1 + \frac{(g_{m1} + g_{m2})}{2R_{TAIL}}}$$

$$A_{cm} = - \frac{g_m R_D}{1 + 2(g_{m1} + g_{m2})R_{TAIL}}$$

$$CMRR = \frac{A_{dm}}{A_{cm}} \approx 1 + 2(g_{m1} + g_{m2})R_{TAIL}$$

(NEGLECTING r_o) (DIFF. OUTPUT).

INPUT OFFSET VOLTAGE (DUE TO MISMATCH)

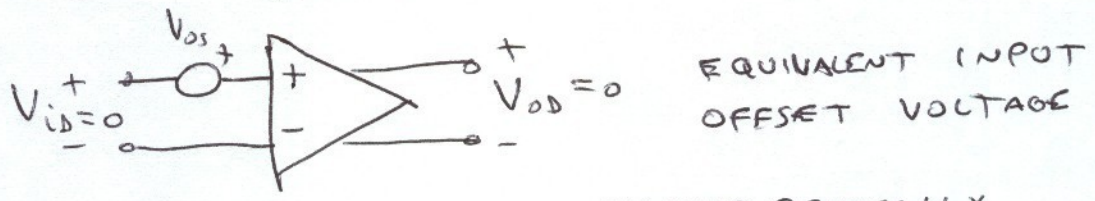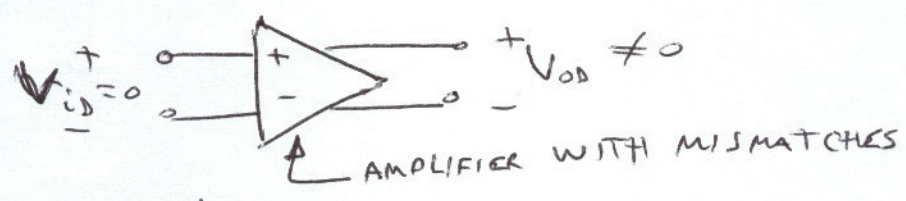

• OFFSET CURRENT IN CMOS AMPLIFIERS GENERALLY NEGLIGIBLE.

$$V_{os} = \underbrace{\Delta V_t}_{\text{AROUND } 2\text{mV}} + \frac{V_{ov}}{2} \left(- \frac{\Delta R_D}{R_D} - \frac{\Delta \left(\frac{W}{L} \right)}{\left(\frac{W}{L} \right)} \right)$$

$V_{ov} \uparrow \implies$ MORE OFFSET DUE TO MISMATCH IN R_D AND $\frac{W}{L}$.