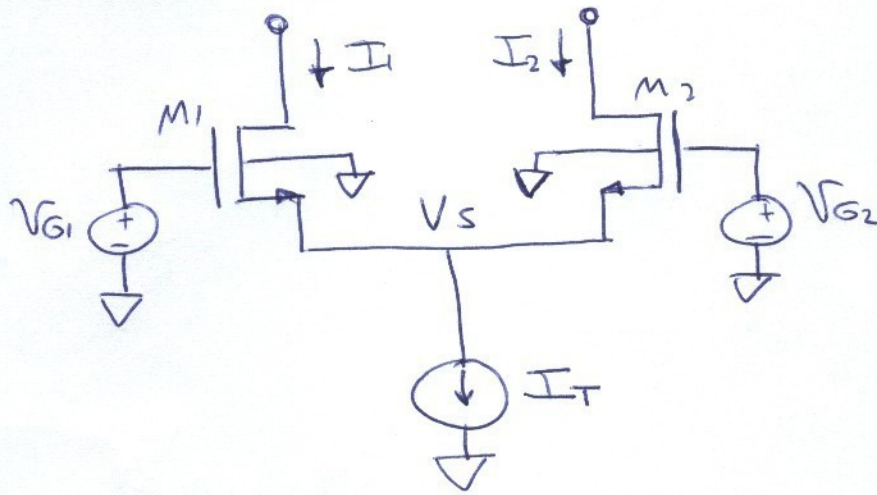


DIFFERENTIAL AMPLIFIER: SOURCE-COUPLED PAIR

①



$$V_{ID} = V_{G1} - V_{G2}$$

• ASSUME $M_1 = M_2$, AND BOTH IN ACTIVE REGION ($i_f \gg i_r$)

$$\left. \begin{aligned} I_{OD} &= I_1 - I_2 \\ I_T &= I_1 + I_2 \end{aligned} \right\} \Rightarrow \begin{cases} I_1 = \frac{I_{OD} + I_T}{2} \\ I_2 = \frac{I_T - I_{OD}}{2} \end{cases}$$

$$\left\{ \begin{aligned} \frac{V_{P1} - V_S}{V_T} &= \mathcal{F}\left(\frac{I_1}{I_S}\right) \quad (\text{SAME FOR } M_2) \\ V_{P1} &\approx \frac{V_{G1} - V_{th}}{n} \end{aligned} \right.$$

$$\frac{V_{G1} - V_{th}}{nV_T} - \frac{V_S}{V_T} = \mathcal{F}\left(\frac{I_1}{I_S}\right)$$

$$\therefore \mathcal{F}\left(\frac{I_1}{I_S}\right) - \mathcal{F}\left(\frac{I_2}{I_S}\right) = \frac{V_{G1} - V_{G2}}{nV_T} = \frac{V_{ID}}{nV_T}$$

$$\boxed{\frac{V_{ID}}{nV_T} = \mathcal{F}\left(\frac{I_{OD} + I_T}{2}\right) - \mathcal{F}\left(\frac{I_T - I_{OD}}{2}\right)}$$

NOTE: INDEPENDENT OF V_S

• WEAK INVERSION:

$$\frac{I_{OD}}{I_T} = \tanh\left(\frac{V_{ID}}{2nV_T}\right) \quad (\text{SAME AS WITH BJT})$$

(SATURATION FOR $|V_{ID}| \geq 4nV_T$)

• STRONG INVERSION

$$\frac{I_{OD}}{I_T} = \frac{V_{ID}}{n V_T \sqrt{\frac{I_T}{I_S}}} \sqrt{2 - \left(\frac{V_{ID}}{n V_T \sqrt{\frac{I_T}{I_S}}}\right)^2}, \quad \frac{|V_{ID}|}{n V_T \sqrt{\frac{I_T}{I_S}}} \leq 1$$

(SATURATION FOR $|V_{ID}| > n V_T \sqrt{\frac{I_T}{I_S}}$)

OVERDRIVE VOLTAGE
TO CONDUCT I_T
THROUGH M_1 OR M_2

OBSERVATION: FOR VERY SMALL V_{ID} , $\frac{I_{OD}}{I_T}$ CAN BE


APPROXIMATED LINEAR:

W.I.) $\frac{I_{OD}}{I_T} \approx \frac{V_{ID}}{2 n V_T}$

S.I.) $\frac{I_{OD}}{I_T} \approx \frac{\sqrt{2}}{n V_T \sqrt{\frac{I_T}{I_S}}} \cdot V_{ID}$

SMALL-SIGNAL ANALYSIS: (TO CONFIRM THIS)

$\frac{1}{2}$ DIFFERENTIAL CIRCUIT.

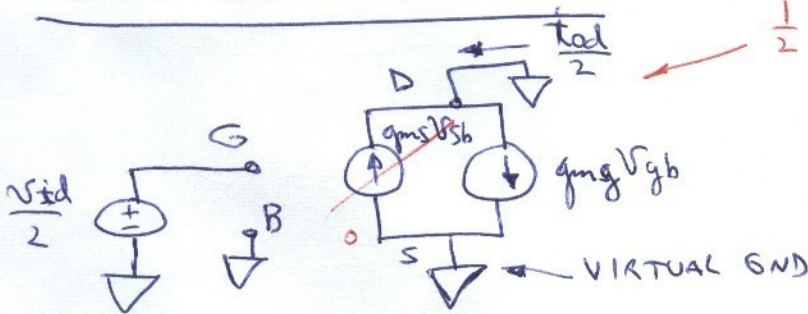

$$g_{mg} = \frac{2 I_S}{n V_T} (\sqrt{1 + i_f} - 1)$$

$$i_f = \frac{I_T}{2 I_S}$$

$$\frac{i_{od}}{2} = g_m \frac{v_{id}}{2}$$

$$i_{od} = g_m v_{id}$$

W.I: $i_{od} \approx \frac{2 I_S}{n V_T} \frac{1}{2} v_{id} = \frac{I_T}{2 n V_T} v_{id}$ ✓

S.I: $i_{od} \approx \frac{2 I_S}{n V_T} \sqrt{i_f} v_{id}$

$$= \frac{2 I_S}{n V_T} \sqrt{\frac{I_T}{2 I_S}} v_{id}$$
 ✓

COMMON-MODE INPUT RANGE

• COMMON-MODE VOLTAGE CONTROLS: V_S


• ASSUME: $V_{G1} = V_{G2} = V_{CM}$

$$V_P = \frac{V_{CM} - V_{th}}{n} \quad (1), \quad \frac{V_P - V_S}{V_T} = f(i_f) \quad (2), \quad i_f = \frac{I_T}{2I_S} \quad (3)$$

$$V_S = -V_T f\left(\frac{I_T}{2I_S}\right) + \frac{V_{CM} - V_{th}}{n}$$

$$= \frac{V_{CM}}{n} - \text{CONSTANT} \quad (\text{ASSUMING } n = \text{CONSTANT})$$

C_1

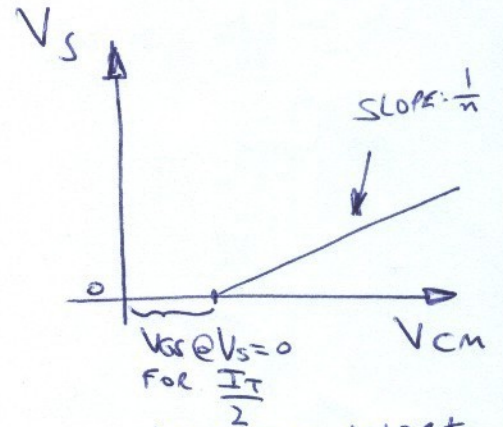

- 2 LIMITS
- CURRENT SOURCE NEEDS MINIMUM V_S TO WORK.
 - M_{1-2} NEED V_{DSSAT} TO BE ACTIVE

$$V_{S_{MIN}} \leq V_S \leq V_D - V_{DSSAT}$$

$$V_{S_{MIN}} \leq \frac{V_{CM}}{n} - C_1 \leq V_D - V_{DSSAT}$$

$$n(V_{S_{MIN}} + C_1) \leq V_{CM} \leq n(V_D - V_{DSSAT} + C_1)$$

EXAMPLE (7.6 SCHNEIDER/GALLUP)

$$I_T = 140 \text{ nA}$$

$$V_{D1} = V_{D2} = 3.3 \text{ V}$$

$$V_{S_{MIN}} = 100 \text{ mV}$$

$$V_{th} = 0.5 \text{ V}$$

$$n = 1.2$$

$$I_{SQ} = 70 \text{ nA}$$

a) $\frac{W}{L} = 100$

$i_f = \frac{140 \text{ nA}}{2 \times \underbrace{70 \text{ nA} \times 100}_{I_s}} = 0.01 \text{ (W.I.)}$

$V_{DSSAT} = V_T (\sqrt{1+i_f} + 3) = 104 \text{ mV}$

$C_1 = \frac{V_{th}}{n} + V_T \mathcal{F}(i_f) = 0.5 \text{ V} + 26 \text{ mV} \mathcal{F}(0.01) = 0.253 \text{ V}$
 $\mathcal{F}(0.01) \approx -6.3$

$0.423 \text{ V} \leq V_{cm} \leq 4.14 \text{ V}$ ← CAN GO LOWER IN W.I.

b) $\left. \begin{matrix} \frac{W}{L} = 0.01 \\ i_f = 100 \end{matrix} \right\} \rightarrow 0.93 \text{ V} \leq V_{cm} \leq 4.37 \text{ V}$

INPUT OFFSET VOLTAGE

ASSUME: $V_{th1} = V_{th2} + \Delta V_{th}$, $I_{s1} = I_{s2} + \Delta I_s$

$I_{D1} \approx I_{s1} i_f(V_G - V_{th1}, V_s)$

~~$I_{D1} \approx I_{D0} + I_{s1} \left[\frac{\partial i_f}{\partial V_G} \Delta V_G - \frac{\partial i_f}{\partial V_{th1}} \Delta V_{th1} + \frac{\partial i_f}{\partial I_{s1}} \Delta I_{s1} \right]$~~

$I_{D2} = I_{D1} + \frac{\partial I_D}{\partial I_s} \Delta I_s + \frac{\partial I_D}{\partial V_G} \Delta V_G + \frac{\partial I_D}{\partial V_{th}} \Delta V_{th}$

$I_{D2} - I_{D1} = \Delta I_s + g_m (\Delta V_G - \Delta V_{th})$

$\frac{\Delta I_D}{I_D} = \frac{\Delta I_s}{I_s} + \frac{g_m}{I_D} (\Delta V_G - \Delta V_{th})$

$\Delta V_G \Big|_{\frac{\Delta I_D}{I_D} = 0} = -\frac{I_D}{g_m} \frac{\Delta I_s}{I_s} + \Delta V_{th}$

$$g_m = \frac{2 I_D}{n V_T} \frac{1}{\sqrt{1 + \frac{I_D}{I_S}}}$$

$$V_{os} = \Delta V_G = - \frac{n V_T}{2} \left(\sqrt{1 + \frac{I_D}{I_S}} + 1 \right) \frac{\Delta I_S}{I_S} + \Delta V_{th}$$

OFFSET VOLTAGE

NOTES: 1. CAN NOT CANCEL ΔV_{th} WITH ΔI_S BECAUSE SIGNS UNKNOWN

2. $\frac{\Delta I_S}{I_S}$ BECOMES LESS IMPORTANT IN MODERATE/WEAK INVERSION \rightarrow BETTER THAN STRONG INVERSION.

EXAMPLE: $I_T = [100 \text{ nA}, 2 \text{ mA}]$
 $I_S = 1 \mu\text{A}$
 $\Delta V_{th} = 1 \text{ mV}$
 $\Delta I_S = 10 \text{ nA}$
 $n = 1.2$
 $V_T = 25 \text{ mV}$

} WORST-CASE V_{os} ?

$$V_{os} = [0.3 \text{ mV} + 1 \text{ mV}, 4.8 \text{ mV} + 1 \text{ mV}]$$

DIFF. MODE COMMON-MODE SMALL-SIGNAL ANALYSIS (NEEDS RESISTIVE LOAD AT LEAST)

(TAKE FROM OLD NOTES)