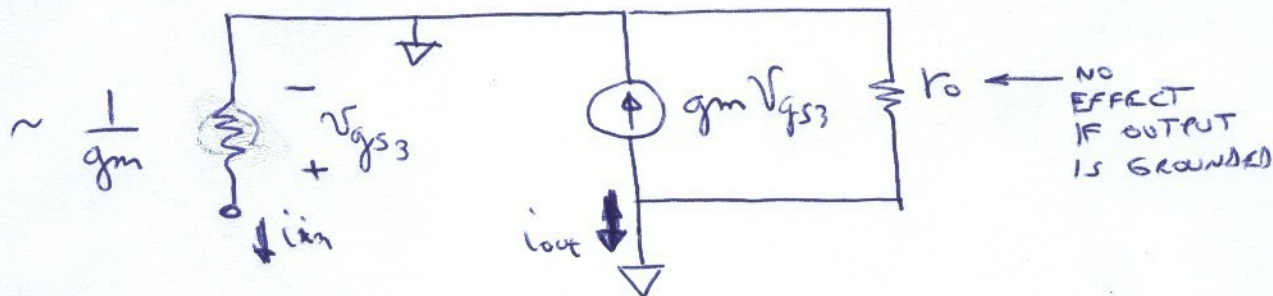



CURRENT - MIRROR LOADED DIFFERENTIAL AMPLIFIER

• CURRENT MIRROR ALONE:




$$i_{out} = i_{in}$$

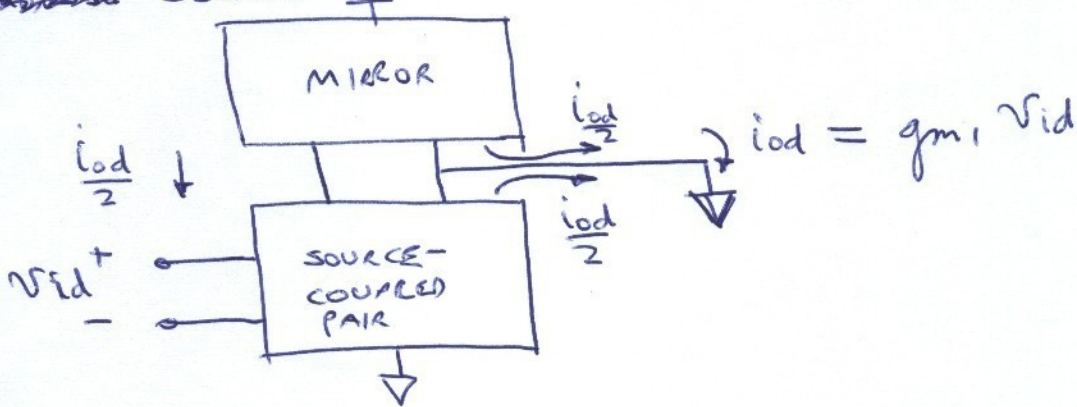• ~~Source-coupled~~ SOURCE-COUPLED PAIR COUPLED WITH CURRENT MIRROR:



• EFFECT OF OUTPUT RESISTANCE OF TRANSISTORS:

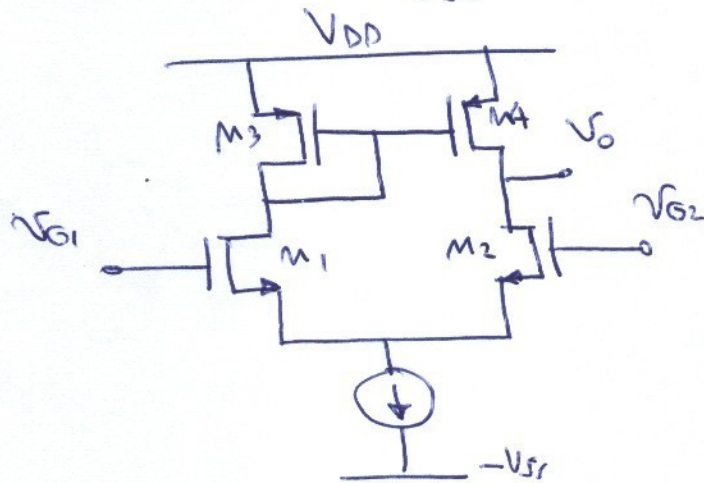- OUTPUT NO LONGER GROUNDING
- TOTAL ~~CONDUCTANCE~~ TRANSCONDUCTANCE : g_{m1}
- TOTAL RESISTANCE : $r_{o2} \parallel r_{o4}$
- VOLTAGE GAIN = $\frac{V_o}{V_{id}} = g_{m1} (r_{o2} \parallel r_{o4})$



$$g_{m1} = \frac{2 I_T}{2^n V_T} \frac{1}{\sqrt{1 + \frac{I_T}{2 I_{S1}}} + 1}$$

$$(I_{S1} = I_{S2})$$

7

$$r_{o2} = \frac{L_2}{I_D \left| \frac{\partial X_D}{\partial V_{DS}} \right|_N}, \quad r_{o4} = \frac{L_4}{I_D \left| \frac{\partial X_D}{\partial V_{DS}} \right|_P}$$

$$\frac{1}{r_{o2} \parallel r_{o4}} = \frac{I_T}{2} \left[\frac{\left| \frac{\partial X_D}{\partial V_{DS}} \right|_N}{L_2} + \frac{\left| \frac{\partial X_D}{\partial V_{DS}} \right|_P}{L_4} \right]$$

$$a_{dm} = \frac{v_o}{v_{id}} = \frac{\frac{I_T}{n V_T}}{\frac{I_T}{2} \left[\frac{\left| \frac{\partial X_D}{\partial V_{DS}} \right|_N}{L_2} + \frac{\left| \frac{\partial X_D}{\partial V_{DS}} \right|_P}{L_4} \right] \left[\sqrt{1 + \frac{I_T}{2 I_{S1}}} + 1 \right]}$$

$$= \frac{2}{n V_T} \times \frac{1}{\sqrt{1 + \frac{I_T}{2 I_{S1}}} + 1} \times \frac{1}{\frac{\left| \frac{\partial X_D}{\partial V_{DS}} \right|_N}{L_2} + \frac{\left| \frac{\partial X_D}{\partial V_{DS}} \right|_P}{L_4}}$$

- a_{dm} INCREASES WITH LOWER i_{p1}
- a_{dm} INCREASES WITH L_2, L_4 . ASSUMING $L_2 = L_4 = L$

$a_{dm} \propto L$

- MAKING $\frac{\left| \frac{\partial X_D}{\partial V_{DS}} \right|_N}{L_2} = \frac{\left| \frac{\partial X_D}{\partial V_{DS}} \right|_P}{L_4}$ (TO DISTRIBUTE OUTPUT RESISTANCES EQUALLY \rightarrow MOST BANG FOR THE BUCK)

$$a_{dm} = \frac{L_2}{n V_T \left| \frac{\partial X_D}{\partial V_{DS}} \right|_N \left[\sqrt{1 + \frac{I_T}{2 I_{S1}}} + 1 \right]}$$

$$\text{WITH: } L_4 = \frac{\left| \frac{\partial X_D}{\partial V_{DS}} \right|_P}{\left| \frac{\partial X_D}{\partial V_{DS}} \right|_N}$$

- IF LOAD CAPACITOR ADDED:

$$GBW \approx \frac{g_m}{C_L} \rightarrow \text{SAME AS WITH ACTIVELY-LOADED CS AMPLIFIER.}$$

VERIFY EXPRESSION \rightarrow

$$= \frac{2 I_{S1}}{n V_T C_L} \left(\sqrt{1 + \frac{I_T}{2 I_{S1}}} - 1 \right) \rightarrow \text{BETTER IN STRONG INVERSION}$$

COMMON-MODE REJECTION RATIO (CMRR)

$$CMRR \approx 2 g_{m1} R_T g_{m4} (r_{o2} \parallel r_{o4}) \quad (\text{NOT CONSIDERING TRANSISTOR MISMATCH})$$


$$= 2 R_T g_{m4} a_{dm}$$

$$g_{m4} = \frac{I_T}{V_T} \frac{1}{\sqrt{1+\mu_{f4}^2} + 1}$$

$$R_T = \frac{L_5}{I_T \left| \frac{\partial X_D}{\partial V_{DS}} \right|_n}$$

$$g_{m4} R_T = \frac{L_5}{V_T \left| \frac{\partial X_D}{\partial V_{DS}} \right|_n (\sqrt{1+\mu_{f4}^2} + 1)}$$

IF IMPLEMENTED WITH A SINGLE TRANSISTOR

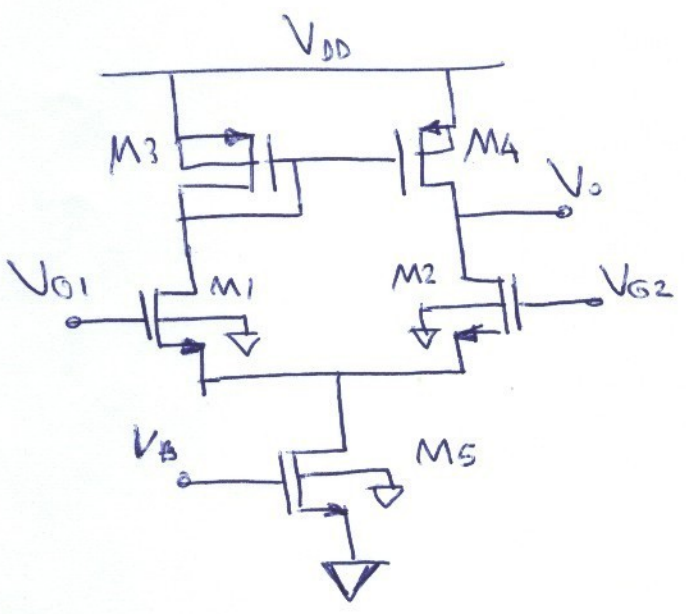

COMMON-MODE INPUT RANGE

- SIMILAR TO CMIR OF SOURCE-COUPLED PAIR, BUT REPLACE V_D WITH $(V_{DD} - V_{DS3})$.

$$|V_{DS3}| = |V_{GS3}|$$

- ALSO $V_{S_{MIN}} = V_{DS_{SAT5}}$

OUTPUT VOLTAGE RANGE

$$V_{OUT MAX} = V_{DD} - V_T \left(\sqrt{1 + i_{f4}} + 3 \right)$$

$$V_{OUT MIN} = \frac{V_{ICM} - V_{thn}}{n_n} - V_T \left[-5 + \ln \left(\sqrt{1 + i_{f1}} - 1 \right) \right]$$

OFFSET VOLTAGE

• MUST ADD TERMS DUE TO MISMATCH OF M3, M4 :

$$V_{OS} \leq \Delta V_{thn} + \Delta V_{thp} \frac{n_n}{n_p} \frac{\sqrt{1 + i_{f1}} + 1}{\sqrt{1 + i_{f4}} + 1}$$

$$+ n_n V_T \frac{\sqrt{1 + i_{f1}} + 1}{2} \left(\frac{\Delta I_{sp}}{I_{sp}} + \frac{\Delta I_{sn}}{I_{sn}} \right)$$

• FOR SIMILAR INVERSION LEVELS IN M1, M4 AND MODEKATE OR WEAK INVERSION :

$$\boxed{V_{OS} \approx \Delta V_{thn} + \Delta V_{thp}}$$

EXAMPLE

DESIGN A DIFFERENTIAL AMPLIFIER WITH A GAIN (DIFF) OF 2000 AND A CMRR OF 30 dB. CALCULATE THE INPUT COMMON-MODE RANGE AND THE OUTPUT VOLTAGE RANGE OF YOUR DESIGN. USE $L_{min} = 1 \mu m$.

$$n_n = n_p = 1.2$$

$$V_T = 26 mV$$

$$V_{thn} = -V_{thp} = 0.4 V$$

$$I_{sqn} = 100 nA$$

$$I_{sqp} = 40 nA$$

$$\left| \frac{\partial X_D}{\partial V_{DS}} \right|_n = 0.01 \frac{\mu m}{V}$$

$$\left| \frac{\partial X_D}{\partial V_{DS}} \right|_p = 0.015 \frac{\mu m}{V}$$

$$a_{dm} \approx g_{m1} (r_{o2} \parallel r_{o4})$$

$$= \frac{2 I_T}{2 n V_T} \frac{1}{\sqrt{1+i_{f1}} + 1} \cdot \frac{1}{\left(\frac{L_2}{i_{f1} I_{Dn}} \left| \frac{\partial X_D}{\partial V_{DS}} \right|_n \right)^{-1} + \left(\frac{L_4}{i_{f4} I_{Dp}} \left| \frac{\partial X_D}{\partial V_{DS}} \right|_p \right)^{-1}}$$

$= \frac{I_T}{2} \qquad \qquad \qquad = \frac{I_T}{2}$

$$= \frac{2}{n V_T (\sqrt{1+i_{f1}} + 1)} \frac{1}{\frac{\left| \frac{\partial X_D}{\partial V_{DS}} \right|_n}{L_2} + \frac{\left| \frac{\partial X_D}{\partial V_{DS}} \right|_p}{L_4}}$$

← MAKE THESE EQUAL

$$= \frac{L_2}{n V_T (\sqrt{1+i_{f1}} + 1) \left| \frac{\partial X_D}{\partial V_{DS}} \right|_n} = 2000$$

↑ CHOOSE MODERATE-WEAK INVERSION → ~~BETTER~~ LOWER OFFSET. (SHORTER L)

$$\frac{L_2}{(\sqrt{1+i_{f1}} + 1)} = 2000 n V_T \left| \frac{\partial X_D}{\partial V_{DS}} \right|_n = 0.62 \mu m$$

CHOOSING $i_{f1} = 10$ (MODERATE) → $L_2 = 2.67 \mu m$

$$L_4 = \frac{0.015}{0.01} \times 2.24 \mu m = 4.84 \mu m$$

NOTE: IN PRACTICE YOU SHOULD LEAVE SOME MARGIN (10% OR SO)

$$CMRR \approx 2 R_T g_{m4} \frac{a_{dm}}{=2000} \geq 10000$$

∴ $R_T g_{m4} \geq 2.5$ → SHOULD BE OK WITH ANY CHOICE WE MAKE.

$I_{D4} = I_{sep} \left(\frac{W}{L} \right)_4 i_{f4}$ → TO EQUALIZE GATE AREAS OF NMOS AND PMOS ADJUST i_{f4} .
 $I_{D1} = I_{sem} \left(\frac{W}{L} \right)_1 i_{f1}$ (NORMALLY i_{f4} WOULD BE CALCULATED FROM V_{OUTMAX})

SINCE $I_{D4} = I_{D1}$ $\Rightarrow i_{f4} \left(\frac{W}{L} \right)_4 = i_{f1} \left(\frac{W}{L} \right)_1$

$W_1 = \frac{A}{L_1} \Rightarrow \left(\frac{W}{L} \right)_1 = \frac{A}{L_1^2}, \left(\frac{W}{L} \right)_4 = \frac{A}{L_4^2}$

$\frac{I_{SEP}}{L_4^2} i_{f4} = \frac{I_{SAN}}{L_1^2} i_{f1} \Rightarrow i_{f4} = \frac{I_{SAN}}{I_{SEP}} \frac{L_4^2}{L_1^2} i_{f1} = 56.2$

CHOOSING $A = 10 \mu m^2 \Rightarrow \begin{cases} W_1 = 3.74 \mu m \\ W_4 \approx 2.4 \mu m \end{cases}$

$I_T = 2 I_{SEP} \left(\frac{3.74}{2.24} \right) \times 10 \approx 2.8 \mu A$

$\left(\frac{W}{L} \right)_1 = \left(\frac{W}{L} \right)_2 = \left(\frac{4.46 \mu m}{2.24 \mu m} \right)$
 $\left(\frac{W}{L} \right)_3 = \left(\frac{W}{L} \right)_4 = \left(\frac{3 \mu m}{3.36 \mu m} \right)$
 $I_T = 2.8 \mu A$

$g_{m4} = \frac{2 I_{D4}}{n V_T} \frac{1}{\sqrt{1 + 56.2^2} + 1} = 0.0105 mS$


$\therefore R_T \geq 238 k\Omega$

• CALCULATION OF INPUT-OUTPUT RANGES LEFT AS EXERCISES..

EFFECT OF CAPACITIVE LOAD

(12)

1) FREQUENCY RESPONSE

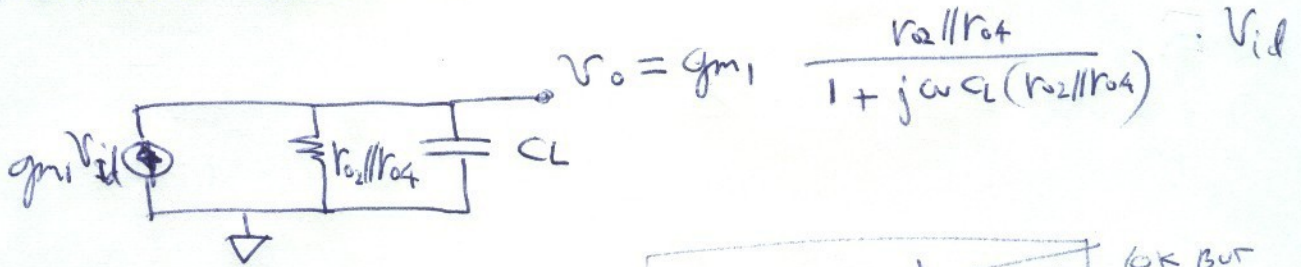

$$GBW = \frac{\omega}{2\pi} \Big|_{\left| \frac{V_o}{V_{ID}} \right| = 1} = \frac{g_{m1}}{2\pi C_L} = \frac{\frac{I_T}{n V_T C_L}}{\sqrt{1 + f_1^2} + 1}$$

(OK BUT DON'T USE IT)

$$= \frac{2 I_{S1}}{n V_T C_L} (\sqrt{1 + f_1^2} - 1) \leftarrow \text{BETTER FOR STRONG INV.}$$

$$= \frac{2 I_{S1}}{n V_T C_L} \left(\sqrt{1 + \frac{I_T}{2 I_{S1}}} - 1 \right)$$

• GIVEN GBW VALUE, 2 WAYS TO ACHIEVE IT

1. INCREASE I_{S1}
2. INCREASE f_1

• IF f_1 IS BOUNDED DUE TO a_{dm} OR V_{DS} CONSTRAINTS, WE CAN INCREASE $\left(\frac{W}{L}\right)_1$ TO INCREASE GBW.

↳ TRADE OFF →

- MOORE AREA $\Rightarrow I_{S1}$
- MOORE TAIL CURRENT

• ALSO NOTE PARASITIC DRAIN CAPACITANCE INCREASES WITH W_1

2) SLEW RATE

• LOAD CAPACITOR CAN BE CHARGED/DISCHARGED WITH I_T AT MOST.


• SLOPE IS:

$$\dot{C} = C_L \frac{dV_o}{dt} \Rightarrow \frac{dV_o}{dt} \Big|_{\max} = \frac{I_T}{C_L} \text{ SLEW RATE}$$

↳ $I_{\max} = I_T$


• OVERALL CONCLUSION: A FAST AMPLIFIER REQUIRES MORE $I_T \Rightarrow$ MORE POWER CONSUMPTION.

CASCODE AMPLIFIER

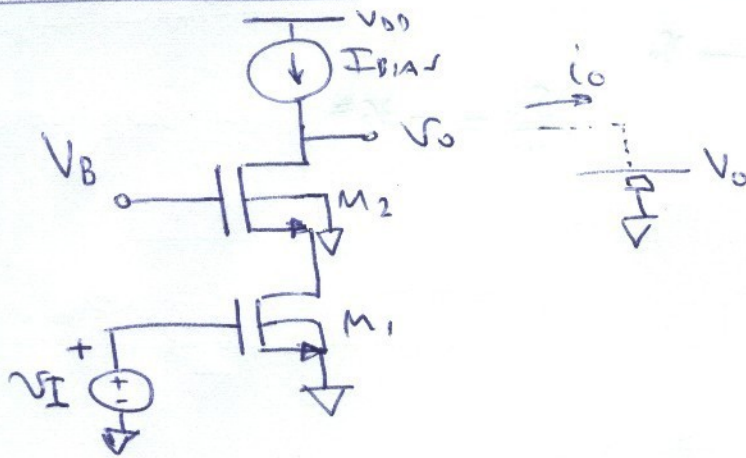

• APPROXIMATE ANALYSIS USING SHORT-CIRCUIT TRANSCONDUCTANCE AND OUTPUT RESISTANCE:

- ASSUME V_o @ OUTPUT IS FIXED

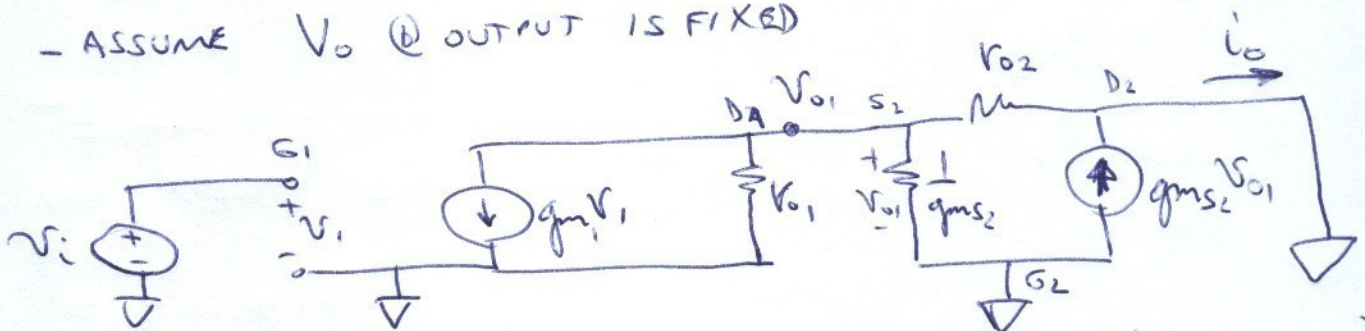

$$V_{o1} = -g_{m1} V_i \left(r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}} \right) \approx -\frac{g_{m1}}{g_{m2}} V_i \quad \left(\frac{1}{g_{m2}} \ll r_{o1}, r_{o2} \right)$$

$$i_o = g_{m2} V_{o1} + \frac{V_{o1}}{r_{o2}} \approx g_{m2} V_{o1} \quad \left(g_{m2} \gg \frac{1}{r_{o2}} \right)$$

∴ TOTAL TRANSCONDUCTANCE

$$\boxed{\frac{i_o}{V_i} \approx -g_{m1}}$$

SAME AS TRANSCONDUCTANCE OF C.S. AMPLIFIER

- NOW IF V_o IS LEFT FLOATING,

$$V_o = i_o \left(R_{out\ cascode} \parallel R_{out\ IBIAS} \right)$$


$$R_{out\ cascode} \approx (g_{m2} r_{o2}) r_{o1}$$

$$\therefore \frac{v_o}{v_i} \approx -g_{m1} \left[\underbrace{(g_{m5} r_{o2} r_{o1})}_{\text{VERY LARGE}} // \underbrace{R_{out, I_{BIAS}}}_{\text{VERY LARGE TOO}} \right]$$

VERY LARGE

IF I_{BIAS} IS ALSO CARDED, VERY LARGE TOO

EXAMPLE

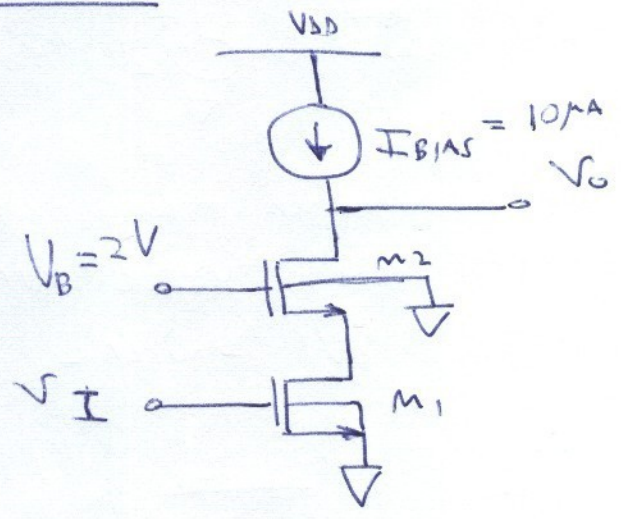

$v_o = ?$ $V_I = ?$ $V_{DS1} = ?$
 $\frac{v_o}{v_i}$
 $n = 1.25$
 $V_{th} = 0.6V$
 $I_{S1,2} = 1\mu A$ $V_{A1} = V_{A2} = 25V$
 $R_{out, I_{BIAS}} = 40M\Omega$

a) BIASING

$$I_{f1} = I_{f2} = \frac{10\mu A}{1\mu A} = 10$$

$$\frac{V_I - V_{th}}{nV_T} = \mathcal{F}(10) = 2.16 \Rightarrow V_I = 0.67V$$

$$\frac{V_B - V_{th} - V_{S2}}{nV_T} = \mathcal{F}(10) = 2.16$$


$$V_{S2} = 1.06V \Rightarrow V_{GS2} = 0.936V \quad (\text{BODY EFFECT})$$

$$g_{m1} = \frac{2I_D}{nV_T} \frac{1}{\sqrt{1+i_f} + 1} = 0.143 \text{ ms} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \frac{v_o}{v_i} = -5.720$$

$$r_{o1} = r_{o2} = \frac{V_A}{I_D} = 2.5M\Omega \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} R_{out} = 1.16\Omega$$

$$g_{m5} = n g_{m1}$$


CASCODE DIFFERENTIAL AMPLIFIER

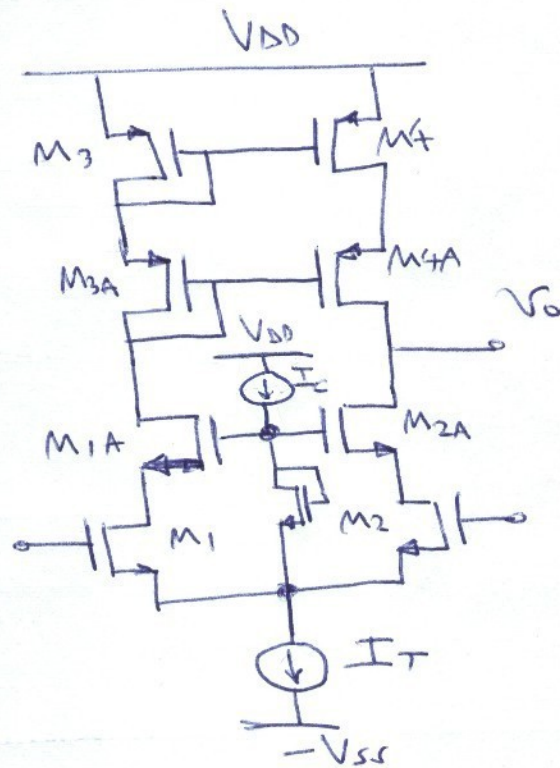

- ADVANTAGE: MORE GAIN
- DISADVANTAGE:
 - NEEDS MORE SUPPLY VOLTAGE
 - REDUCED V_{OS} , V_{ICM} RANGE.

DIFFERENTIAL AMPLIFIER WITH IMPROVED VOLTAGE RANGE

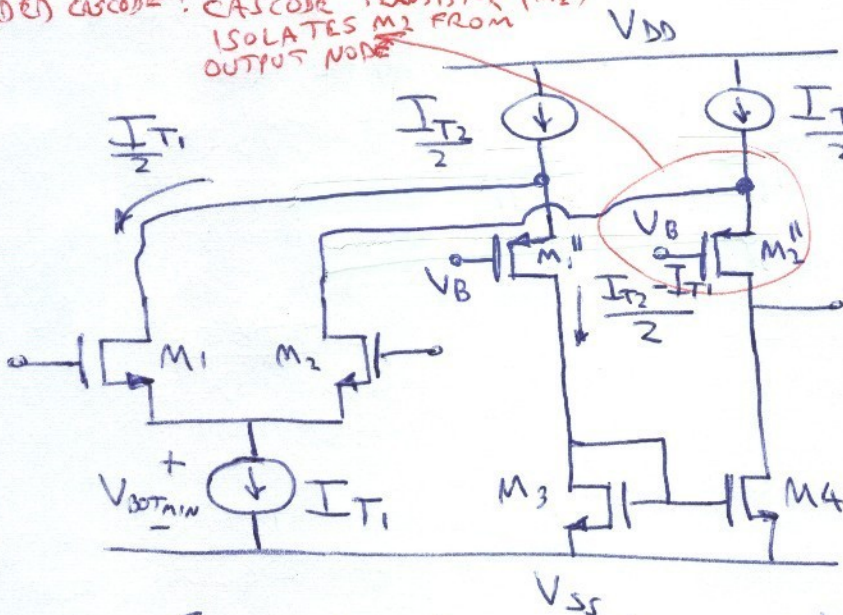FOLDED CASCODE: CASCODE TRANSISTOR (M_2'') ISOLATES M_2 FROM OUTPUT NODE




V_{TOPMIN}
 $V_{MAX} = V_B + \sqrt{I_{D2}''} / \mu_n C_{OX} W_{2}'' + V_{DSAT2}''$
 $V_{MIN} = V_{DSAT4}$

V_{ICM}


- MAX: $V_{DD} - V_{TOPMIN} + V_{DSAT1} + V_{GS1}$ ← NORMALLY CLOSE OR ABOVE V_{DD}
- MIN: $V_{BOTMIN} + V_{GS1MIN}$

- CURRENT MIRROR CAN BE CASCODED FOR EXTRA GAIN
- NEEDS EXTRA BIASING CURRENT COMPARED TO ORIGINAL.

PSRR (POWER SUPPLY REJECTION RATIO)

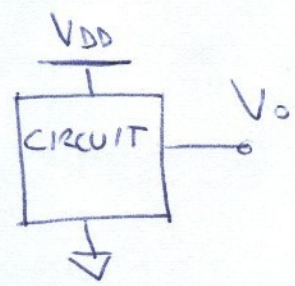
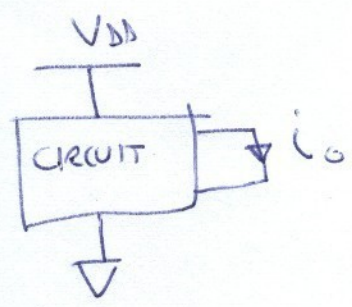
$$PSRR = 20 \log_{10} \left(\frac{\Delta V_{DD}}{\Delta V_O} \right)$$



$$PSRR = 20 \log_{10} \left(\frac{\Delta V_{DD}}{V_{DD}} \frac{I_O}{\Delta I_O} \right)$$

EXAMPLE:

