

- USUALLY NEEDS A COMPENSATION NETWORK (NOT SHOWN)
- CAN ONLY DRIVE CAPACITIVE LOADS. IF A RESISTIVE LOAD MUST BE DRIVEN (INCLUDING FEEDBACK NETWORK), AN ADDITIONAL STAGE MUST BE ADDED TO THE OUTPUT.
- MOST ON-CHIP OP-AMPS ONLY DRIVE CAPACITIVE LOADS SO THIS DESIGN IS OK.

DC CHARACTERISTICS

- INPUT - COMMON - MODE RANGE: SAME AS DIFFERENTIAL AMPLIFIER
- OUTPUT VOLTAGE RANGE:

$$-V_{SS} + |V_{DS,sat}| \leq V_o \leq V_{DD} - |V_{DS,sat}|$$

COMMON-MODE AND DIFFERENTIAL GAIN

- GAINS ARE EQUAL TO THE PRODUCT OF DIFF. AMP. GAIN TIMES COMMON-SOURCE STAGE GAIN.
- CMRR EQUAL TO CMRR OF DIFFERENTIAL AMPLIFIER (SINCE THE CS. GAIN IS CANCELLED IN $\frac{a_{dm}}{a_{cm}}$).

(18)

$$a_{dm} \approx g_{m1} (r_{o2} \parallel r_{o4}) g_{m6} (r_{o6} \parallel r_{o7})$$

$$a_{dm} \approx \left(\frac{2}{nV_T} \right)^2 \frac{1}{\sqrt{1+i_{f1}} + 1} \cdot \frac{1}{\sqrt{1+i_{f6}} + 1} \cdot \frac{1}{\left| \frac{dX_D}{dV_{DS}} \right|_P + \left| \frac{dX_D}{dV_{DS}} \right|_N} \cdot \frac{1}{\left| \frac{dX_D}{dV_{DS}} \right|_N + \left| \frac{dX_D}{dV_{DS}} \right|_P}$$

MODERATE/WEAK INVERSION
MODERATE/STRONG INVERSION (STABILITY)
USUALLY MATCHED

OFFSET VOLTAGE

- RANDOM OFFSET COMPONENT: SAME AS DIFF. AMPLIFIER
- SYSTEMATIC OFFSET:

$$V_{DS6} = V_{DS4} = V_{DS3} \rightarrow \text{IF } M_3, M_4 \text{ AND } M_6 \text{ DESIGNED TO HAVE SAME INVERSION LEVEL (} i_{f3} = i_{f4} = i_{f6} \text{)}$$

∴ SYSTEMATIC OFFSET: ACTUAL OUTPUT ↔ IDEAL OUTPUT WITH $V_{ID} = 0$

$$V_{OS} = \frac{(V_{GS3} - V_{SS}) - \frac{(V_{DD} - V_{SS})}{2}}{a_{dm}}$$

$$i_{f3} = i_{f4} = i_{f6}$$

$$I_{D3} \frac{I_T}{I_{D3}^2 \left(\frac{W}{L} \right)_3} = \frac{I_T}{I_{D4}^2 \left(\frac{W}{L} \right)_4} = \frac{I_{D6}}{I_{D6} \left(\frac{W}{L} \right)_6}$$

$$I_{D6} = I_{D7} = \frac{I_{DS}}{\left(\frac{W}{L} \right)_5} \left(\frac{W}{L} \right)_7 = I_T \frac{\left(\frac{W}{L} \right)_7}{\left(\frac{W}{L} \right)_5}$$


$$2 \frac{I_T}{\left(\frac{W}{L} \right)_3} = \frac{I_T \left(\frac{W}{L} \right)_7}{\left(\frac{W}{L} \right)_6 \left(\frac{W}{L} \right)_5} \Rightarrow$$

$$\frac{1}{2} \frac{\left(\frac{W}{L} \right)_6}{\left(\frac{W}{L} \right)_3} = \frac{\left(\frac{W}{L} \right)_7}{\left(\frac{W}{L} \right)_5}$$

FOR SAME CURRENT DENSITY.


OTHER OPERATIONAL AMPLIFIER TOPOLOGIES

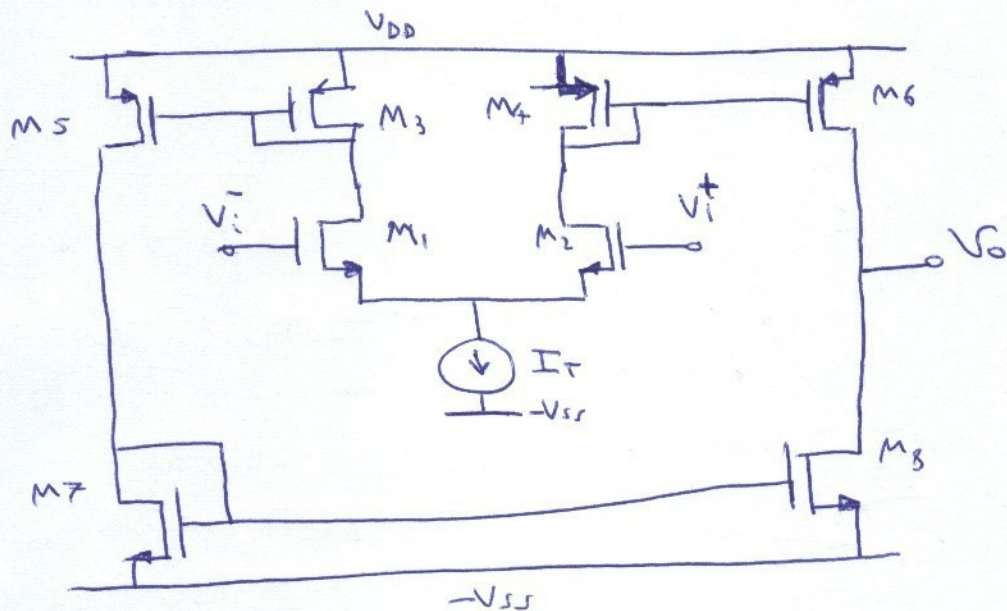- 1) DIFFERENTIAL AMPLIFIER STAGE → HAS REDUCED OUTPUT VOLTAGE RANGE
- 2) RANGE CAN BE INCREASED USING A FOLDED CASCODE CONFIGURATION OR:
- 3) SYMMETRIC OPERATIONAL AMPLIFIER



- MORE OUTPUT VOLTAGE RANGE
- BETTER FREQUENCY RESPONSE IF SOURCE HAS HIGH IMPEDANCE.
- NORMALLY $M_5 = M_3 = M_4 = M_6$, $M_1 = M_2$, $M_7 = M_8$

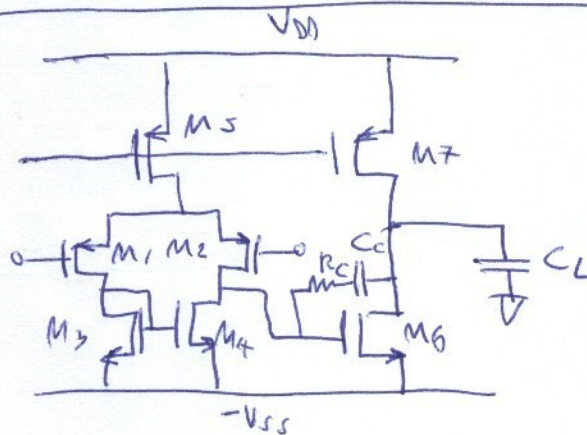COMPENSATION NETWORK FOR 2-STAGE OP. AMP. SUMMARY



$$C_c = \frac{g_{m1}}{g_{m6}} C_L$$

(MAKE $g_{m6} > g_{m1}$)

$$R_c \approx \frac{1}{g_{m6}}$$

THIS GIVES $PM \approx 45^\circ$