

EXAMPLE: DESIGN A 2-STAGE OP. AMP FOR THE FOLLOWING


SPECIFICATIONS: $V_{DD} = V_{SS} = 1.5V$, $C_L = 1pF$, $\omega_0 \geq 2\pi \times 100MHz$
 $a_{dm} \geq 1000$, V_o SWING $> 2V$, $V_{Icm} = 0V$, $PM \approx 45^\circ$

PARAMETERS

$I_{sqn} = 80nA$, $I_{ser} = 20nA$
 $V_{thn} = 0.65V$, $V_{thp} = -0.65V$
 $n_n \approx n_p \approx 1.2$
 $\left| \frac{\partial X_0}{\partial V_{bs}} \right|_{n-p} \approx 0.06 \frac{\mu m}{V}$

SOLUTION:

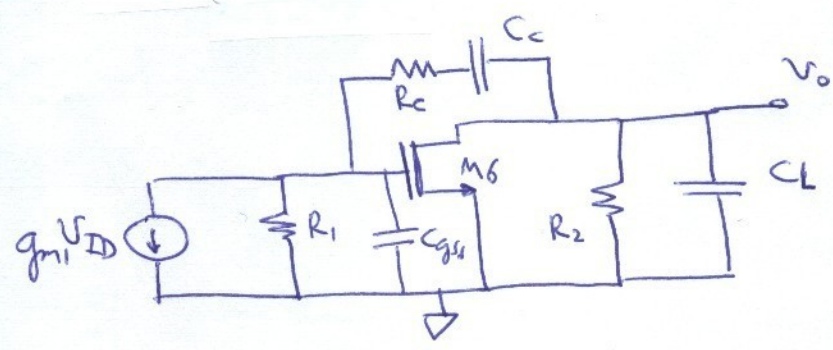1. SOME MORE DETAILS ABOUT FREQUENCY RESPONSE/STABILITY.



- ASSUME $C_c \gg C_{gs6}$
- $R_1 = r_{o4} || r_{o2}$
- $R_2 = r_{o6} || r_{o7}$

POLES:

$P_1 \approx -\frac{1}{g_{m6} R_2 R_c C_c}$ DOMINANT POLE


$P_2 \approx -\frac{g_{m6}}{C_L}$ ← THIS ENDS UP BEING @ ω_0 LOCATION

$P_3 \approx -\frac{1}{R_c C_{gs6}}$ VERY HIGH FREQ. (NO EFFECT)

$z = \frac{1}{\left(\frac{1}{g_{m6}} - R_c\right) C_c}$
 MAKE $R_c = \frac{1}{g_{m6}} \Rightarrow$ ZERO MOVES TO ∞

\therefore FOR $\omega_0 \geq 2\pi \times 100MHz \Rightarrow -2\pi \times 100MHz \geq -\frac{g_{m6}}{C_L}$
 $g_{m6} \geq \underline{0.628 mS}$
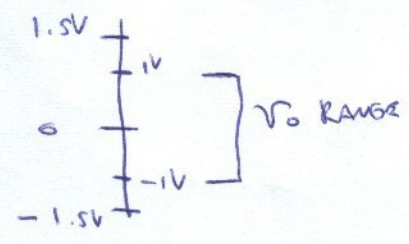
$$g_{m6} = \frac{2 I_5}{n V_T} \left(\sqrt{1 + i_{f6}} - 1 \right) \rightarrow \text{WILL TRY SELECTING } i_{f6} = 100 \text{ TO REDUCE AREA.}$$



$$\Rightarrow V_{DSAT6} \leq 0.5V$$

$$V_{DSAT6} = V_T \left[\sqrt{1 + i_{f6}} + 3 \right]$$

$$i_{f6 \text{ MAX}} = 262 \quad (\text{WOULD BE OK WITH } 100)$$

LOW-FREQ. GAIN: ASSUME L IS THE SAME FOR ALL TRANSISTORS

$$a_{dm} \approx \frac{1}{(n V_T)^2} \frac{1}{\sqrt{1 + i_{f1}} + 1} \frac{1}{\sqrt{1 + i_{f6}} + 1} \frac{L^2}{2 \left| \frac{\partial X_D}{\partial V_{DS}} \right|^2}$$

• WE'LL TRY USING MODERATE INVERSION FOR M_1, M_2 : $i_{f1} = 10$

$$\therefore L_{MIN} = n V_T \left| \frac{\partial X_D}{\partial V_{DS}} \right| \sqrt{2 (\sqrt{1 + i_{f1}} + 1) (\sqrt{1 + i_{f6}} + 1)} \sqrt{a_{dm}}$$


$$\approx 0.58 \mu m \Rightarrow \text{TAKE } L = 1 \mu m \Rightarrow a_{dm} \approx 3000 \quad (\text{SHOULD BE OK})$$

• MUST CHOOSE INVERSION LEVEL OF MIRROR TRANSISTORS M_5, M_7 .

CHOOSE NEAR STRONG INVERSION (SAVE AREA)

$$i_{f5} = i_{f7} = 100$$

• CHECK V_{icm} IS OK:

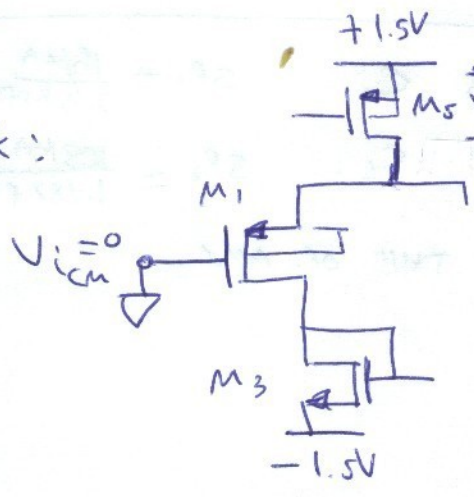

$$V_{S \text{ MAX}}: 1.5V - |V_{DSAT5}| - |V_{DS7}|$$

$$\text{SUM} < 1.5V$$

MIN: SHOULD BE OK, LEFT AS EXERCISE

• FIND $|V_{GS1}|$:

$$|V_p| = \frac{V_G - V_{th1}}{n} = 0.71V$$

1.5V

$$\frac{|V_p| - |V_s|}{V_T} = f(i_{f1}) = 2.15 \Rightarrow |V_s| = 0.65V = |V_{DS1}|$$

REFERS TO VDD

∴ WE HAVE ENOUGH ROOM TO KEEP M_S ACTIVE WHEN $V_{icm} = 0V$

• FIND $(\frac{W}{L})$ FOR ALL TRANSISTORS ⇒ MUST SELECT TAIL CURRENT

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 20 \Rightarrow I_{D1} = \frac{I_{sap}}{20} = \frac{20nA}{20} = 1nA$$

$i_{f1} = 10$

$$I_T = 2 I_{D1} = 2nA$$

$$\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 = \frac{4nA}{80nA \times 100} = 0.5 \Rightarrow \text{TOO SMALL} \Rightarrow \text{DOUBLE } I_T$$

$i_{f3} = i_{f4} = i_{f6}$

$$I_T = 16nA \Rightarrow \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 40$$

$$\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4 = 1$$

$$\left(\frac{W}{L}\right)_5 = \frac{16nA}{20nA \times 100} = 8$$

$$q_{m5} = 0.628 ns = 2 \times \frac{I_{sen} (\frac{W}{L})_6}{n V_T} (\sqrt{1+100} - 1)$$

$$\left(\frac{W}{L}\right)_6 = 13.5 \Rightarrow I_{D6} = 80nA \times 13.5 \times 100 = 108nA$$

(COULD USE SOME MARGIN)


$$\left(\frac{W}{L}\right)_7 = \frac{108nA}{20nA \times 100} = 54$$

$$R_c = 1592 \Omega$$

$$C_c = \frac{q_{m1}}{q_{m6}} C_L = \frac{0.118 ns}{0.628 ns} \times 1pF = 0.187 pF$$

(MAY NEED TO CONSIDER C_{gd6} HERE)

22'

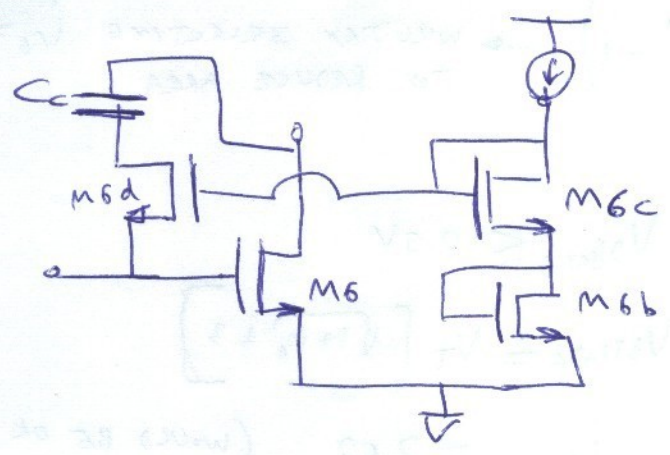


$$I_{D6d} = 0 \Rightarrow i_{f6d} = i_{r6d}$$

$$\frac{V_{P6d} - V_{G6}}{V_T} = \frac{V_{P6d} - V_{G6}}{V_T}$$

$$g_{mS6d} = g_{mD6d} \quad (\text{SAME AS } M6)$$

$$g_{mG6d} = 0$$

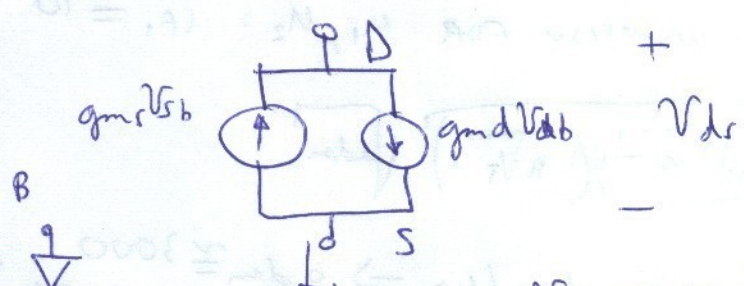

$$i_o = -g_{mS} V_{sb} + g_{mD} V_{db} = g_{mS} (V_{db} - V_{sb})$$

$$= g_{mS} V_{ds}$$

∴ M6d EQUIVALENT TO A RESISTOR

$$R_{eq} = \frac{1}{g_{mS6}} = \frac{1}{n g_{m6}}$$

SLEW RATE:

DUE TO C_c : $SR_1 = \frac{16 \mu A}{0.187 PF} = 85 \frac{V}{\mu s}$ ← LIMITING FACTOR

DUE TO C_L : $SR_2 = \frac{108 \mu A}{1.187 PF} = 90 \frac{V}{\mu s}$ ← ONLY GOING UP

$SR \approx 85 \frac{V}{\mu s}$ FOR THIS OP. AMP.