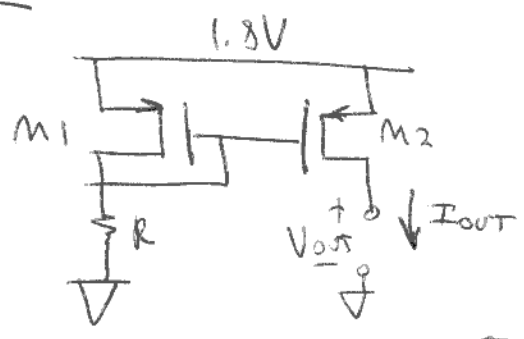


- ALSO TUNNELING @ GATE-DRAIN OVERLAP REGION TO BULK : GATE-INDUCED DRAIN LEAKAGE (GIDL)
- IMPACT IONIZATION CURRENTS : ELECTRON-HOLES PAIRS CREATED THAT PRODUCE A D-B CURRENT. DOES NOT HAPPEN IN LOW-VOLTAGE TECHNOLOGIES.

MORE ON CURRENT MIRRORS (INTRODUCE CURRENTS MIRRORS PAGE 21)

EXAMPLE : PROBLEM 5.1



$V_{th} = -0.4V$
 $I_S = 1\mu A$
 $n = 1.25$
 $M_1 = M_2$

- CALCULATE R FOR $I_{OUT} = [0.5 \text{ TO } 50] \mu A$
- " " $V_{OUT} \text{ MAX}$
- $V_A = 5V$, CALCULATE ΔI FOR $V_{OUT} = 0$
- $V_A = 0V$, " " ΔI FOR $V_{th2} = V_{th1} \pm 10mV$

e) $I_{OUT} = I_{D2} \approx I_S$ if (ASSUME $i_f \gg i_r$)

$\therefore i_f = \frac{I_{OUT}}{I_S} = [0.5 \text{ TO } 50]$

$\frac{V_P}{V_T} = \Phi(i_f) = \sqrt{1+i_f} - 2 + \ln(\sqrt{1+i_f} - 1) = [-2.28, 6.96]$

$V_S = 0$

$V_P = \frac{V_G - V_{th}}{n} \Rightarrow V_G = (V_{th} + nV_P) = [-0.33V, -0.63V]$

$$R = \frac{1.8V + V_G}{I_{OUT}} = [2.94M\Omega, 234k\Omega]$$

b) $V_{DSSAT} \approx V_T (\sqrt{1+i_f} + 3)$ (USING $\beta = 0.018$)
 FROM NOW ON
 $V_{DSSAT} \approx V_T (\sqrt{1+i_f} + 3.6)$
 $\beta = 0.01$

$$V_{DSSAT} \approx [-0.11V, -0.264V]$$

$\therefore V_{OUT MAX} = [1.69V, 1.54V]$

c) $r_{ds} = \frac{V_A}{I_D}$

$$\Delta I = \frac{\Delta V}{r_{ds}} = \frac{1.8V - |V_G|}{V_A} \times I_D$$

$$\Delta I = [0.15mA, 11.7\mu A]$$

30% 23% ← NOT MUCH DIFFERENCE

d) $V_{G1} = V_{G2}$ BUT $V_{P1} \neq V_{P2}$

ASSUME $I_{D1} = [0.5 \rightarrow 50\mu A] \Rightarrow V_{G1} = [-0.33V, -0.63V]$
 $\pm 10mV$

$$V_{P2} = \frac{V_{G1} - V_{th2}}{n} = V_{P1} + \frac{\Delta V_{th}}{n}$$

• 2 WAYS OF SOLVING THIS:

1. USE $i_f = \mathcal{F}^{-1}\left(\frac{V_P}{V_T}\right)$

2. USE LINEAR APPROXIMATION:

$$\frac{\Delta V_P}{V_T} \approx \frac{d\mathcal{F}(i_f)}{di_f} \Delta i_f$$

$\mathcal{F}(i_f = 0.5) \quad i_f = 50$

$$\frac{d\mathcal{F}}{di_f} = \frac{1}{2\sqrt{1+i_f}} \left[1 + \frac{1}{\sqrt{1+i_f} - 1} \right] = [2.22, 0.081]$$

$$= \frac{1}{2(\sqrt{1+i_f} - 1)}$$


VERY SIMPLE!

$$\Delta i_f = \frac{\Delta V_p}{V_T \left(\frac{\partial f}{\partial i_f} \right)} = \left[\frac{0.0036}{V_T}, \frac{0.099}{V_T} \right]$$

$$\Delta I_D = I_S \Delta i_f \approx \left[0.14 \mu A, 3.81 \mu A \right]$$


28% 7.6%

← LESS EFFECT NEAR STRONG INVERSION


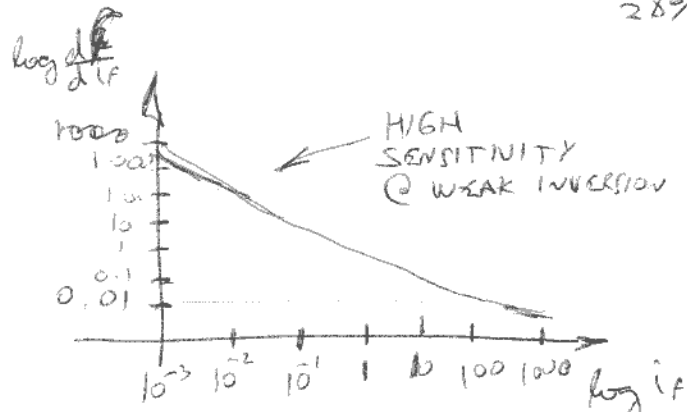


∴ MATCHING MORE DIFFICULT IN WEAK INVERSION.
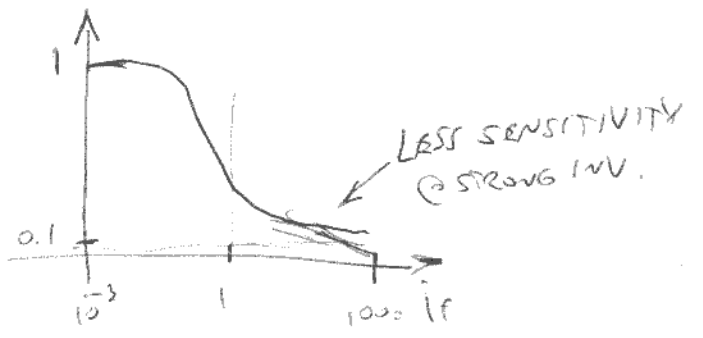
$$\frac{\Delta i_f}{i_f} = \frac{\Delta V_p}{V_T i_f \left(\frac{\partial f}{\partial i_f} \right)} \propto \frac{1}{i_f \frac{\partial f}{\partial i_f}}$$



CURRENT MIRROR GAIN

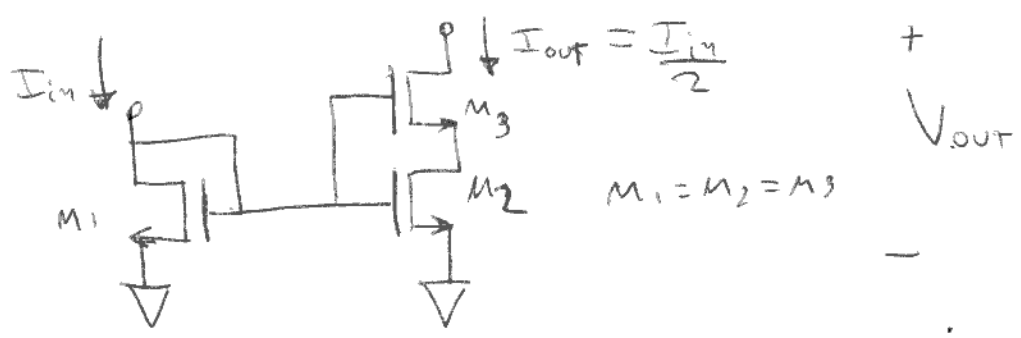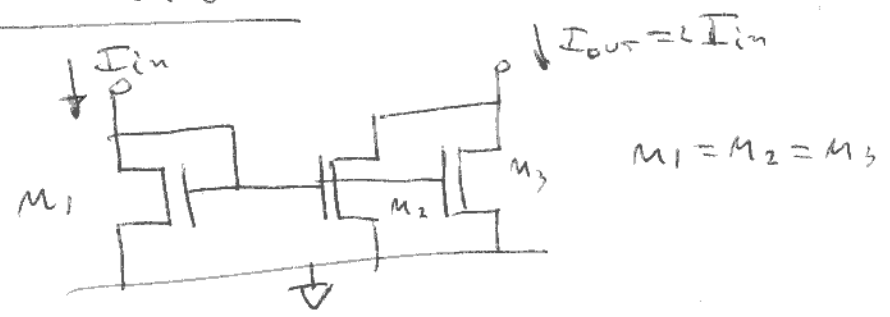

• $M_1 = M_2$ AND $V_{G1} = V_{G2} \Rightarrow i_{f1} = i_{f2}$


• $i_{r2} = i_{f3}$ SINCE $V_{D2} = V_{S3}$ AND $M_2 = M_3$ (M_2 TRIODE)

• ASSUMING V_{OUT} IS HIGH ENOUGH, $i_{r3} \approx 0$ (M_3 ACTIVE REGION)


$\therefore i_{f3} = i_{f2} - i_{r2} = i_{f2} - i_{f3}$

$\therefore i_{f3} = \frac{i_{f2}}{2} = \frac{i_{f1}}{2} \Rightarrow I_{OUT} = \frac{I_{IN}}{2}$

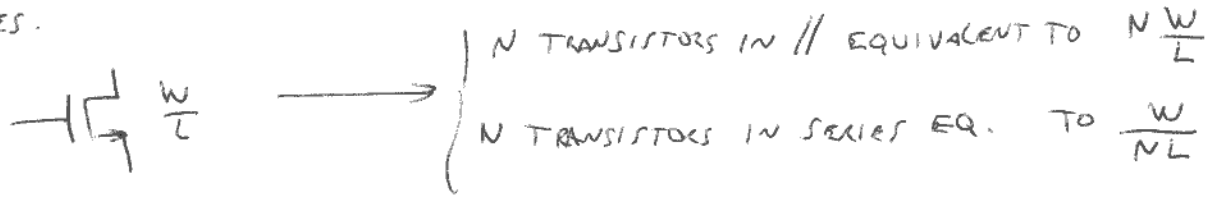• THE SAME WORKS FOR ANY NUMBER OF TRANSISTORS IN SERIES.



EXAMPLE: PROBLEM 5.4

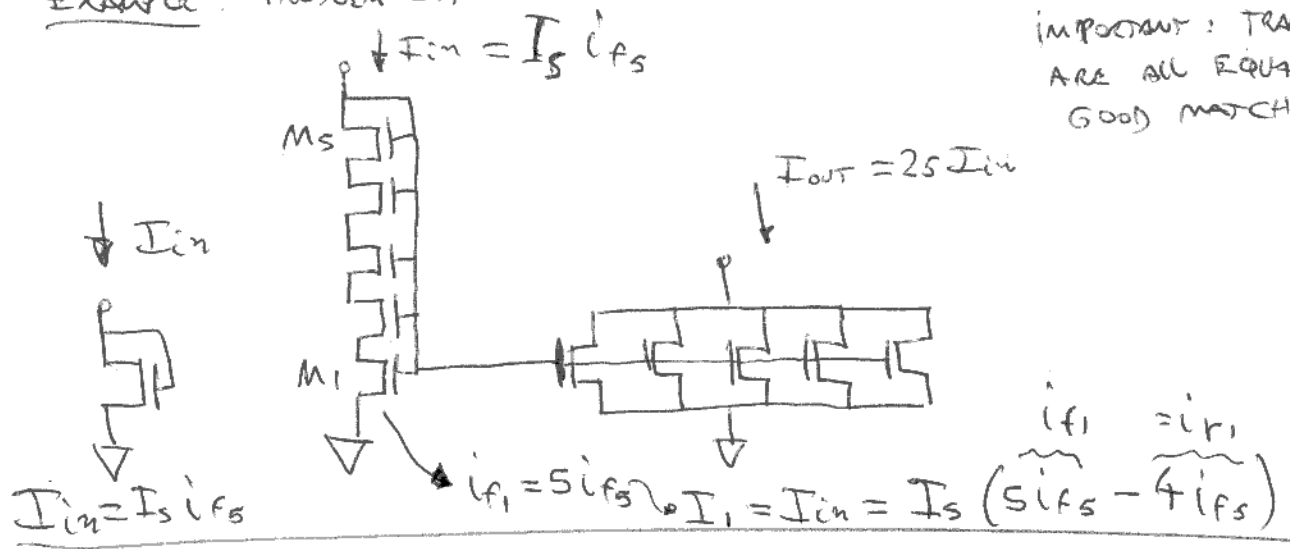

CASCODE CURRENT MIRRORS: TO GET HIGH OUTPUT RESISTANCE

