
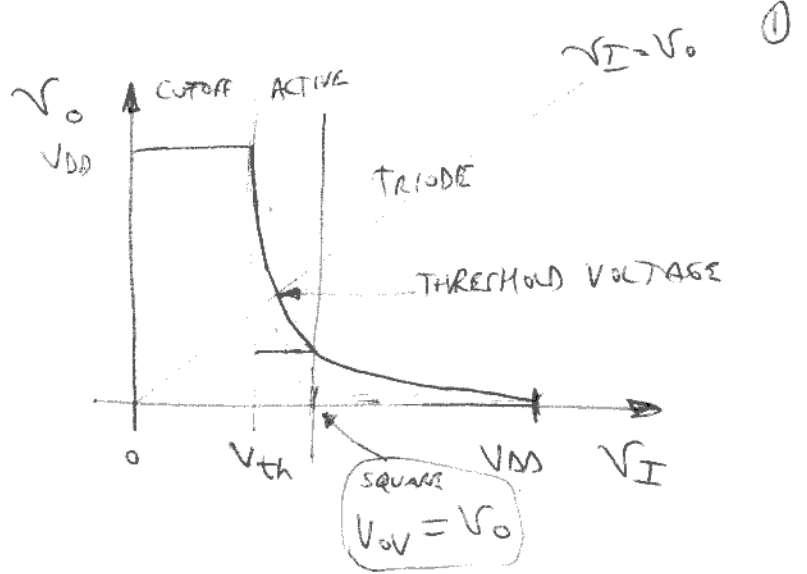


INVERTERS

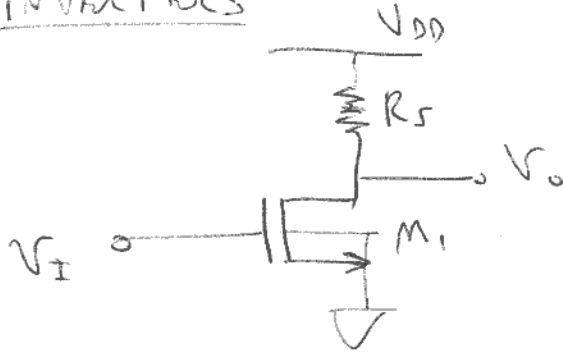

$$V_O = V_{DD} - i_D R_S$$

$$V_O = V_{DD} - \frac{k'}{2} \frac{W}{L} N_{OV}^2 R_S \quad (\text{ACTIVE MODE}) \quad (\text{SINCE } V_{GS} = V_{DS})$$



$$V_O = V_I \Rightarrow V_{OV} = V_I - V_{TH} = V_O - V_{TH}$$


$$V_O = V_{DD} - \frac{k'}{2} \frac{W}{L} (V_O - V_{TH})^2 R_S \rightarrow \text{SOLVE QUADRATIC EQ.}$$

$$\frac{\partial V_O}{\partial V_I} = -\frac{k'}{2} \frac{W}{L} (V_I - V_{TH}) R_S = -k' \frac{W}{L} R_S V_{OV} \quad (\text{SMALL-SIGNAL GAIN})$$

$\left| \frac{\partial V_O}{\partial V_I} \right| \gg 1$ FOR SIGNAL REGENERATION
(INTRODUCE SIMPLIFIED S.S. MODEL HERE)

CMOS INVERTER

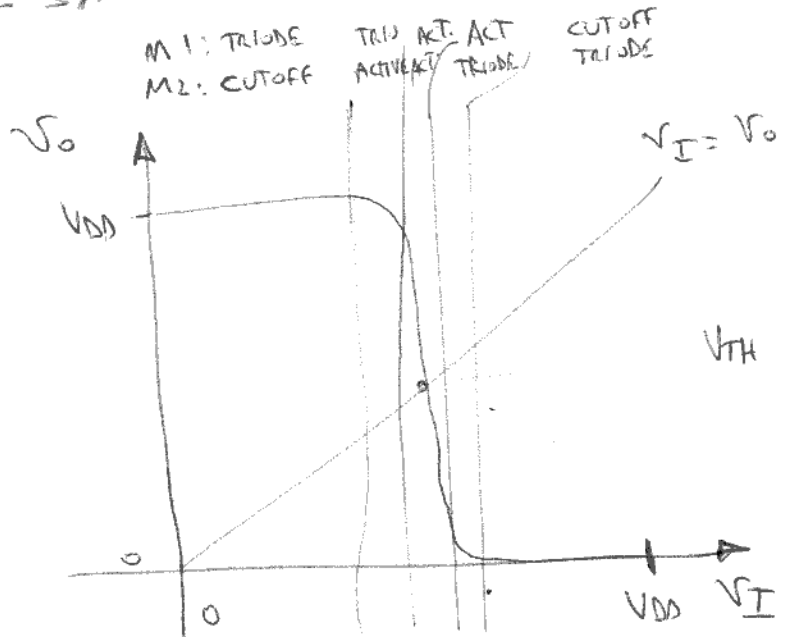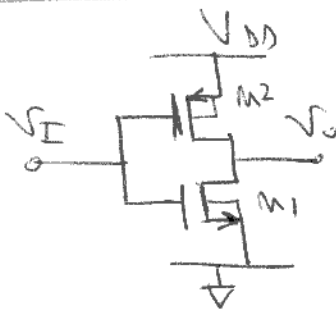

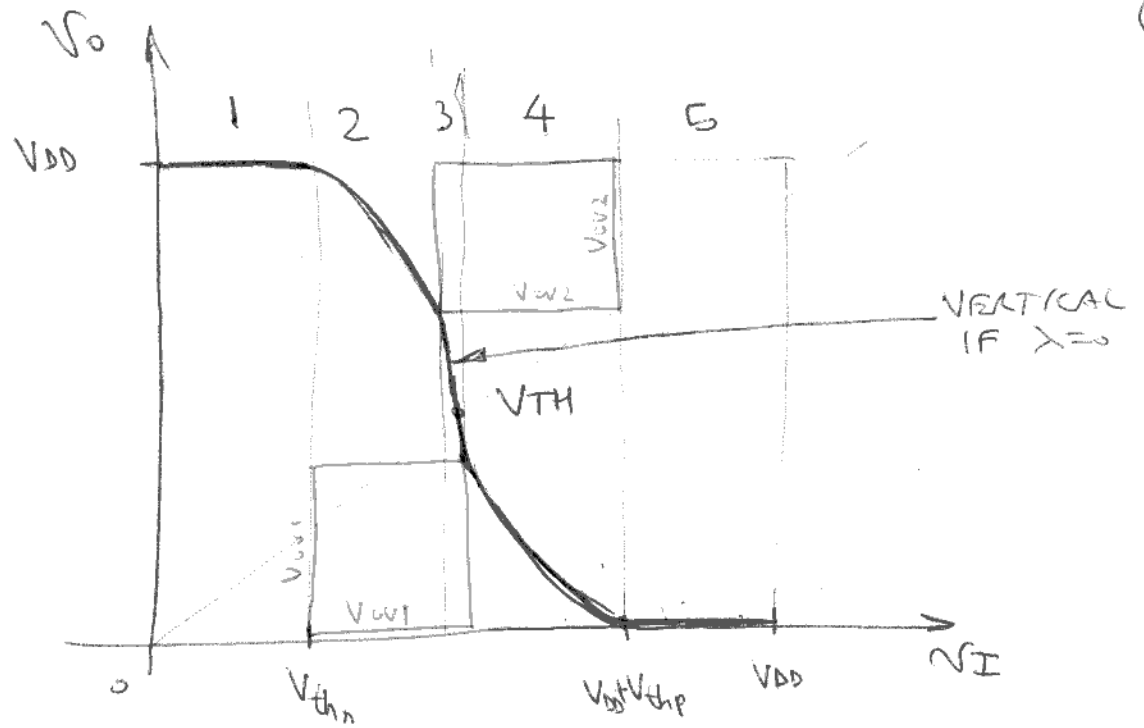

	M1	M2
1.	CUTOFF	TRIODE
2.	ACTIVE	TRIODE
3.	ACTIVE	ACTIVE
4.	TRIODE	ACTIVE
5.	TRIODE	CUTOFF

NOTE: M1, M2 ARE BOTH ACTIVE @ V_{TH} SINCE $V_{DS} = V_{GS}$
 FOR BOTH TRANSISTORS AT THAT POINT.

$$I_{D1} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_1 (V_{TH} - V_{thn})^2$$

$$I_{D2} = \frac{\mu_p C_{ox}}{2} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{th} + V_{thp})^2$$

$$I_{D1} = I_{D2} \rightarrow \text{FIND } V_{th}$$

$$V_{th} = \frac{V_{thn} + (V_{DD} + V_{thp}) \sqrt{\mu_p \left(\frac{W}{L}\right)_2 / \mu_n \left(\frac{W}{L}\right)_1}}{1 + \sqrt{\mu_p \left(\frac{W}{L}\right)_2 / \mu_n \left(\frac{W}{L}\right)_1}}$$

EXAMPLE

$$\mu_n' = 180 \frac{\mu\text{A}}{\text{V}^2}$$

$$V_{thn} = 0.76 \text{ V}$$

$$\frac{W}{L} = \frac{1.2 \mu\text{m}}{0.6 \mu\text{m}} \text{ FOR BOTH TRANSISTORS}$$

$$\mu_p' = 40 \frac{\mu\text{A}}{\text{V}^2}$$

$$V_{thp} = -0.66 \text{ V}$$

$$V_{DD} = 3.3 \text{ V}$$

$$V_{TH} = \frac{0.76 \text{ V} + (3.3 \text{ V} - 0.66 \text{ V}) \sqrt{\frac{40 \frac{\mu\text{A}}{\text{V}^2} \cdot \frac{1.2}{0.6}}{180 \frac{\mu\text{A}}{\text{V}^2} \cdot \frac{1.2}{0.6}}}}{1 + \sqrt{\frac{40 \frac{\mu\text{A}}{\text{V}^2}}{180 \frac{\mu\text{A}}{\text{V}^2}}} = 1.55 \text{ V} \quad (\text{NOT TOO BAD})$$

NOTE: $\frac{V_{DD}}{2} = 1.65 \text{ V}$

IF $V_{thn} = |V_{thp}|$ AND $\mu_n = \mu_p \Rightarrow V_{TH} = \frac{V_{DD}}{2}$ NOISE MARGIN MAXIMIZED.

FOR CMOS: $\left\{ \begin{array}{l} NMH = V_{DD} - V_{TH} \\ NML = V_{TH} \end{array} \right.$

• FOR ASSIGNMENT \rightarrow CONVERT ANALOG - DIGITAL WITH SPECIFIC V_{TH} .