

# ENGI 2132 Electronics II

## Practice Problems for Final Exam — Fall 2017

- Closed notes, closed books. No electronic devices allowed except non-programmable calculator
- Show calculation steps for full marks

### Equations

$$P_{DC} = \frac{2V_{CC}V_O}{\pi R_L}$$

$$P_{D,max} = \frac{2V_{CC}^2}{\pi^2 R_L}$$

$$i_C \approx I_S \exp(v_{BE}/V_T)$$

$$g_m = I_C/V_T$$


$$r_\pi = \beta/g_m$$

$$r_e = \alpha/g_m = \beta/((\beta + 1)g_m)$$

$$r_o = V_A/I_C$$

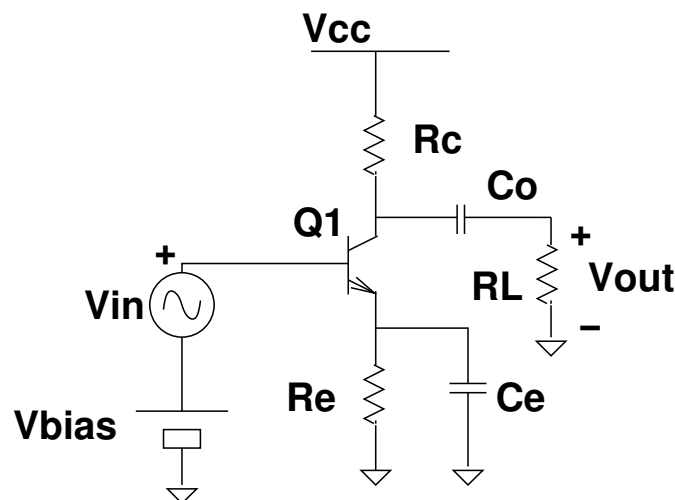
### Problems

- In the following circuit,  $V_{CC} = 12 \text{ V}$ ,  $R_E = 40 \Omega$ ,  $R_C = 80 \Omega$ ,  $R_L = 200 \Omega$ . The desired collector current in  $Q_1$  is 60 mA. Assume  $\beta$  of  $Q_1$  is very large,  $V_{BE,on} = 0.7 \text{ V}$  and  $V_{CE,sat} = 0.4 \text{ V}$ .
  - Calculate the required value for  $V_{BIAS}$  and the operating point of  $Q_1$ .
  - Calculate maximum positive and negative voltage swing at load resistor.
  - Calculate DC supply power, load power and power efficiency for maximum sinusoidal output.
  - $Q_1$  has a TO-220 package with  $\theta_{JA} = 70^\circ\text{C/W}$ ,  $T_{MAX} = 150^\circ\text{C}$  and the ambient temperature is  $27^\circ\text{C}$ . Is a heat sink required or not? Justify your answer.




2. In the following circuit,  $R_S = 1\text{ k}\Omega$ ,  $v_S = 1\text{ V}$  and the operational amplifier is fed with supply voltages  $\pm 12\text{ V}$ .

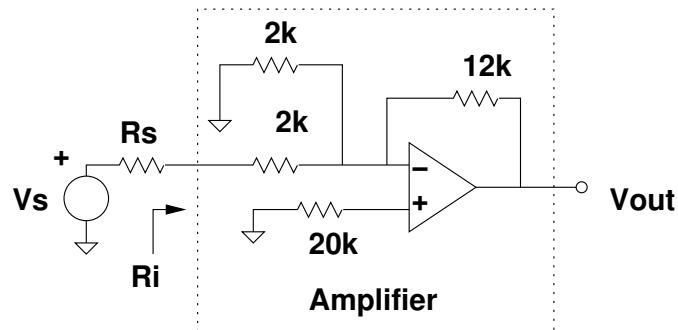- (a) Is the feedback positive or negative?
- (b) Calculate the input resistance of the amplifier ( $R_i$ )
- (c) Calculate the current through  $R_S$
- (d) Calculate  $v_{OUT}$
- (e) Calculate  $v_{OUT}$  if  $v_S$  is increased to  $5\text{ V}$




3. In the following circuit,  $R = 10\text{ k}\Omega$  and the operational amplifier is fed with supply voltages  $\pm 12\text{ V}$ .

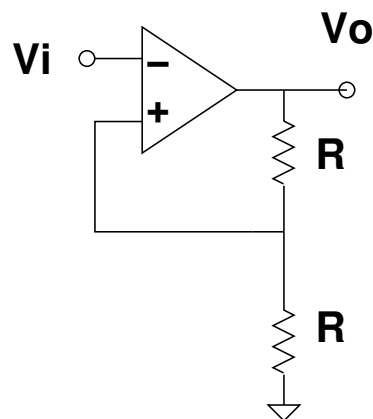- (a) Is the feedback positive or negative?
- (b) Plot  $v_O$  vs.  $v_I$
- (c) Sketch the input and output voltages if  $v_I$  is a sine wave with a peak of  $10\text{ V}$ .




4. In the circuit below,  $R_1 = 1\text{ k}\Omega$ ,  $R_2 = 50\text{ k}\Omega$  and the circuit is driven with an ideal voltage source (zero internal resistance).

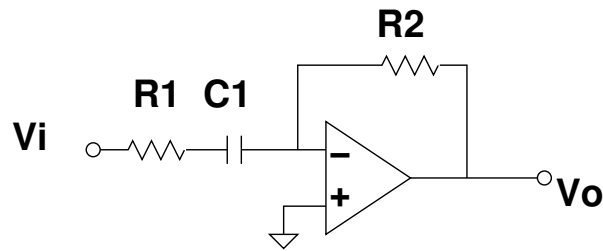- (a) Calculate  $C_1$  to obtain a gain with magnitude 10 at a frequency of  $10\text{ kHz}$ .
- (b) Is this a high-pass or a low-pass filter?
- (c) Calculate the  $-3\text{ dB}$  cutoff frequency of the circuit.



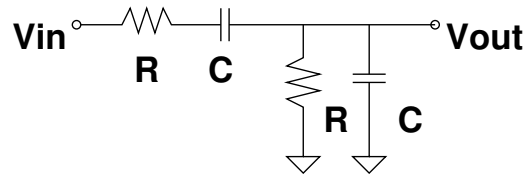
5. Refer to the network shown below.

- Symbolically derive the transfer function  $V_{out}/V_{in}$
- If this network is used to build a feedback oscillator, explain how the oscillation frequency is determined (from your result in (a)) and what is the required amplifier gain.
- Show an schematic diagram of the feedback oscillator that uses this network.




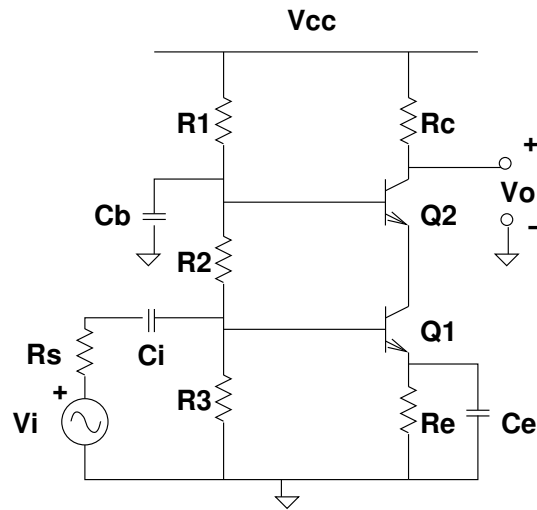6. In the circuit below,  $V_{CC} = 15\text{ V}$ ,  $R_S = 300\ \Omega$ ,  $R_E = 1.5\text{ k}\Omega$  and  $R_C = 4\text{ k}\Omega$ . The bipolar transistors are equal with  $\beta = 160$ ,  $V_A = \infty$ ,  $V_{BE,on} = 0.7\text{ V}$  and  $V_{CE,sat} = 0.3\text{ V}$ . The bipolar transistors are to be biased with  $I_C = 1.5\text{ mA}$  and  $V_{CE1} = 1.5\text{ V}$ .

- Design  $R_1$ ,  $R_2$  and  $R_3$ .
- Draw the small-signal circuit of the amplifier. Assume capacitors are short-circuits at the frequency of operation.
- Calculate the overall voltage gain  $v_o/v_s$  at mid-frequencies.



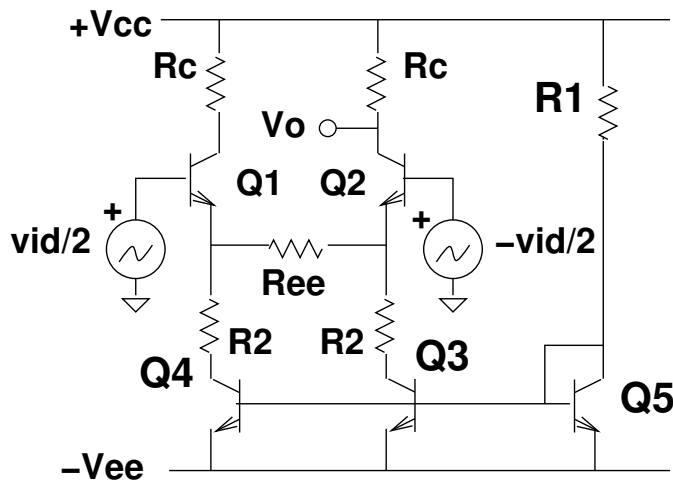7. In the circuit below,  $V_{CC} = 12\text{ V}$ ,  $V_{EE} = 6\text{ V}$ ,  $R_2 = 50\ \Omega$  and  $R_C = 3\text{ k}\Omega$ . The bipolar transistors are all equal with  $\beta = 200$ ,  $V_A = 80\text{ V}$ ,  $V_{BE,on} = 0.7\text{ V}$  and  $V_{CE,sat} = 0.3\text{ V}$ . You can neglect base currents in DC analysis.
- Calculate  $R_1$  to make the DC component of  $v_O$  equal to 6 V.
  - Calculate  $V_{CE}$  in  $Q_1$  and  $Q_3$ .
  - Draw the common-mode small-signal half-circuit and calculate the common-mode gain.
  - Draw the differential-mode small-signal half-circuit and calculate  $R_{EE}$  for a differential-mode gain equal to 10.



8. Design a voltage regulator based on the KA7809E to provide 9 V to a load of at least 15  $\Omega$ . The regulator is encapsulated in a TO-220 package with  $\theta_{JA}=65^\circ\text{C}/\text{W}$ ,  $\theta_{JC}=5^\circ\text{C}/\text{W}$  (assume  $\theta_{CS}=0.5^\circ\text{C}/\text{W}$ ),  $T_{MAX} = 125\text{ }^\circ\text{C}$  and the ambient temperature is 40  $^\circ\text{C}$ . Refer to the attached specification table for electrical parameters. Specify the following for your design: circuit schematic, supply voltage, minimum required supply current, maximum power dissipated in regulator and maximum heat allowable sink resistance (if needed at all).

**Electrical Characteristics (KA7809E / KA7809ER)**Refer to test circuit,  $-40^{\circ}\text{C} < T_J < 125^{\circ}\text{C}$ ,  $I_O = 500\text{ mA}$ ,  $V_I = 15\text{ V}$ ,  $C_I = 0.33\text{ }\mu\text{F}$ ,  $C_O = 0.1\text{ }\mu\text{F}$ , unless otherwise specified.

Symbol	Parameter	Conditions	Min.	Typ.	Max.	Unit	
$V_O$	Output Voltage	$T_J = +25^{\circ}\text{C}$	8.65	9.00	9.35	V	
		$5.0\text{ mA} \leq I_O \leq 1.0\text{ A}$ , $P_O \leq 15\text{ W}$ , $V_I = 11.5\text{ V to }24\text{ V}$	8.60	9.00	9.40		
Regline	Line Regulation <sup>(9)</sup>	$T_J = +25^{\circ}\text{C}$	$V_I = 11.5\text{ V to }25\text{ V}$		6	180	mV
			$V_I = 12\text{ V to }17\text{ V}$		2	90	
Regload	Load Regulation <sup>(9)</sup>	$T_J = +25^{\circ}\text{C}$	$I_O = 5\text{ mA to }1.5\text{ A}$		12	180	mV
			$I_O = 250\text{ mA to }750\text{ mA}$		4	90	
$I_Q$	Quiescent Current	$T_J = +25^{\circ}\text{C}$		5	8	mA	
$\Delta I_Q$	Quiescent Current Change	$I_O = 5\text{ mA to }1.0\text{ A}$ $V_I = 11.5\text{ V to }26\text{ V}$			0.5	mA	
					1.3		
$\Delta V_O/\Delta T$	Output Voltage Drift <sup>(10)</sup>	$I_O = 5\text{ mA}$		-1		mV/ $^{\circ}\text{C}$	
$V_N$	Output Noise Voltage	$f = 10\text{ Hz to }100\text{ kHz}$ , $T_A = +25^{\circ}\text{C}$		58		$\mu\text{V}$	
RR	Ripple Rejection <sup>(10)</sup>	$f = 120\text{ Hz}$ , $V_I = 13\text{ V to }23\text{ V}$	56	71		dB	
$V_{\text{drop}}$	Dropout Voltage	$I_O = 1\text{ A}$ , $T_J = +25^{\circ}\text{C}$		2		V	
$R_O$	Output Resistance <sup>(10)</sup>	$f = 1\text{ kHz}$		17		m $\Omega$	
$I_{\text{SC}}$	Short-Circuit Current	$V_I = 35\text{ V}$ , $T_A = +25^{\circ}\text{C}$		250		mA	
$I_{\text{PK}}$	Peak Current <sup>(10)</sup>	$T_J = +25^{\circ}\text{C}$		2.2		A	

**Notes:**

9. Load and line regulation are specified at constant junction temperature. Changes in  $V_O$  due to heating effects must be taken into account separately. Pulse testing with low duty is used.
10. These parameters, although guaranteed, are not 100% tested in production.