


ENGI 5131

Midterm Exam — Winter 2017


Parameters for all problems: $I_{SQn} = 280 \text{ nA}$, $V_{thn} = 0.5 \text{ V}$, $|\partial L/\partial V_{DS}|_n = 0.03 \text{ } \mu\text{m/V}$, $I_{SQp} = 80 \text{ nA}$, $V_{thp} = -0.55 \text{ V}$, $|\partial L/\partial V_{DS}|_p = 0.04 \text{ } \mu\text{m/V}$, $n_n = n_p = 1.3$, $t_{OX} = 6 \text{ nm}$ and $A_{\beta} = 3 \text{ } \%$.

Note: show units for all results.

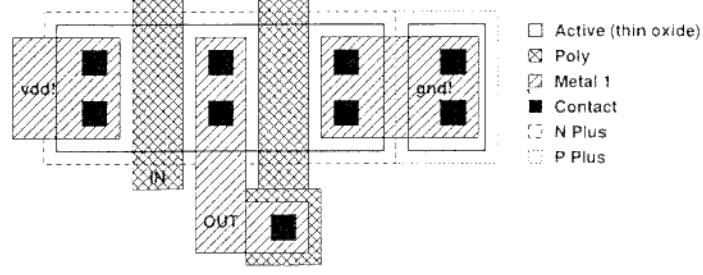
- The following layout is for a process with p-type substrate. Draw an schematic diagram of the circuit in this layout. Use the provided node labels.




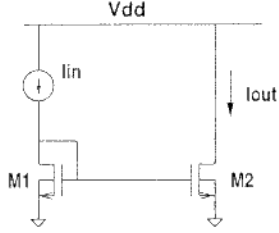- In the figure, $I_{in} = 20 \text{ } \mu\text{A}$, $V_{DD} = 2.5 \text{ V}$ and $(W/L)_1 = (W/L)_2 = (2 \text{ } \mu\text{m}/2 \text{ } \mu\text{m})$.
 - Calculate I_{out} considering the effect of channel-length modulation, assuming perfect matching. Show calculation steps.
 - Neglecting channel-length modulation, estimate the standard deviation in output current due to transistor mismatch.




- A standard cascode PMOS current mirror is designed to operate at an inversion level of 30. The supply voltage is 3 V.
 - What is the maximum output voltage (at the load) that the mirror can handle?
 - If the design is changed to a high-swing cascode (with same inversion level), what is the maximum output voltage that the mirror can handle?
- In the figure, $I_{in} = 0.5 \text{ } \mu\text{A}$, $V_{DD} = 3 \text{ V}$ and all transistors are equal with $(W/L) = 20$. Justify your answers.
 - Specify regions of operation for each of M1, M2 and M3: inversion level (weak, moderate or strong) and triode or active.
 - Neglecting channel-length modulation calculate i_{r2} and i_{r2} .

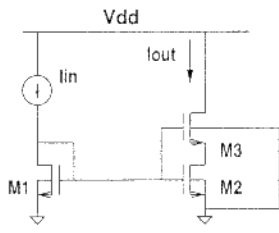

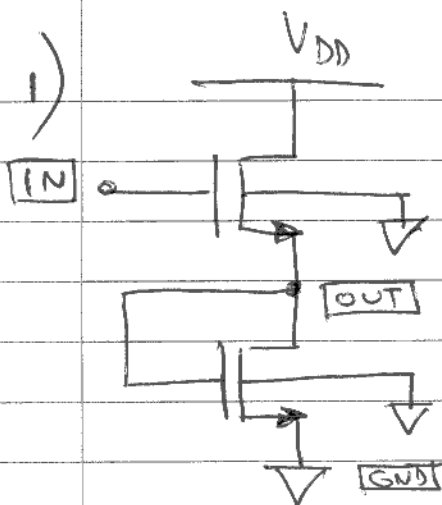

(+3) CLEAR LABELS CORRECT

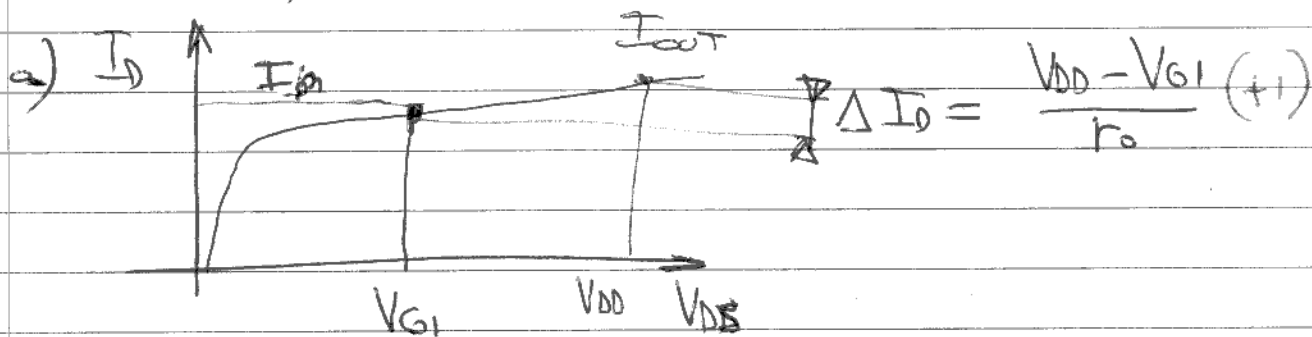2) $I_{in} = 20 \mu A$ $V_{DD} = 2.5 V$ $\frac{W}{L} = \frac{2 \mu m}{2 \mu m}$



$$V_{G1} = V_{th} + n V_T f(I_f)$$

$$I_f = \frac{20 \mu A}{I_{se} \frac{W}{L}} = 71.4 \approx \sqrt{71.4}$$

$$V_{G1} = 0.5 V + 1.3 \times 26 mV \times 8.52 = 0.79 V (+1)$$

$$I_{OUT} = I_{in} + \frac{V_{DD} - V_{G1}}{r_o} = I_{in} + \frac{V_{DD} - V_{G1}}{V_A} \times I_{in}$$

$$= I_{in} \left(1 + \frac{V_{DD} - V_{G1}}{V_A} \right)$$

$$V_A = \frac{L}{\left| \frac{\partial I_D}{\partial V_{DS}} \right|} = \frac{2 \mu m}{0.03 \frac{\mu m}{V}} = 66.7 V (+1)$$

$$\therefore I_{out} = 20 \mu A (1 + 0.026)$$


$$\approx \boxed{20.5 \mu A} \quad (+1)$$

$$b) \sigma \left(\frac{\Delta I_D}{I_D} \right)^2 = \frac{2}{4 (\mu m)^2} \left[\underbrace{\left(\frac{6 \text{ mV } \mu m}{1.3 \times 26 \text{ mV}} \right)^2}_{0.032} \underbrace{\ln(1+71.4)}_{0.659} + \underbrace{(0.03 \mu m)^2}_{0.0009} \right]$$

$$= 0.014 (+1)$$

$$\therefore \sigma \left(\frac{\Delta I_D}{I_D} \right) = \sqrt{0.014} = 0.037 = 3.7\% \quad (+1)$$

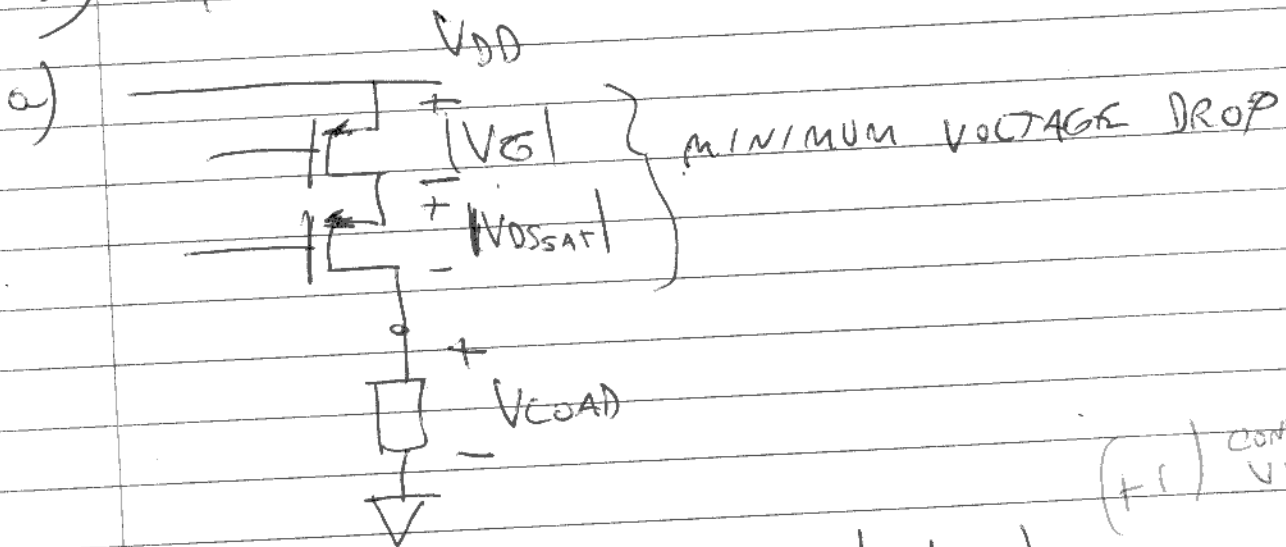3) $i_f = 30$ $V_{DD} = 3V$ (PMOS CASCODE MIRROR)




$$\therefore V_{LOAD \text{ MAX}} = V_{DD} - |V_{DSAT}| - |V_G| \quad ?$$

$$|V_G| = |V_{thp}| + n V_T \left(\frac{i_f}{I_D} \right) = 0.722V \quad (+1)$$

$$|V_{DSAT}| = V_T \left(3 + \underbrace{\sqrt{1+i_f'}}_{5.56} \right) = 0.223 V \quad (\#4)$$
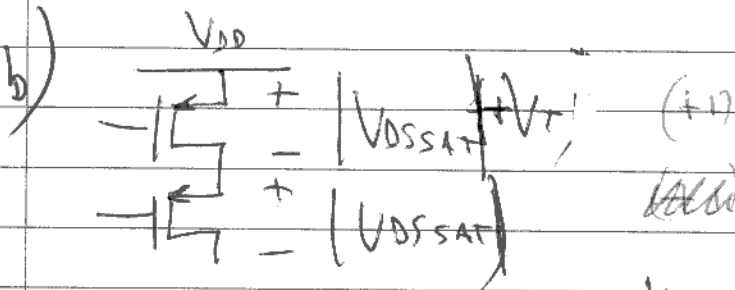
$$V_{LOAD MAX} \approx 2.05 V \quad (+1)$$



$$\begin{aligned} \therefore V_{LOAD MAX} &= V_{DD} - \underbrace{2|V_{DSAT}| - V_T}_{= V_T(6 + 2\sqrt{1+i_f'} + 1)} \\ &= V_T(6 + 2\sqrt{1+i_f'} + 1) \end{aligned}$$

$$V_{LOAD MAX} = V_{DD} - V_T(7 + 2\sqrt{1+i_f'}) \approx 2.53 V \quad (+2)$$

4) M_1 : DIODE-CONNECTED \rightarrow ACTIVE (+2) M_1, M_3

$$i_{f1} = \frac{0.5 \mu A}{20 I_{SQ}} = 0.089 \Rightarrow \text{WEAK INVERSION} \quad (\#4)$$

(WE SHOULD ACTUALLY VERIFY THAT $V_G > V_{DSAT}$ TO BE SURE OF ACTIVE REGION) (+1) BONUS

$$V_{G1} = 0.5 V + n V_T \ln(0.089) = 1.69 V > 100 mV \quad (OK)$$

M_2 : $\frac{V_G - V_{th}}{n} = V_p$ SAME AS $M_1 \Rightarrow$ WEAK INVERSION

$$\frac{V_p - 0}{V_T} = \ln(i_{f2}) \quad \frac{V_p - V_{D2}}{V_T} = \ln(i_{r2}) \quad (1)$$

($i_{f2} = i_{f1}$) CAN NOT TELL IF ACTIVE OR NOT YET.

M3: $V_{P3} = V_{P2} = V_{P1} \Rightarrow$ ALL WEAK INVERSION ⁽⁺¹⁾

$$\frac{V_P - V_{S3}}{V_T} = f(i_{F3}) \quad (2)$$

SINCE $V_{D3} = V_{DD} = 3V \Rightarrow V_{DS3}$ LARGE \Rightarrow ACTIVE ^{M3}

$$I_{OUT} = I_S i_{F3} = I_S (i_{F2} - i_{r2})$$

$$\text{BUT } V_{S3} = V_{D2} \Rightarrow i_{F3} = i_{r2}$$

↑
FROM (1), (2)

b) \therefore M2 ⁽⁺¹⁾ IS IN TRIODE SINCE i_{r2} IS SIGNIFICANT.

$$I_{OUT} = I_S i_{F3} = \underbrace{I_S i_{r2}} = I_S (i_{F2} - i_{r2})$$

$$2 I_S i_{r2} = I_S i_{F2}$$

$$i_{r2} = \frac{i_{F2}}{2} \quad (+1)$$

$$i_{F2} = i_{F1} = 0.089$$

$$i_{r2} = \frac{0.089}{2} \approx 0.045 \quad (+1)$$

$$I_{OUT} = \frac{I_{in}}{2}$$