

0.0.1 Current-Controlled Current Source

F

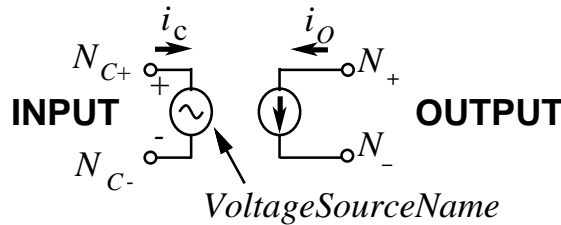


Figure 1: F — current-controlled current source element.

Form:

Fname N_+ N_- *VoltageSourceName* *Gain*

Fname N_+ N_- POLY(D) *VoltageSourceName*₁ ... *VoltageSourceName* _{D} *PolynomialCoefficients*

N_+	is the positive voltage source node.
N_-	is the negative voltage source node.
<i>VoltageSourceName</i>	is the name of the voltage source the current through which is the controlling current. The voltage source must be a V element.
<i>Gain</i>	is the current gain.
POLY	is the identifier for the polynomial form of the element D is the degree of the polynomial. The number of pairs of controlling nodes must be equal to <i>Degree</i> .
<i>VoltageSourceName</i> _{i}	is the name of the voltage source the current through which is the i th controlling current. The voltage source must be a V element.
<i>PolynomialCoefficients</i>	is the set of polynomial coefficients which must be specified in the standard polynomial coefficient format discussed in the description.

Example:

F1 2 3 14 1 2.0

Description:

Polynomial expressions can be used with the controlled source elements (E, F, G and H) to realize nonlinear controlled sources. The specification of the polynomial must be at the end of the input line and has two forms.

The format for a current-controlled current source (the F element) is

POLY(N) *VoltageSourceName*₁ ... *VoltageSourceName* _{N} C_0 C_1 C_2 C_3 ...

where

POLY is the keyword indicating that that a polynomial description follows.
N is the degree of the polynomial.
VoltageSourceName₁ is the name of the voltage source the current through which is control current I_1 .
VoltageSourceName_N is the name of the voltage source the current through which is control current I_N .
C₀ C₁ ... are the polynomial coefficients.
 For these elements the output is calculated as

$$\begin{aligned}
 \text{OUTPUT} = & C_0 \\
 & + C_1 V_1 + \dots + C_N V_N \\
 & + C_{N+1} V_1 V_1 + C_{N+2} V_1 V_2 + \dots + C_{N+N} V_1 V_N \\
 & + C_{2N+1} V_2 V_2 + C_{2N+2} V_2 V_3 + \dots + C_{2N+N-1} V_2 V_N \\
 & \vdots \\
 & + C_{N!/(2(N-2)!)+2N} V_N V_N \\
 & + C_{N!/(2(N-2)!)+2N+1} V_1 V_1 V_1 + C_{N!/(2(N-2)!)+2N+2} V_1 V_1 V_2 \quad (1) \\
 & + \dots + C_{N!/(2(N-2)!)+2N+N-1} V_1 V_1 V_N \\
 & + C_{N!/(2(N-2)!)+3N} V_1 V_2 V_2 + \dots + C_{N!/(2(N-2)!)+3N+N-2} V_1 V_2 V_N \\
 & \vdots \quad (2)
 \end{aligned}$$

An example of a current-controlled current source is:

F1 2 3 POLY(4) VIN V2 (11,0) (13,0) 0.5 1 1 1 1 0.2 0.3 0.2.

Linear Gain Instance

Fname **N₊** **N₋** **N_{C+}** **N_{C-}** **Gain**

The value of the voltage generator is linearly proportional to the controlling current:

$$v_o = \text{Gain} v_c. \quad (3)$$

POLYnomial Instance

Fname **N₊** **N₋** **POLY(D)** (**N_{C1+}** **N_{C1-}**) ... (**N_{CD+}** **N_{CD-}**) **PolynomialCoefficients**

The value of the voltage generator is a polynomial function of the controlling voltages:

$$v_o = f(i_{c1}, \dots, i_{ci}, \dots, i_{cD}) \quad (4)$$


where the number of controlling currents is D — the degree of the polynomial specified on the element line. i_{ci} is the i th controlling current and is the current flowing from the +

terminal to the – terminal in the i th voltage source of name *VoltageSourceName*.

Notes:

The actual element in *fREEDA*[™] is the **F** element. See **F** for full documentation.

Credits:

Name	Affiliation	Date	Links
Satish Uppathil svuppath@eos.ncsu.edu	NC State University	Sept 2000	 www.ncsu.edu